

Under the Hood of a Multiphase Synchronous Rectified Boost Converter


David Baba

Agenda


- **Synchronous boost introduction**
 - Deciding how many phases to use
- **Synchronous multiphase boost waveforms**
- **Design example single phase/two phase**
 - Component selection
 - Loss calculations
 - Compensation
- **Results**
- **Summary**

Changing to Synchronous Rectification

Non Synchronous Buck to Synchronous Buck

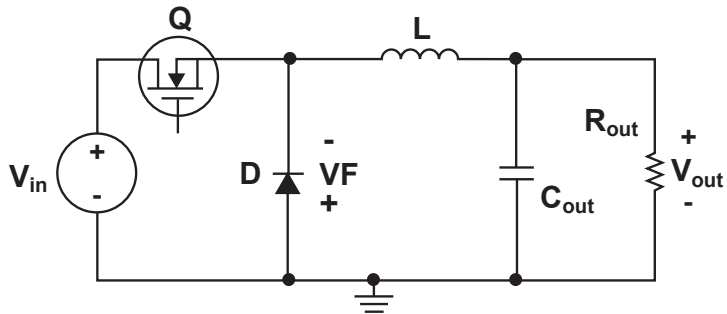

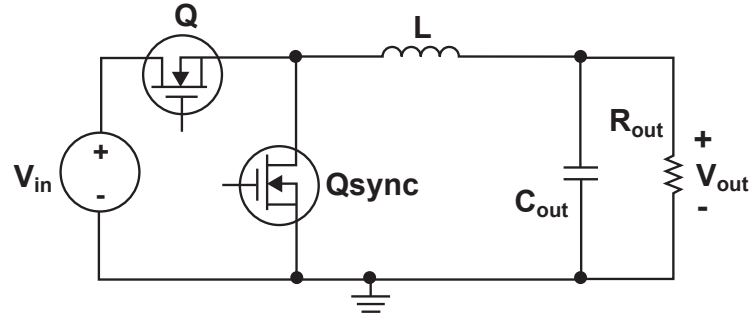
$$\text{Losses} = (1 - D) \times I_{\text{out}} \times VF$$




$$\text{Losses} = I_{\text{RMS}}^2 \times RDS_{\text{on}}$$

Non Synchronous to Synchronous Boost

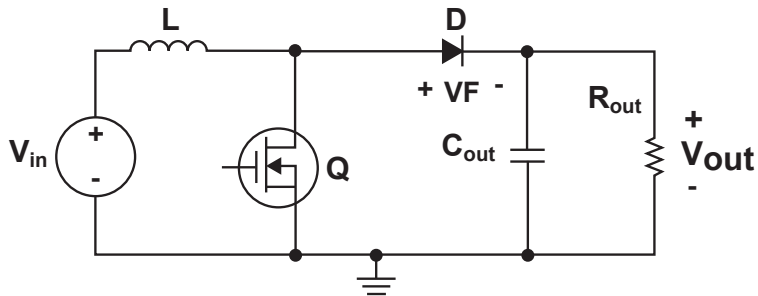

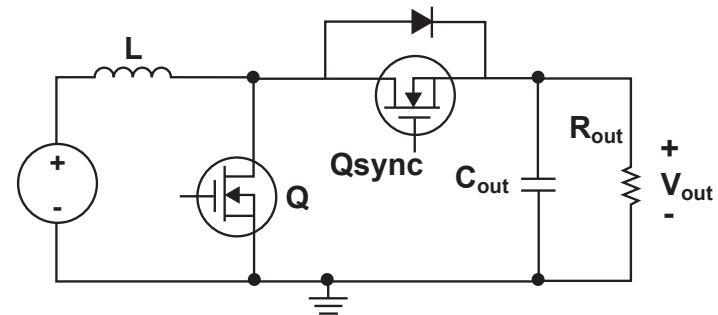
$$\text{Losses} = I_{\text{out}} \times V_F$$




$$\text{Losses} = I_{\text{RMS}}^2 \times RDS_{\text{on}}$$

Boost Converter Basic Operation


Simple Boost Diagram

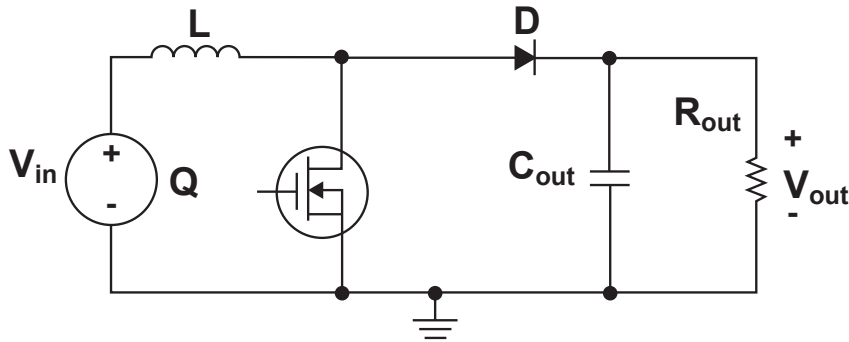

Boost During D_{ON} Period

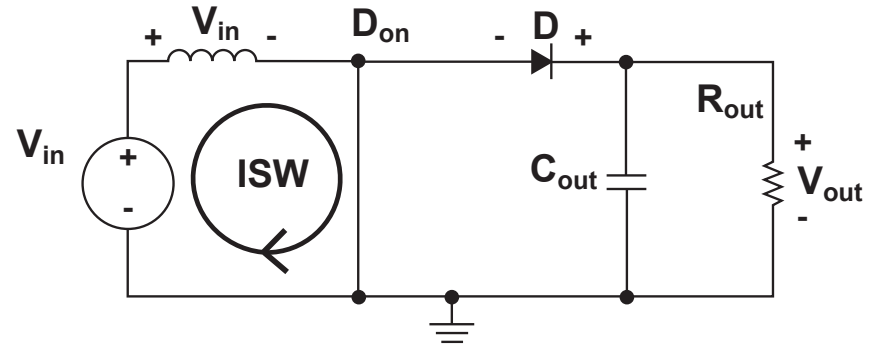


Boost During D_{OFF} Period

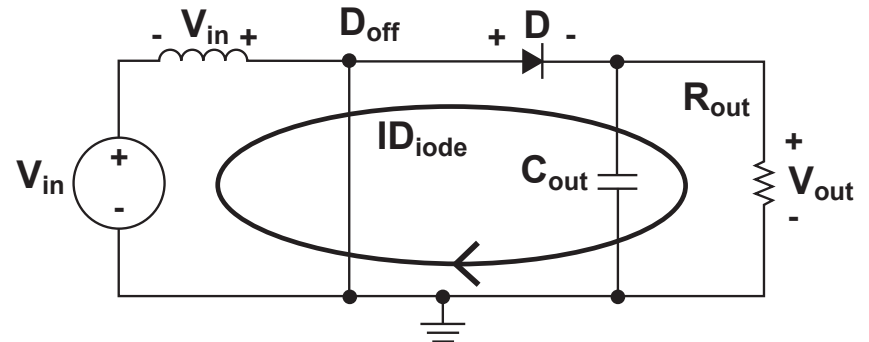


Determine Input Current per Phase

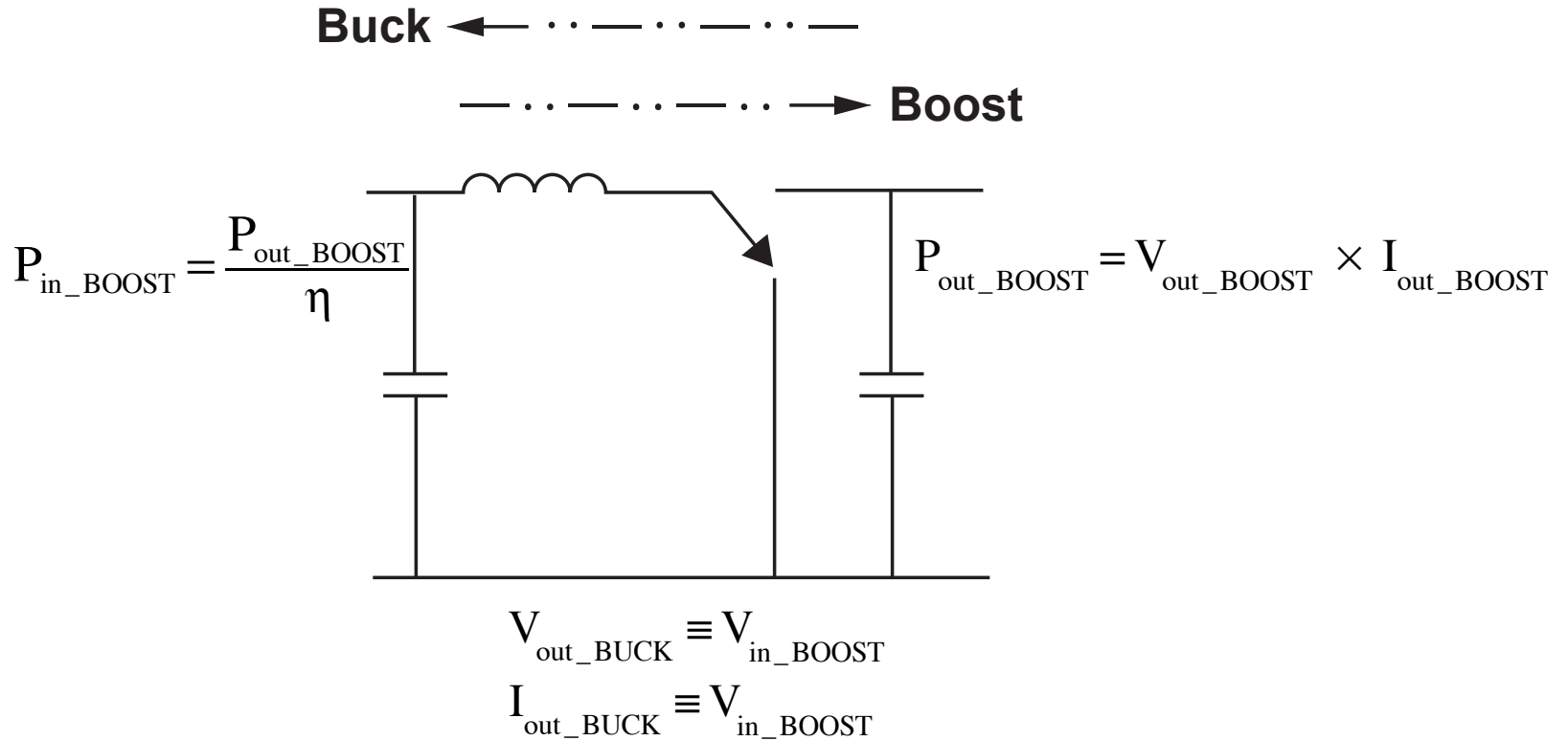Drawing Comparisons Between Buck and Boost




Canonical Schematic


Interleaved Boost Basic Operation

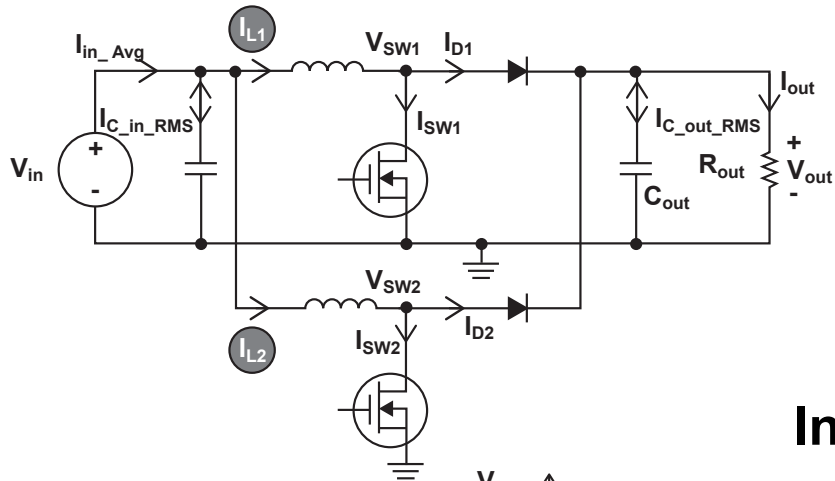





Inductor Currents

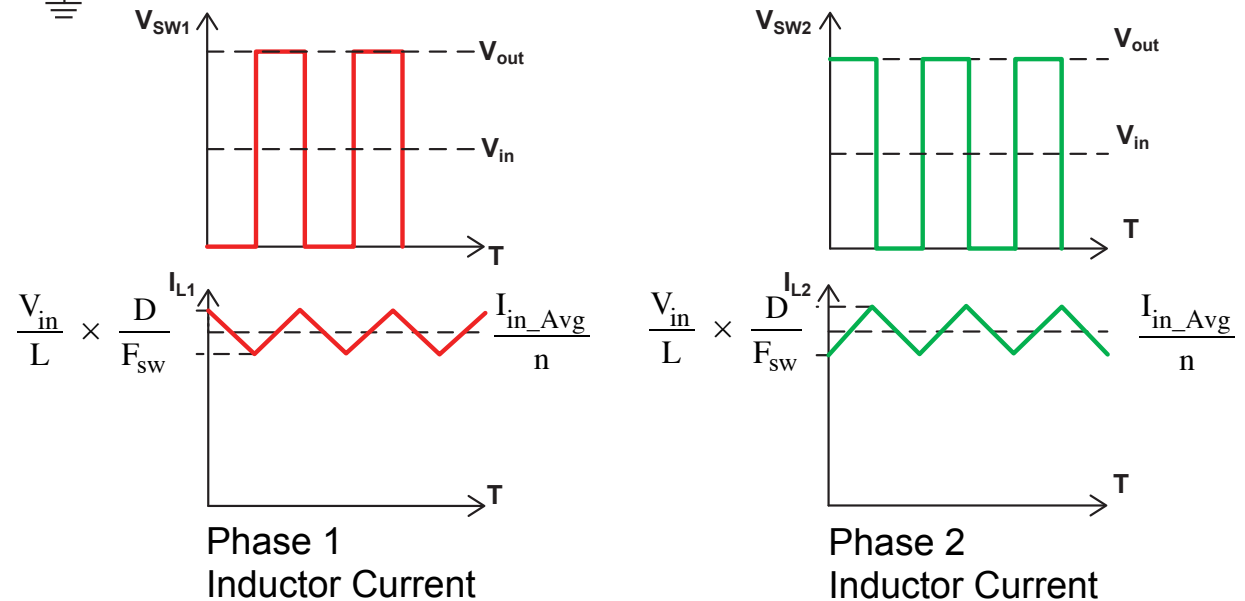

Interleaved Boost Basic Operation

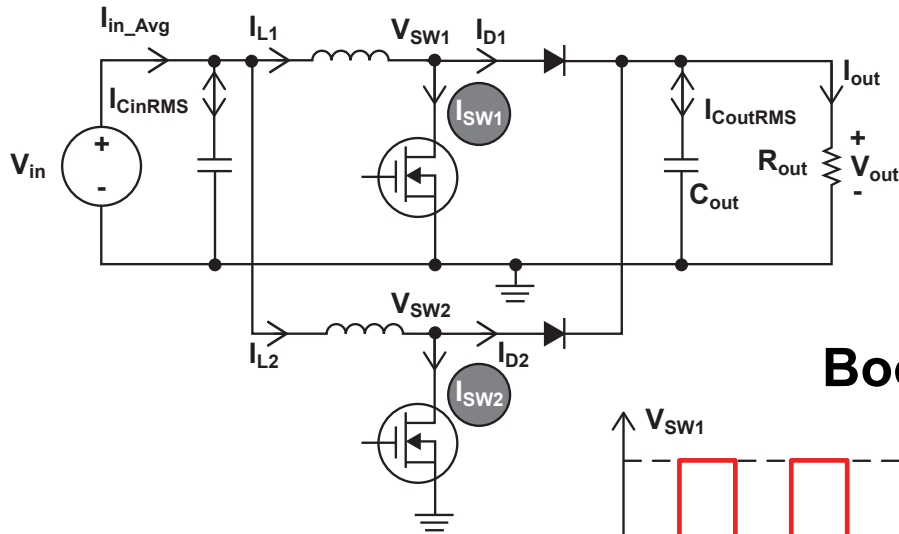


Boost Switch Currents

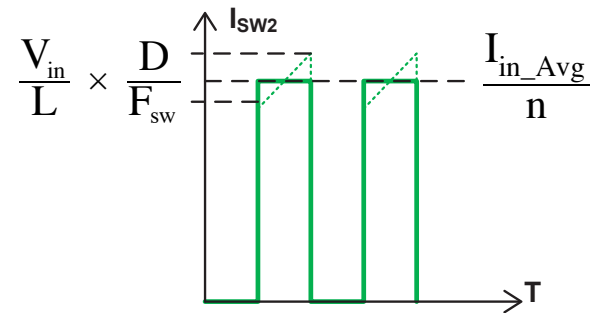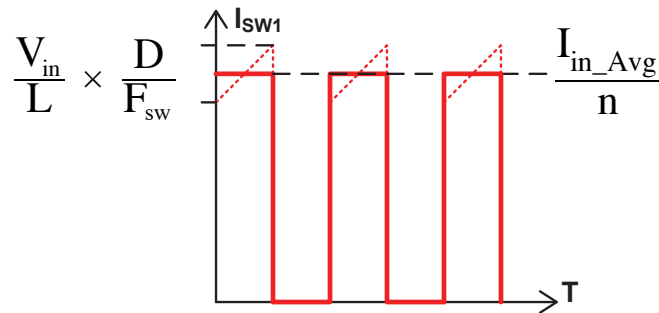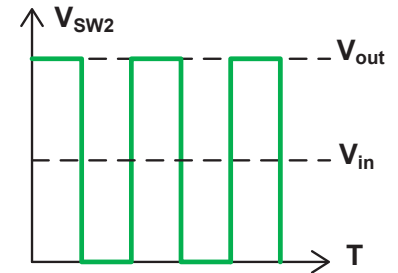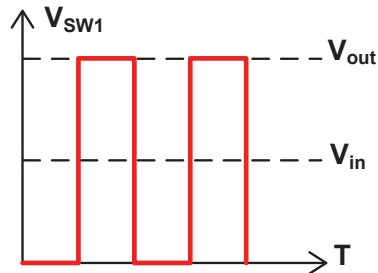





Phase 1 Switch Current

Phase 2 Switch Current

Interleaved Boost Basic Operation

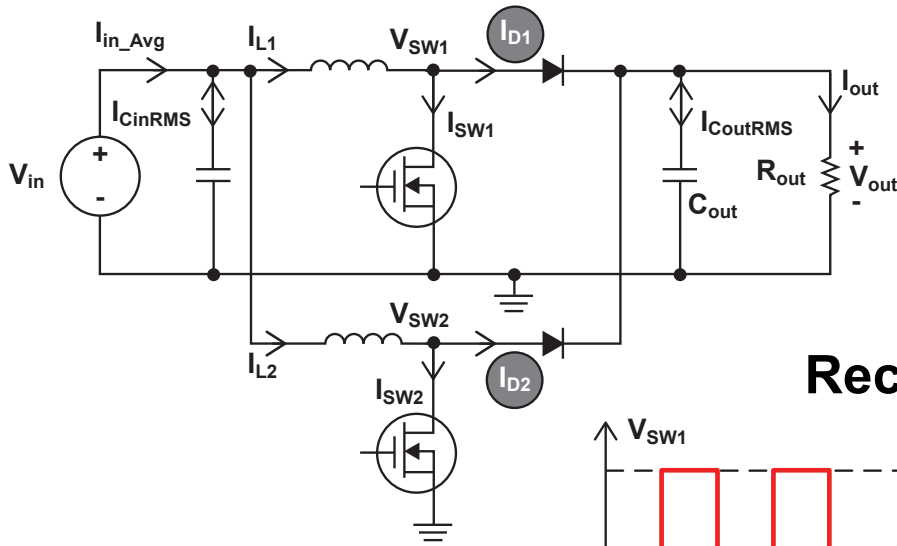


Rectifier Switch Currents

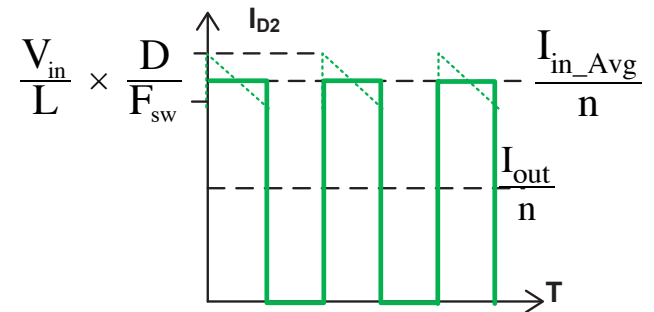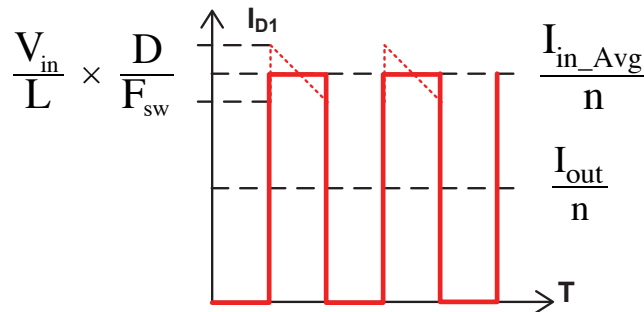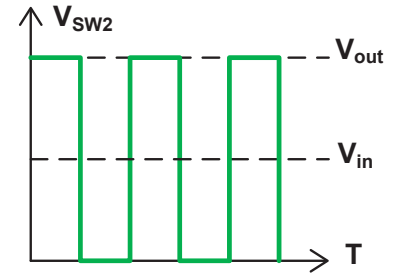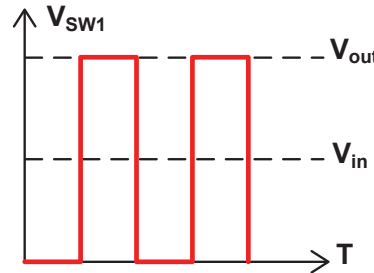




Phase 1 Rectifier Current

Phase 2 Rectifier Current

Interleaved Boost Basic Operation

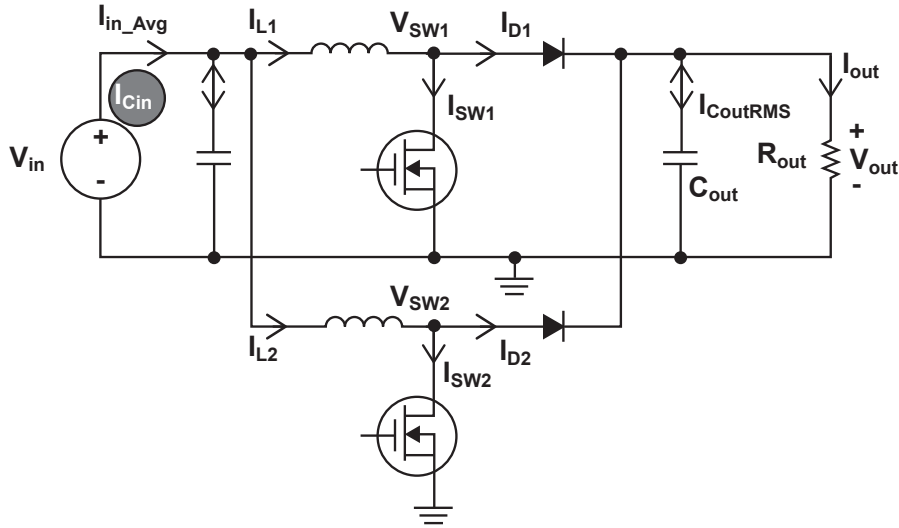


Input Capacitor Currents

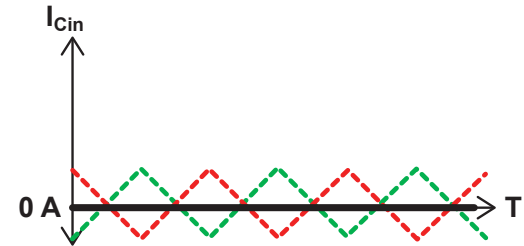
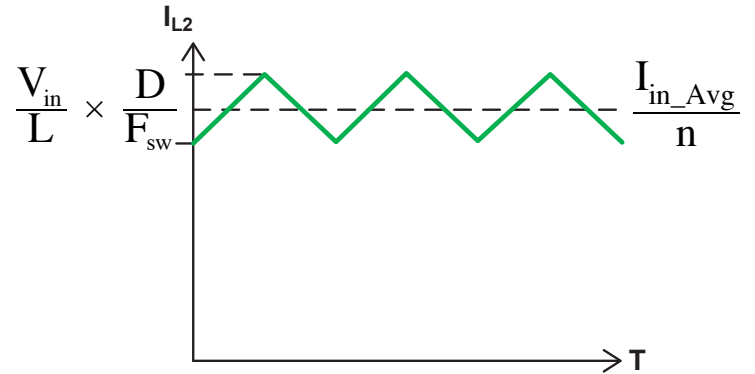
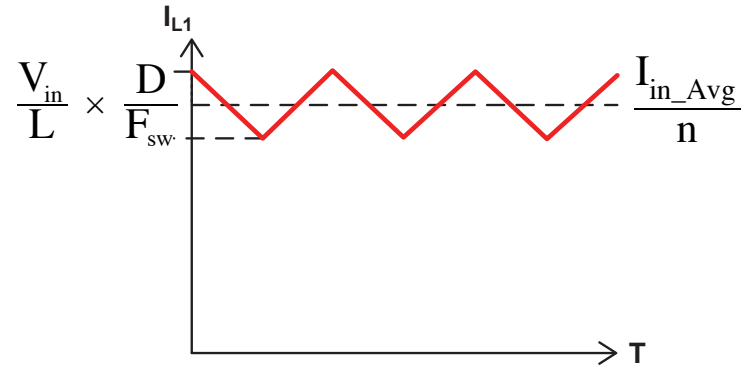


DC content removed
Ripple currents cancel at 50%

Interleaved Boost Basic Operation

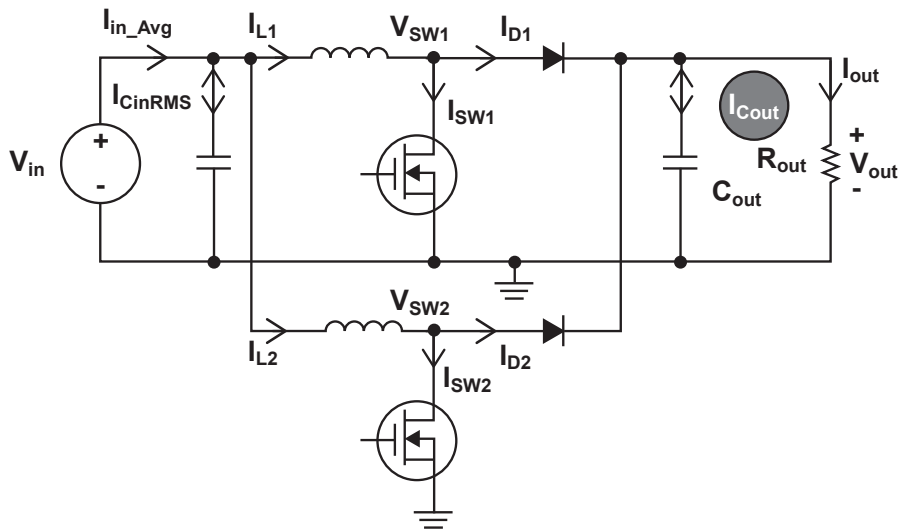

Output Capacitor Currents

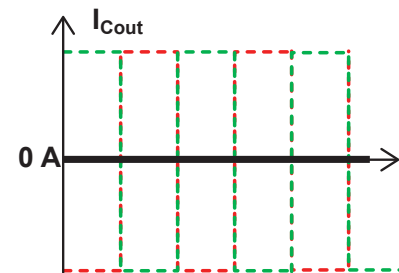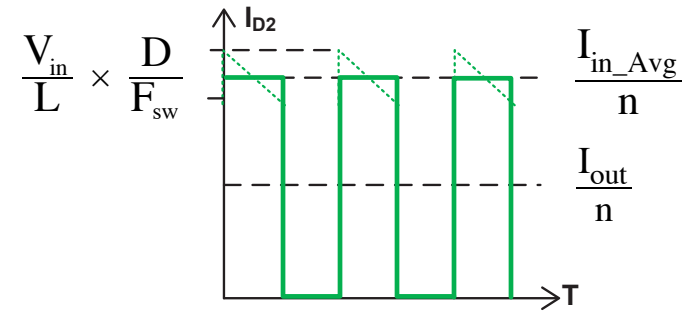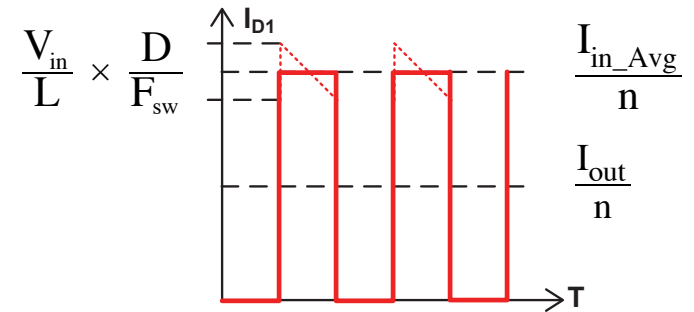

Ripple currents cancel at 50%

The Basic Boost Calculations


Design Example

- Automotive trunk amplifier
- 14 V_{in}
- 24 V_{out} @ 8 A
- Switching Frequency (F_{sw})
 - 250 kHz (single phase)
 - 125 kHz (two phase) system switching frequency held constant

Equation	Single Phase	Two Phase	Comment
	250 kHz	125 kHz	Per Phase F _{sw}
$\frac{V_{out}}{V_{in}} = \frac{1}{1-D}$	14.75 A = $\frac{206 \text{ W}}{14 \text{ V} \times 1}$	6.8 A = $\frac{206 \text{ W}}{14 \text{ V} \times 2}$	Transfer Function
$D = \frac{V_{out} - V_{in}}{V_{out}}$	D = 0.42	D = 0.42	Rearranging for D
$P_{in} = \frac{P_{out}}{\eta}$	P _{in} = 206 W	P _{in} = 206 W	Efficiency Est. 93%
$I_{in_Avg} = \frac{P_{in}}{V_{in} \times n}$	14.75 A = $\frac{206 \text{ W}}{14 \text{ V} \times 1}$	6.8 A = $\frac{206 \text{ W}}{14 \text{ V} \times 2}$	n = No. Phase

Selecting the Right Inductor and Inductance Calculations

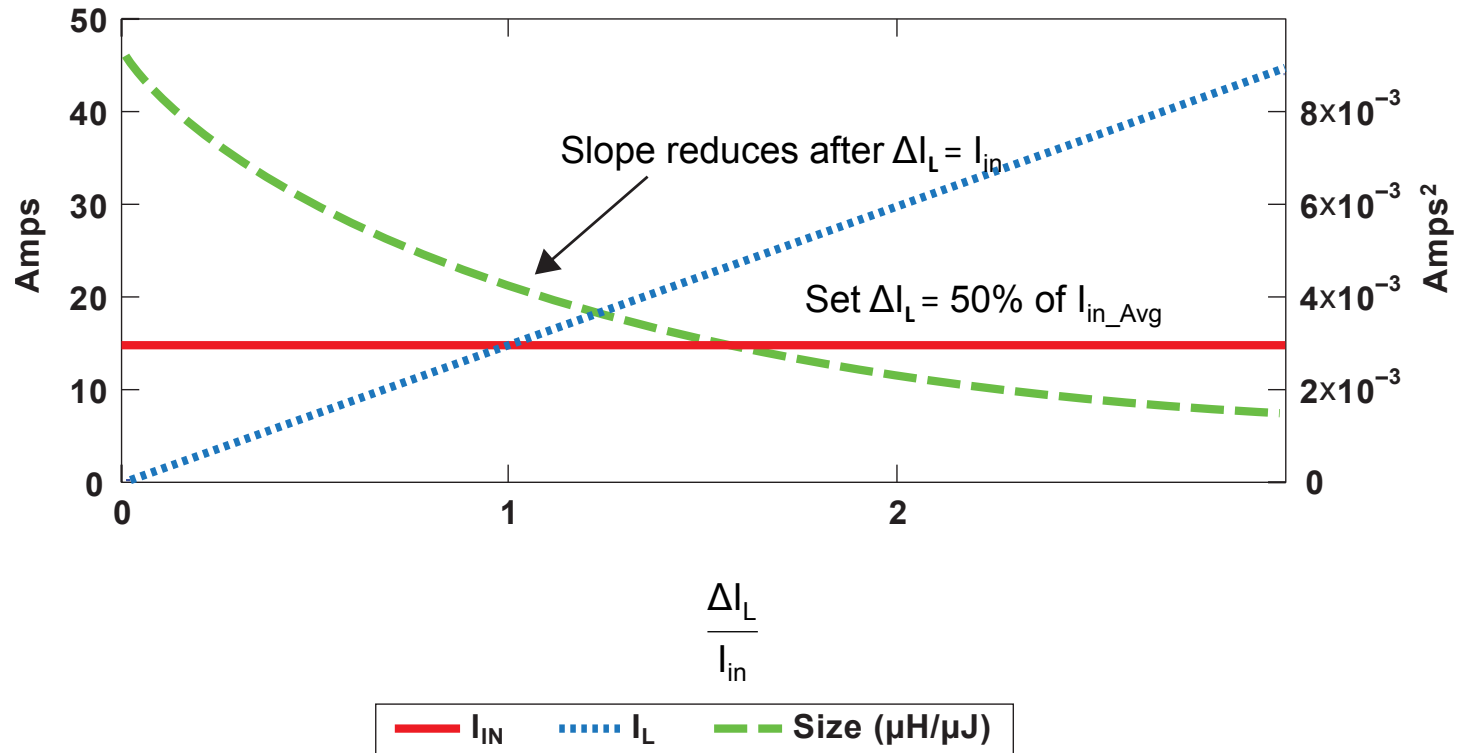Graph showing size factor as a function of ΔI_L



Boost Inductor Losses

Equation	Single Phase	Two Phase	Comment
$\Delta I_L = 0.5 \times I_{in_Avg}$	$\approx 7.5 \text{ A}$	$\approx 3.5 \text{ A}$	Set ΔI_L to 50% of I_{in_Avg}
$I_{L_peak} = \frac{\Delta I_L}{2} + I_{in_Avg}$	$= 18.5 \text{ A}$	$= 8.4 \text{ A}$	I_{sat} to be set higher than I_{L_peak}
$L = \frac{V_{ind} \times D}{\Delta I_L \times F_{SW}}$	$= 3.16 \mu\text{H}$	$= 13.4 \mu\text{H}$	Boost inductor calculation
$I_{L_RMS} = \sqrt{I_{in_Avg}^2 + \left(\frac{\Delta I_L}{\sqrt{12}}\right)^2}$	$= 14.9 \text{ A}$	$= 7 \text{ A}$	RMS current for DCR Loss
Selected Inductor	Coilcraft XAL1580-302	Coilcraft SER1390-153	2 cores for the two phase
Inductor size	13.2, 14.1, 7.5	13.5, 13.5, 9	Volume of inductor (in mm ³)
DCR	3 m Ω	14 m Ω	
$DCR_{loss} = I_{L_RMS}^2 \times DCR$	$= 0.6 \text{ W}$	$= 1.4 \text{ W}$	Total DCR losses
$Coreloss = K_1 \times f^x \times B^y \times V_E$	$= 2.6 \text{ W}$	$= 18 \text{ mW}$	Total from online calculator

AC Inductor Losses

$$\text{Coreloss} = K_1 \times f^x \times B^y \times V_E$$

- K_1 : Constant of the core material
- f : Switching frequency in kHz
 - **Higher frequencies results in higher losses**
- B : Flux density in kGuass
 - **Lower flux density results in lower losses**
- x : Frequency exponent for a specific core material
- y : is the flux exponent for a specific core material
- V_E : Core volume
 - **Larger volume results in more losses**

Boost Converter MOSFET Considerations


- VDS rating must be greater than output voltage
 - 25% margin is generally acceptable
- Calculate losses to determine suitability
- Losses ideally should be distributed evenly between conduction losses and switching losses
 - Higher RMS currents result in larger conduction losses
 - Higher gate charge results in higher switching losses

Control MOSFET Losses

Equation	Single Phase	Two Phase	Comment
FET Selected	CSD18531Q5A	CSD18531Q5A	RDS _{on} , 3 mΩ, hot 4 mΩ
$I_{FET_RMS} = \sqrt{D} \times I_{in_Avg}$	≈ 9 A	≈ 4.47 A	FET RMS current
$P_{FET_Cond} = I_{FET_RMS}^2 \times RDS_{on}$	≈ 0.3 W	≈ 0.16 W	Total conduction losses
$P_{TRANS_Loss} = V_{in} \times I_{in_Avg} \times T_{SLEW} \times F_{SW}$	≈ 0.5 W	≈ 0.24 W	Total transitional losses

Control MOSFET Transitional Losses

Transitional Losses at Turn On

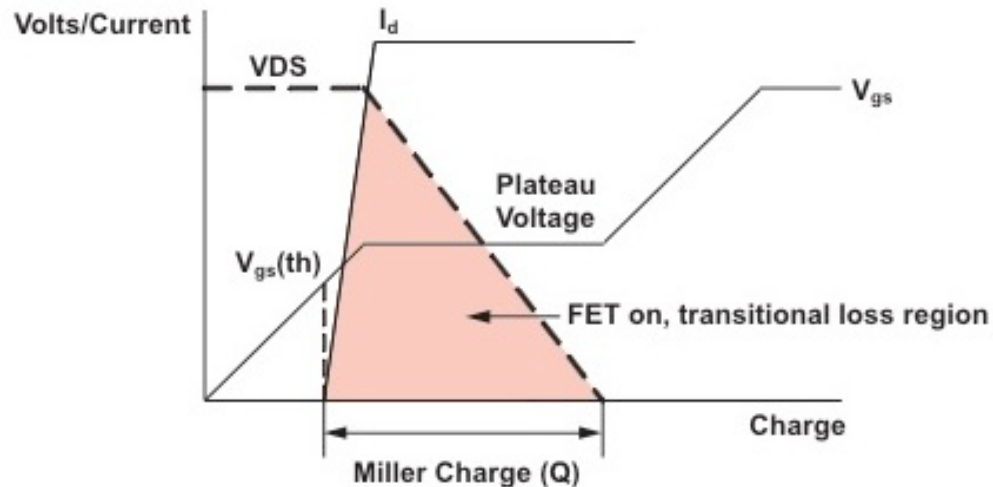

$$SW_{\text{TRANSLoss}} = V_{\text{in}} \times I_{\text{in_Avg}} \times T_{\text{SLEW}} \times F_{\text{SW}}$$



- Use triangular approximation
 - $1/2 \times \text{base} \times \text{height}$
 - For worst case, the “1/2” drops out

Synchronous MOSFET Losses

Equation	Single Phase	Two Phase	Comment
FET Selected	CSD18531Q5A	CSD18531Q5A	RDS _{on} , 3 mΩ, hot 4 mΩ
$I_{\text{FET_RMS}} = \sqrt{1-D} \times I_{\text{in_Avg}}$	≈ 11.2 A	≈ 5.3 A	FET RMS current
$\text{FETCond} = I_{\text{(FET_RMS)}}^2 \times \text{RDS}_{\text{on}}$	≈ 0.44 W	≈ 0.22 W	Conduction losses
$Q_{\text{OSSLoss}} = \frac{Q_{\text{OSS}}}{2} \times V_{\text{out}} \times F_{\text{SW}} \times n$	≈ 0.2 W	≈ 0.2 W	Q _{OSS} losses for both FETs
$Q_{\text{RR_Loss}} = Q_{\text{RR}} \times V_{\text{out}} \times n \times F_{\text{SW}}$	≈ 0.6 W	≈ 0.35 W	100 nC of Q _{RR} losses in boost FET
$I_{\text{C_Loss}} = V_{\text{in}} \times n \times \left\{ (Q_{\text{Gtot}} \times F_{\text{SW}}) + I_{\text{Q}} \right\}$	≈ 0.18 W	≈ 0.33 W	Loss total in IC



Boost Converter FET Switching

Control FET: Turn On

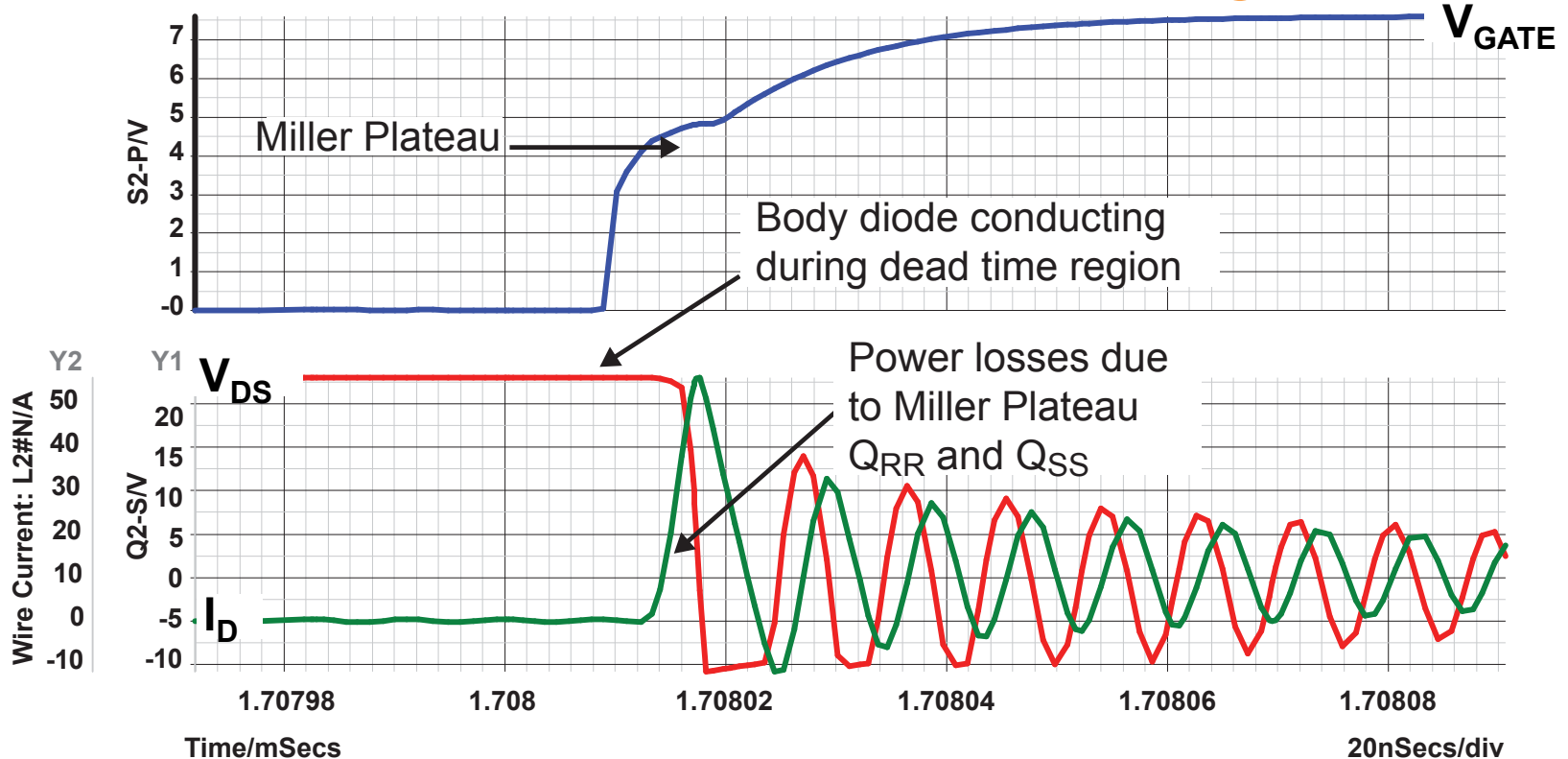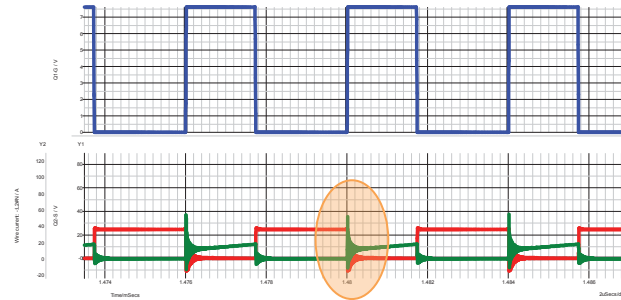



Boost Converter FET Switching

Control FET: Turn Off

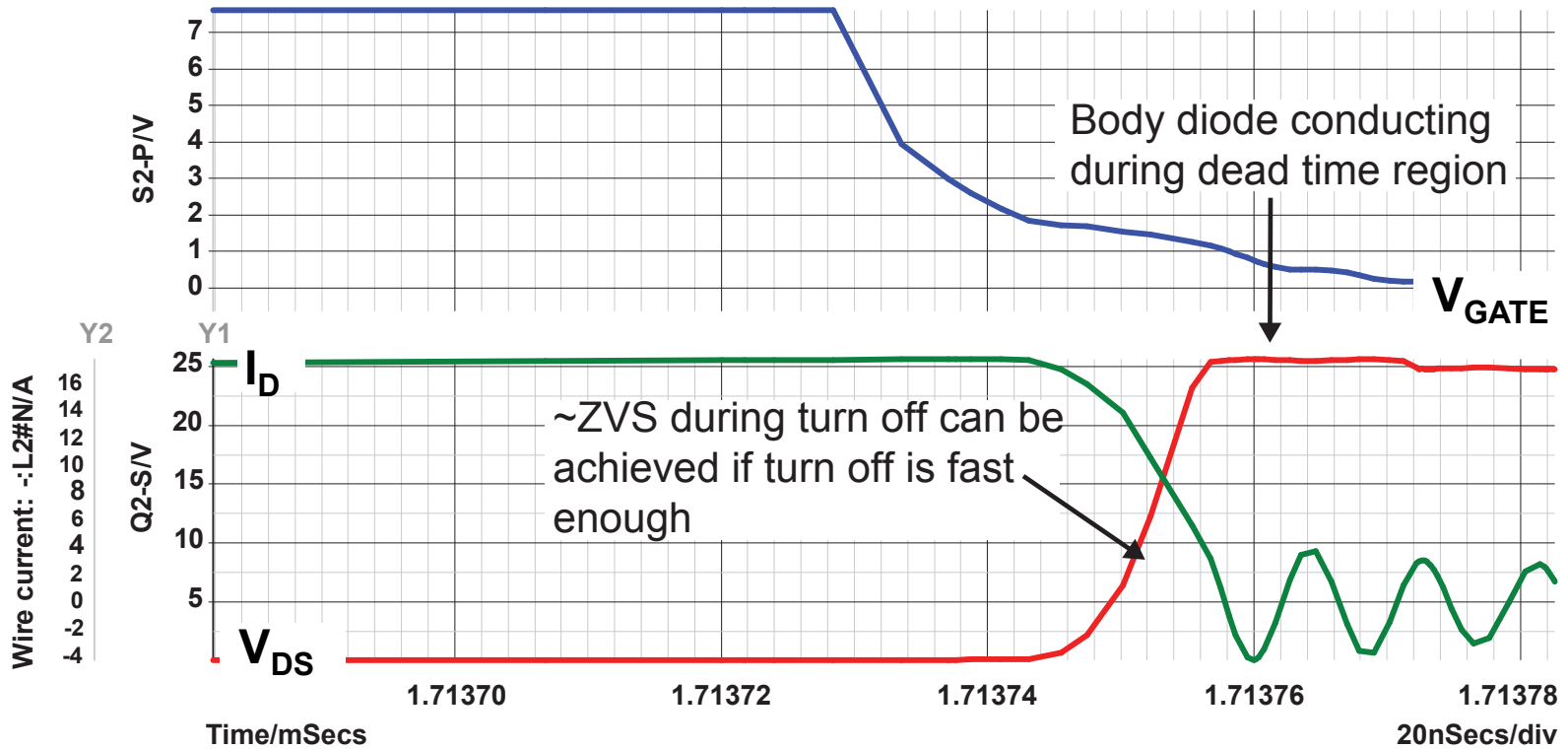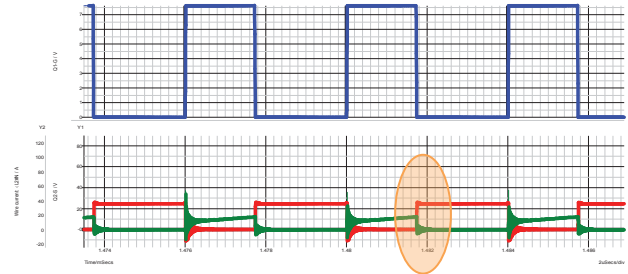



Boost Converter FET Switching

Synchronous FET: Turn On

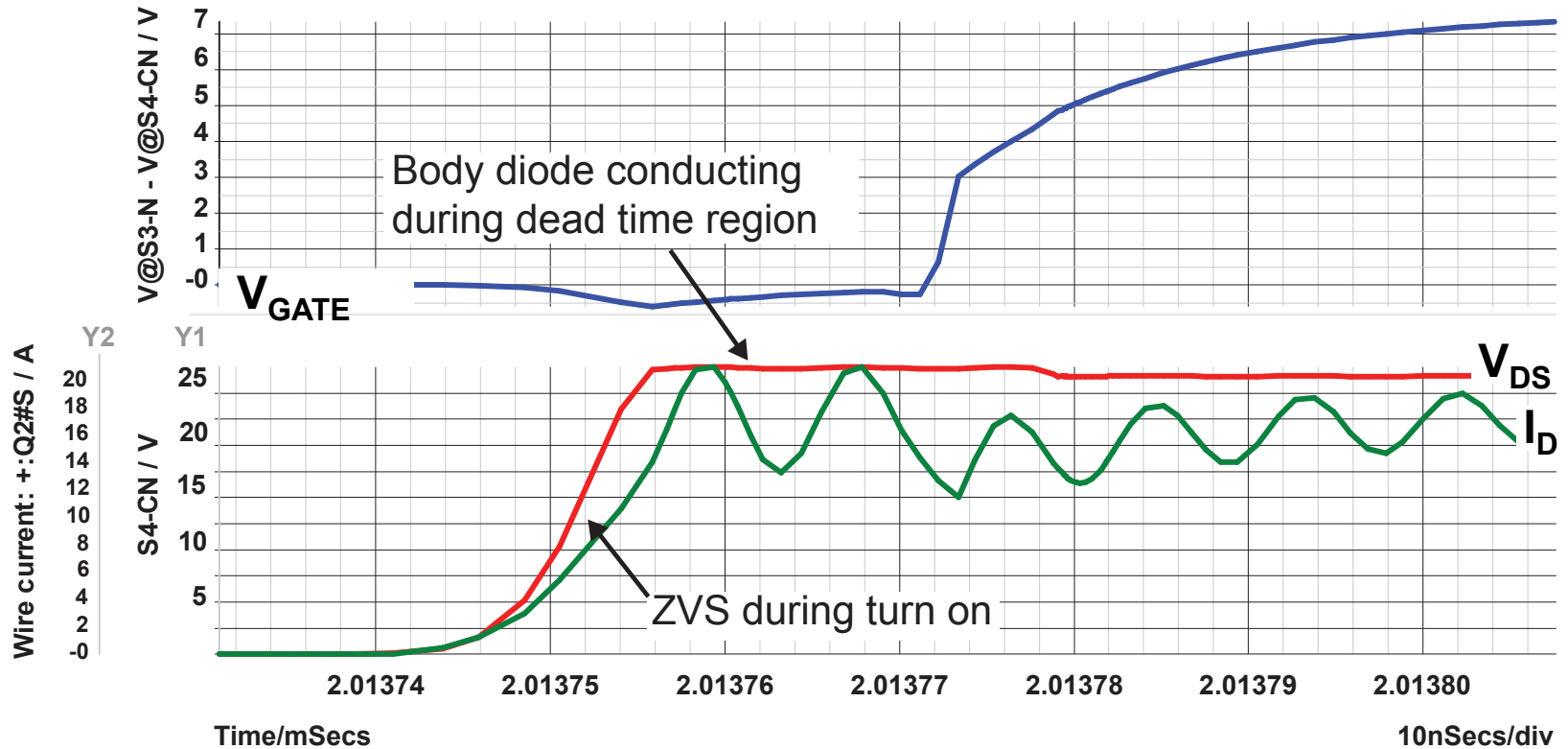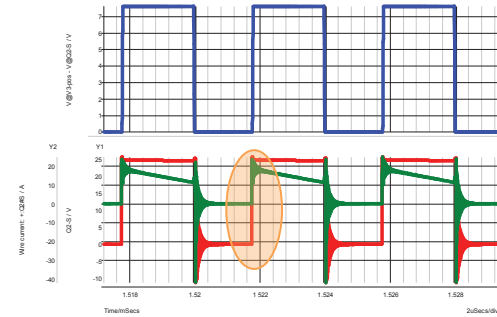

Boost Converter FET Switching

Synchronous FET: Turn Off

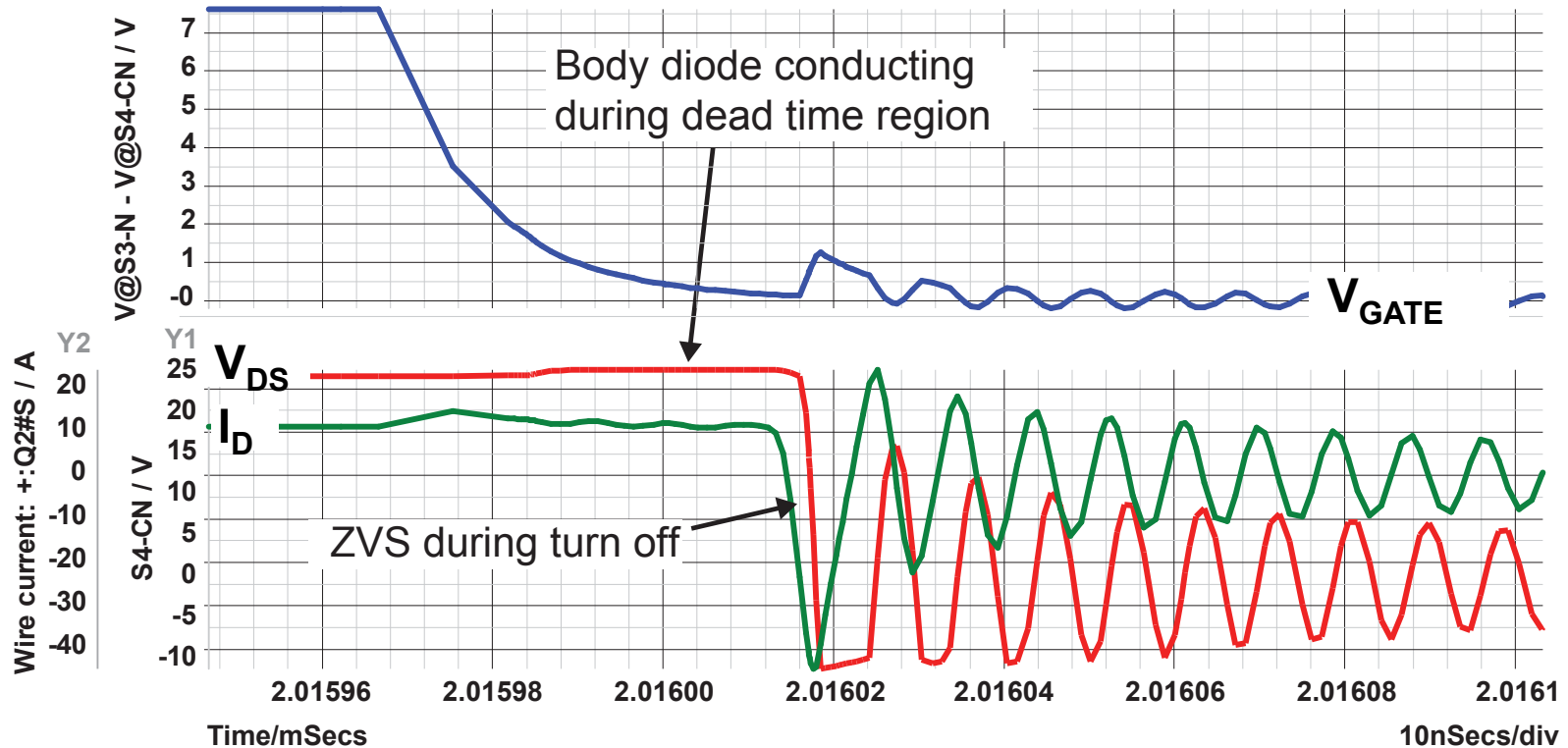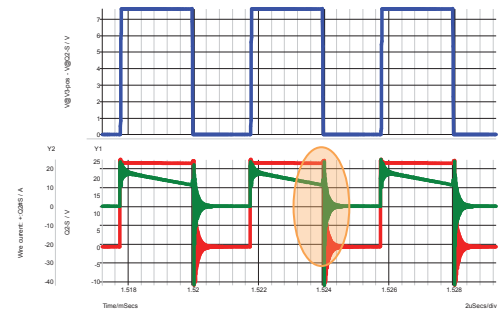

Input/Output RMS Ripple Current


Single Phase	Two Phase	Comment
$I_{C_in_RMS} = \frac{\Delta I_L}{\sqrt{12}} = 2.1 \text{ A}$	$I_{C_in_RMS} = \frac{\Delta I_L}{\sqrt{12}} \times \frac{1-2D}{1-D} = 0.9 \text{ A}$	Two phase D < 0.5
$I_{C_out_RMS} \approx I_{out} \times \sqrt{\frac{D}{(1-D)}} = 6.7 \text{ A}$	$I_{C_out_RMS} \approx \frac{I_{out}}{\sqrt{2}} \times \frac{\sqrt{D \times (1-2D)}}{(1-D)}$ = 2.5 A	Two phase D < 0.5
$\Delta I_{C_out} \approx I_{in_Avg} = 14.75 \text{ A}$	$\Delta I_{C_out} \approx I_{in_Avg} = 6.8 \text{ A}$	Pk-Pk ripple current in C _{OUT}
1 x PCV1E391MCL2GS	2 x PCV1E391MCL2GS	390 μF electrolytic selected

Output Ripple Voltage Calculations

Single Phase	Two Phase	Comment
$V_{C_out_Ripple} = \frac{\Delta I_{C_out} \times D}{F_{SW} \times C_{out}} = 29 \text{ mV}$	$V_{C_out_Ripple} = \frac{\Delta I_{C_out} \times D}{F_{SW} \times C_{out}} = 29 \text{ mV}$	Ripple voltage due to charge C_{out}
$\Delta I_{Cout} \approx \frac{I_{out}}{n \times (1-D)} = 13.7 \text{ A}$	$\Delta I_{Cout} \approx \frac{I_{out}}{n \times (1-D)} = 6.89 \text{ A}$	
$V_{C_out_Ripple_ESR} = \Delta I_{C_out} \times C_{out_ESR}$ $= 137 \text{ mV}$	$V_{C_out_Ripple_ESR} = \Delta I_{C_out} \times C_{out_ESR}$ $= 144 \text{ mV}$	Ripple voltage due to C_{outESR}
$V_{out_Ripple} =$ $\sqrt{V_{C_out_Ripple}^2 + V_{C_out_Ripple_ESR}^2}$ $= 140 \text{ mV}$	$V_{out_Ripple} =$ $\sqrt{V_{(C_out_Ripple)}^2 + V_{(C_out_Ripple_ESR)}^2}$ $= 147 \text{ mV}$	Total ripple voltage


C_{in} RMS Ripple Current Rating Multiphase Boost

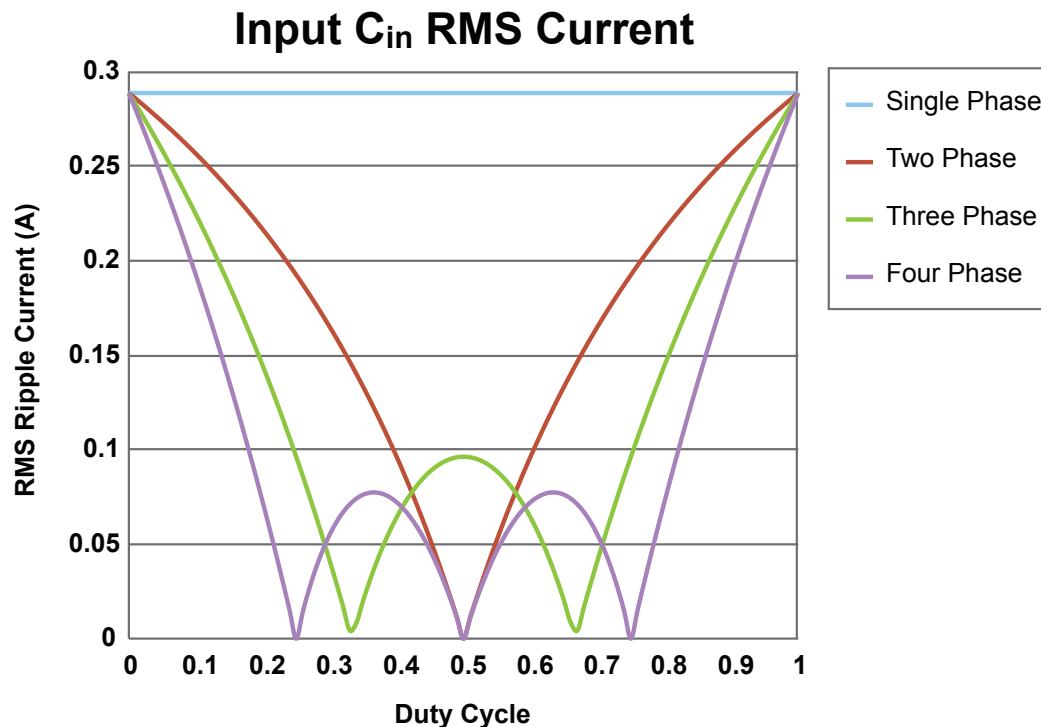- Comparison of ripple current cancelation
- Boost convertor 1, 2, 3 and 4 phase approach
- Using a ΔI_L of 1 A peak to peak



C_{out} RMS Ripple Current Rating Multiphase Boost

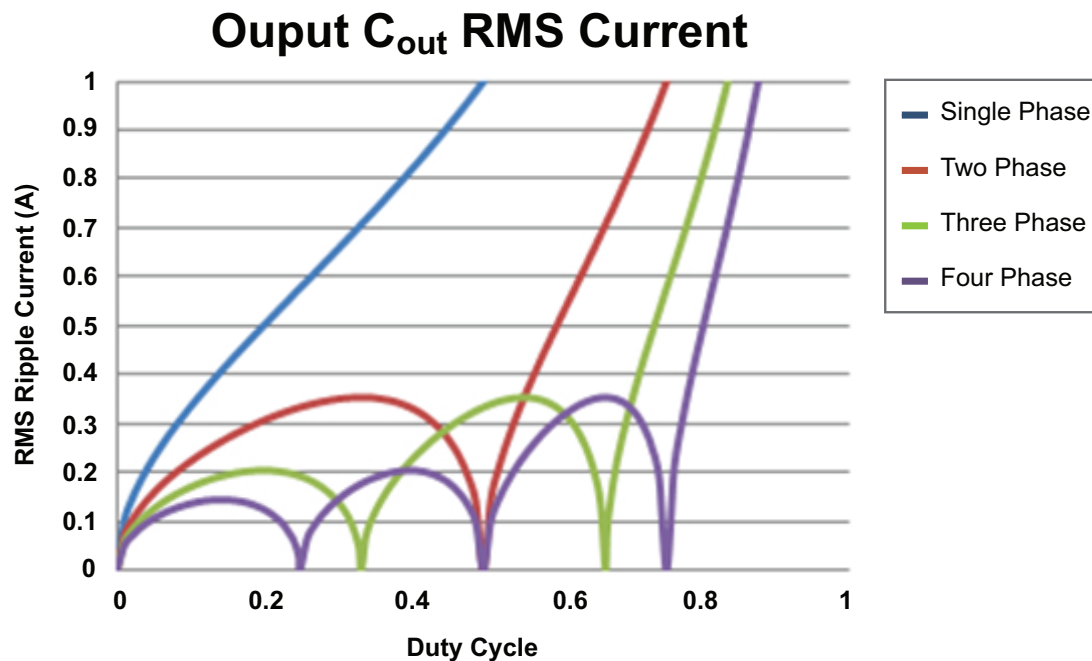- Approximation
- Output ripple current cancelation for a boost convertor
- I_{out} of 1 A using a 1, 2, 3 and 4 phase approach



C_{in} RMS Ripple Current

Condition	Single Phase
$0 < D < 1$	$\frac{\Delta I_L}{\sqrt{12}}$
Condition	Two Phase
$0 < D < 0.5$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{1-2D}{1-D}$
$0.5 < D < 1$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{2D-1}{D}$
Condition	Three Phase
$0 < D < 0.33$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{1-3D}{1-D}$
$0.33 < D < 0.66$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{(1-3D) \times (3D-2)}{3D \times (1-D)}$
$0.66 < D < 1$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{3D-2}{D}$

C_{in} RMS Ripple Current

Condition	Four Phase
$0 < D < 0.25$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{1-4D}{1-D}$
$0.25 < D < 0.5$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{(1-4D) \times (4D-2)}{4D \times (1-D)}$
$0.5 < D < 0.75$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{(3-4D) \times (4D-2)}{4D \times (1-D)}$
$0.75 < D < 1$	$\frac{\Delta I_L}{\sqrt{12}} \times \frac{4D-3}{D}$

C_{out} RMS Ripple Current*

Condition	Single Phase
$0 < D < 1$	$I_{OUT} \times \sqrt{\frac{D}{(1-D)}}$
Condition	Two Phase
$0 < D < 0.5$	$\frac{I_{OUT}}{\sqrt{2}} \times \frac{\sqrt{D \times (1-2D)}}{(1-D)}$
$0.5 < D < 1$	$\frac{I_{OUT}}{2} \times \frac{\sqrt{2 \times (2D-1)}}{\sqrt{1-D}}$
Condition	Three Phase
$0 < D < 0.33$	$\frac{I_{OUT}}{\sqrt{3}} \times \frac{\sqrt{D \times (1-3D)}}{(1-D)}$
$0.33 < D < 0.66$	$\frac{I_{OUT}}{3} \times \frac{(3D-2) \times (1-3D)}{(1-D)}$
$0.66 < D < 1$	$\frac{I_{OUT}}{3} \times \frac{\sqrt{3D-2}}{\sqrt{1-D}}$

*Approximations

C_{out} RMS Ripple Current*

Condition	Four Phase
$0 < D < 0.25$	$\frac{I_{OUT}}{2} \times \frac{\sqrt{D \times (1-4D)}}{(1-D)}$
$0.25 < D < 0.5$	$\frac{I_{OUT}}{2} \times \frac{\sqrt{(4D-2) \times (1-4D)}}{2 \times (1-D)}$
$0.5 < D < 0.75$	$\frac{I_{OUT}}{2} \times \frac{\sqrt{(4D-2) \times (3-4D)}}{2 \times (1-D)}$
$0.75 < D < 1$	$\frac{I_{OUT}}{2} \times \frac{\sqrt{4D-3}}{\sqrt{1-D}}$

*Approximations



Loop Stability of a Current Mode Boost

- Current mode control modifies the complex conjugate double pole to two separate poles
 - The inductor pole pushes to a higher frequency
- Typically use current mode control due to the Right Half Plane Zero (RHPZ)
 - RHPZ causes sudden decrease in the $1-D$ period due to control loop increasing D for sudden load step
 - Adds additional phase drop of negative 90° phase shift
- Cross over frequency below RHPZ frequency to avoid additional phase shift
- For current mode control, duty cycles approaching 0.5 and beyond require modification to the current sense to avoid subharmonic oscillation

Loop Stability of a Dual Phase Current Mode Boost



- Adjustments to accommodate an interleaved configuration
- Divide down the output capacitor by number of phases
 - C_{out} becomes 195 μF from 390 μF
- Multiply the output capacitor ESR by number of phases ESR
 - ESR becomes 40 $\text{m}\Omega$, from 20 $\text{m}\Omega$
- Multiply R_{out} by number of phases
 - R_{out} becomes 6 ohm from 3 Ω
 - All other elements stay the same

Current Mode Boost Power Stage

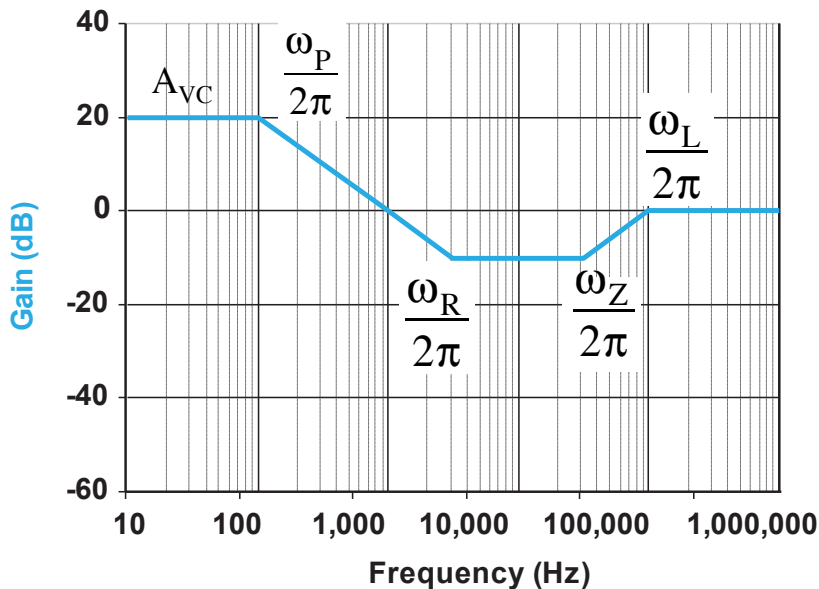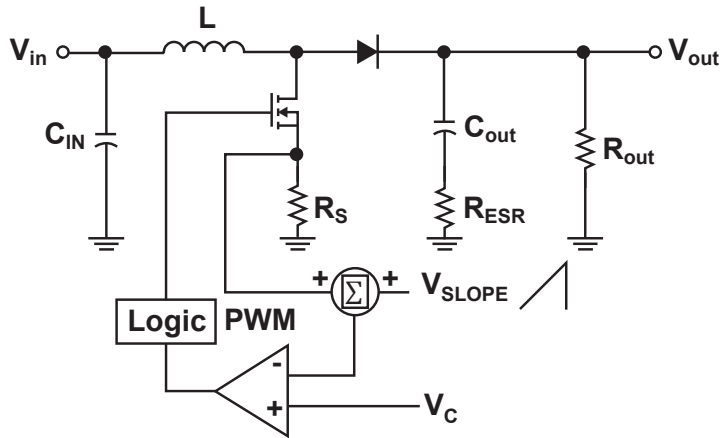

Variable	Equation
$\frac{\hat{V}_{OUT}}{\hat{V}_C}$	$A_{VC} \times \frac{\left(1 - \frac{s}{\omega_R}\right) \times \left(1 + \frac{s}{\omega_Z}\right)}{\left(1 + \frac{s}{\omega_P}\right) \times \left(1 + \frac{s}{\omega_L}\right)}$
R_I	$A_{CS} \times R_S$
A_{VC}	$\approx R_{out} \times n \times \frac{(1-D)}{2 \times R_I}$
ω_P	$\approx \frac{2}{C_{out} \times R_{out}}$
ω_L	$= \frac{K_M \times R_I}{L}$
K_M	$\approx \frac{V_{out}}{V_{SLOPE}}$
ω_Z	$= \frac{1}{C_{out} \times R_{ESR}}$
ω_R	$= \frac{R_{out} \times n \times (1-D)^2}{L}$
V_{SLOPE}	$\frac{(V_{out} - V_{in}) \times R_i}{L \times f_{SW}}$


Type II Error Amplifier

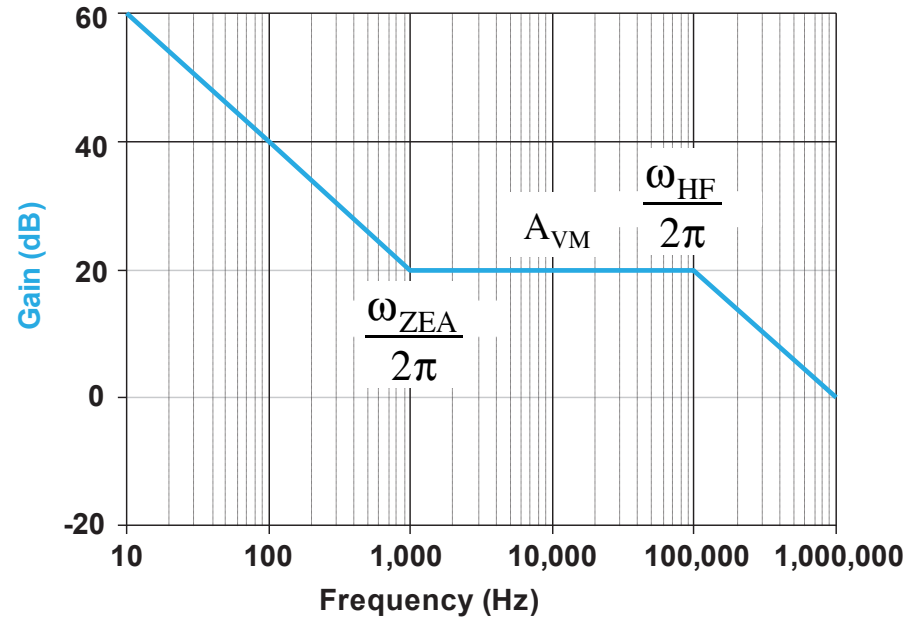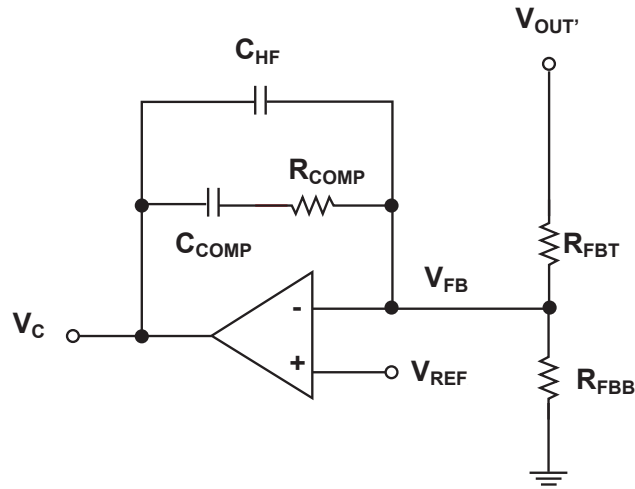

$$\frac{\omega_{ZEA}}{2\pi} = \frac{\omega_C}{2\pi \times 10}$$

$$\frac{\omega_{HF}}{2\pi} = \frac{\omega_R}{2\pi}$$

Type II Error Amplifier

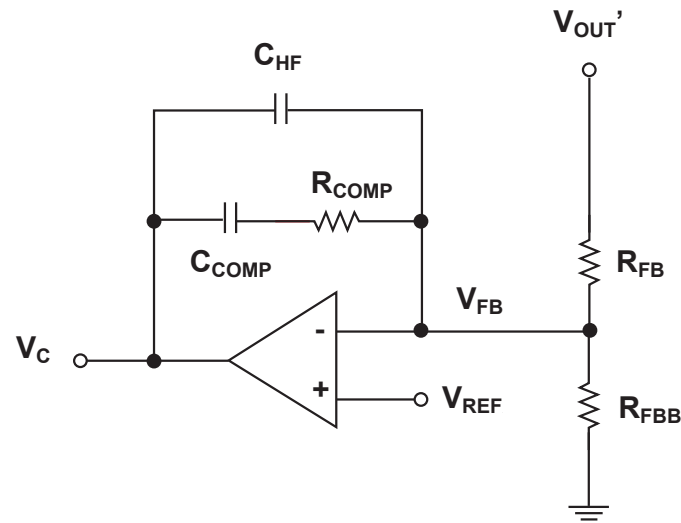


Variable	Single Phase	Two Phase	Comment
R_{FBT}	10 k Ω	10 k Ω	Choose value between 2 k Ω 100 k Ω
D_{MAX}	= 0.625	= 0.625	$= \frac{V_{out} - V_{in_Min}}{V_{out}}$, $V_{in_Min} = 9V$
R_I	= 40 m Ω	= 80 m Ω	$A_{CS} \times R_S$
G_{M_Mod}	= 9.375	= 4.688	$= \frac{1 - D_{max}}{R_I}$

Boost Compensation Approach


Variable	Single Phase	Two Phase	Comment
RHPZ	$\approx 52 \text{ kHz}$	$\approx 21 \text{ kHz}$	$= \frac{R_{\text{out}} \times n \times (1-D)}{L \times 2\pi}$
F_C	$\approx 12.5 \text{ kHz}$	$\approx 5 \text{ kHz}$	$= \frac{\text{RHPZ}}{4}$
ω_C	$\approx 12.5 \text{ kHz} \times 2\pi$	$\approx 5 \text{ kHz} \times 2\pi$	$= \frac{\omega_R}{4}$
A_{VM}	$= 4.4$	$= 1$	$= \frac{\omega_C \times \frac{C_{\text{out}}}{n}}{G_{M_Mod}}$
R_{COMP}	$= 44 \text{ k}\Omega$	$= 10 \text{ k}\Omega$	$= A_{VM} \times R_{FBT}$
C_{COMP}	$\approx 2.8 \text{ nF}$	$\approx 27 \text{ nF}$	$C_{COMP} = \frac{1}{R_{COMP} \times \omega_{ZEA}}$
C_{HF}	$\approx 68 \text{ pF}$	$\approx 720 \text{ pF}$	$C_{HF} = \frac{1}{R_{COMP} \times \omega_{HF}}$

Asymptotic


Power Stage Current Mode Boost

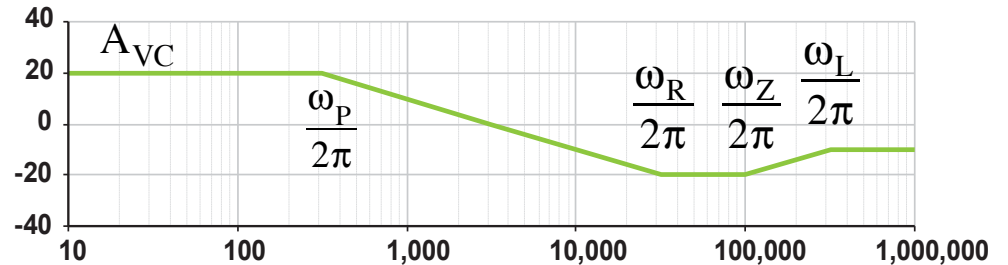

Type II Error Amplifier

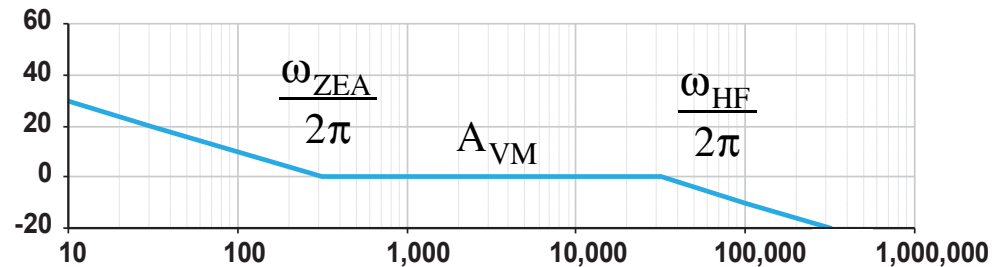


Control Loop

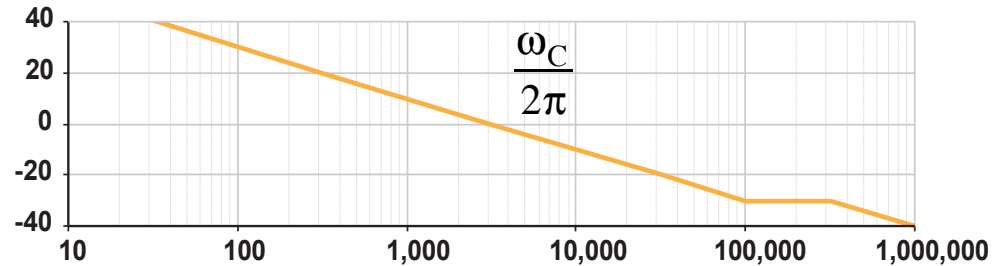

Compensation Results Single Phase


Simulation results

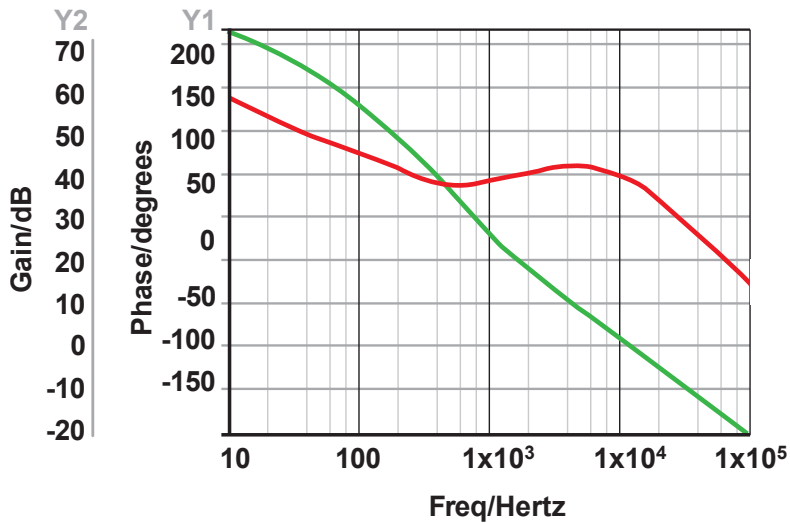- A crossover frequency of ~ 13 k and a PM of ~ 50 degrees



MathCAD results


- F_C of ~ 13 k and a PM of ~ 75 degrees

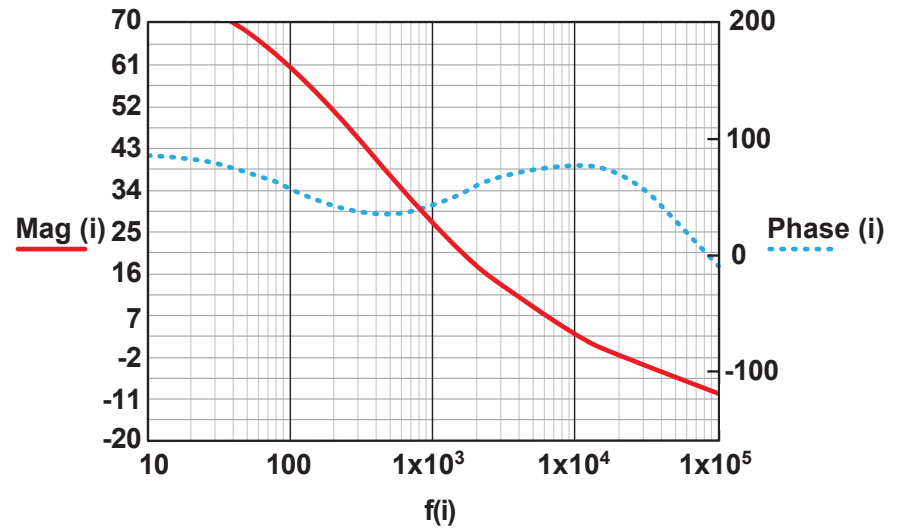

Dual Phase Compensation Results


Simulation results (Simplis)

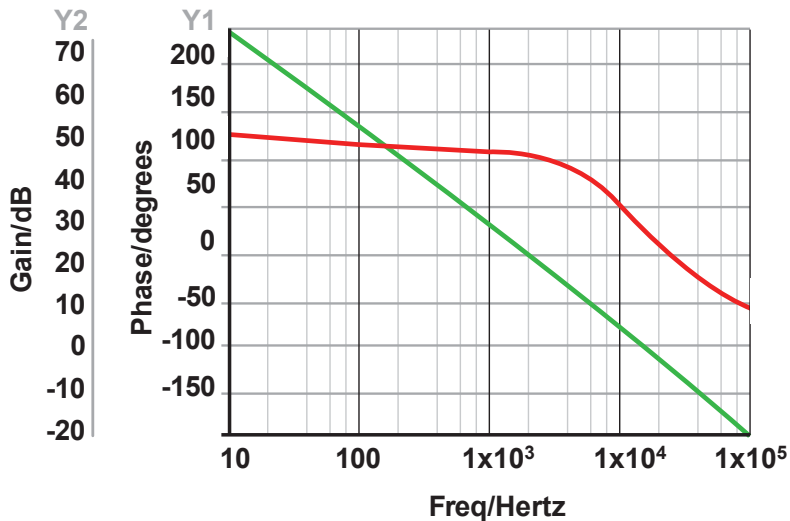- Shows an F_C of ~ 5 kHz and a PM of ~ 56 degrees



Mathcad results

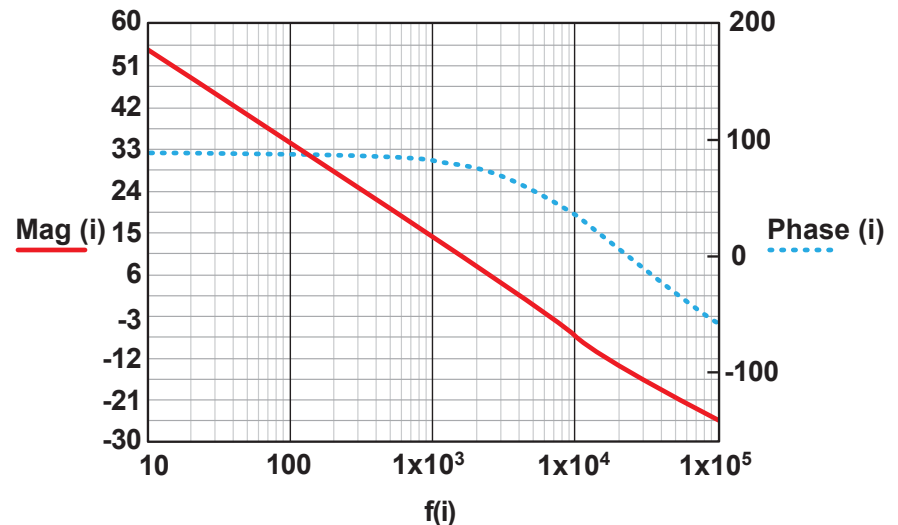- Mathcad result correlate well to simulation showing an F_C of ~ 5 kHz and a PM of ~ 60 degrees



Summary of Results

Parameter	Single Phase	Dual Phase
Per phase switching frequency	250 kHz	125 kHz
Inductance value	3 μ H	15 μ H
I_{sat}	15 A	9 A
Energy $1/2 \times L \times I^2$	337.5 μJ	1.215 mJ
Inductor DCR losses	0.6 W	1.4 W Total
Inductor core losses	2.6 W	0.018 W Total
R_{sense}	4 m Ω	8 m Ω
R_{sense} losses	0.9 W	0.8 W Total
Boost FET conduction losses	0.3 W	0.16 W Total
Boost FET transitional losses	0.525 W	0.25 W Total
FET Q_{OSS} losses	0.2 W	0.2 W Total
Q_{RR} losses	0.35 W	0.35 W
Synchronous FET conduction losses	0.44 W	0.22 W
I_C losses	0.182 W	0.336 W
Total losses	6.097 W	3.724 W
Calculated efficiency	~97%	~98%
C_{in} RMS ripple current rating	2.1 A	0.9 A
C_{out} RMS ripple current rating	6.7 A	2.5 A
C_{in}	22 μ F	22 μ F
C_{out}	780 μ F	390 μ F
F_C	12.5 kHz	5 kHz




Summary of Results

Component Count Comparison

	Part Number	Single Phase	Part Number	Dual Phase
MOSFETs	CSD18531Q5A	2	CSD18531Q5A	4
C_{in}	25 V Ceramic	1	25 V Ceramic	1
C_{out}	PCV1E391MCL2GS	2	PCV1E391MCL2GS	1
Inductor	XAL1580-302	1	SER1390-153	2
IC	LM5122	1	LM5122	2
R_{sense}	2 W Current Sense	1	2 W Current Sense	2
Total		8		12





Bench Test Results: Single Phase (PMP9385)

Efficiency and Thermals Comparison

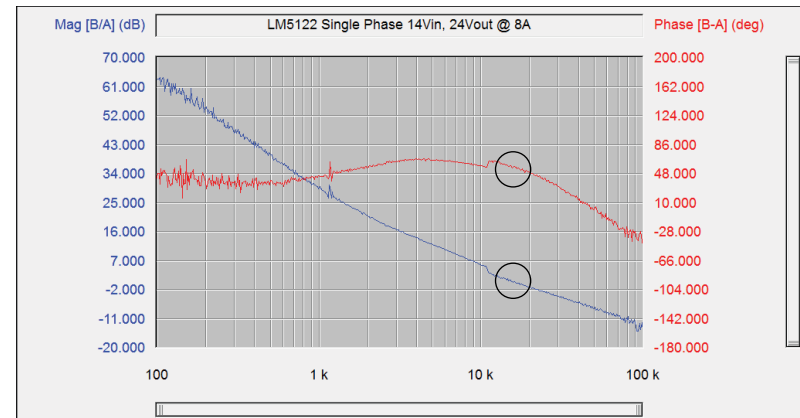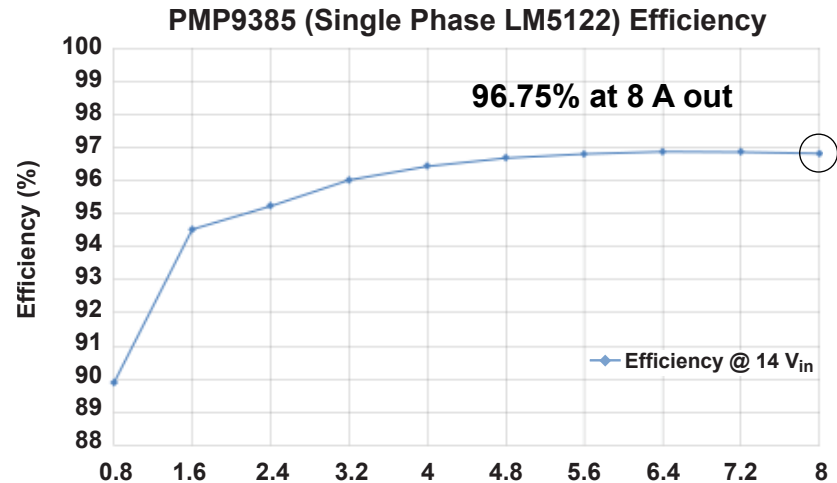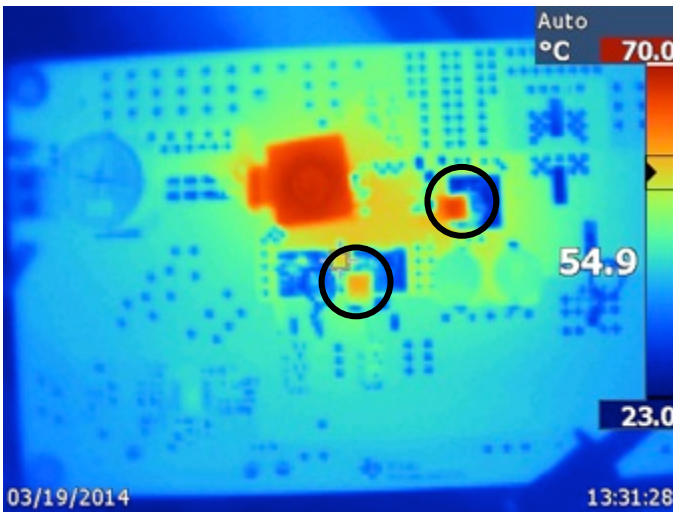

Bench Test Results: Dual Phase (PMP9386)

Efficiency and Thermals Comparison

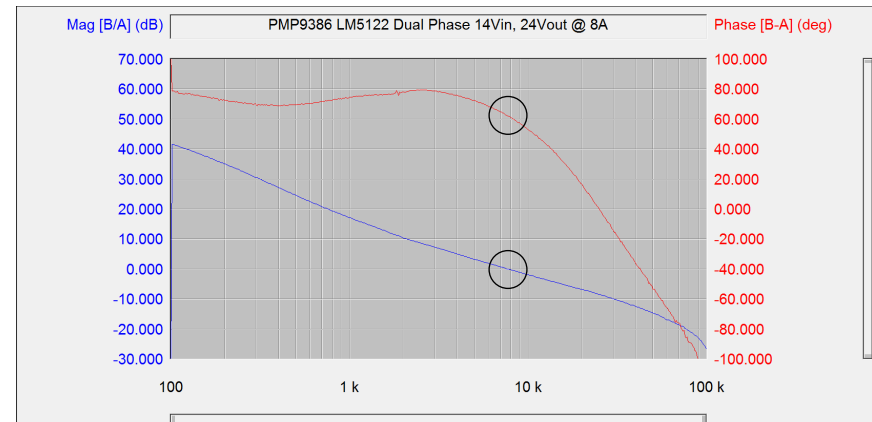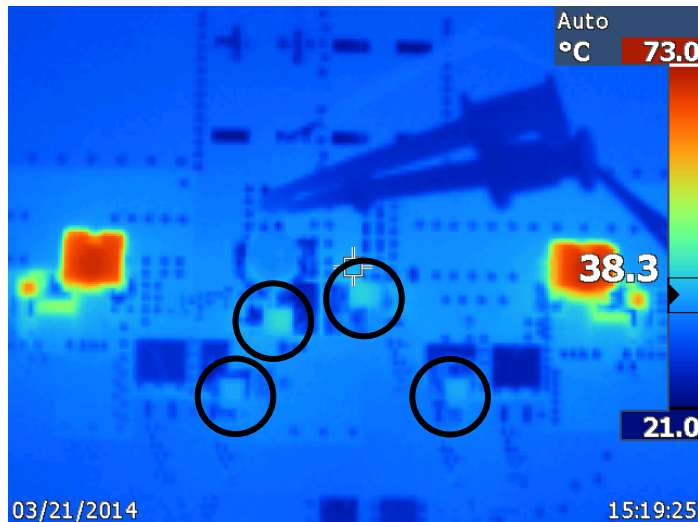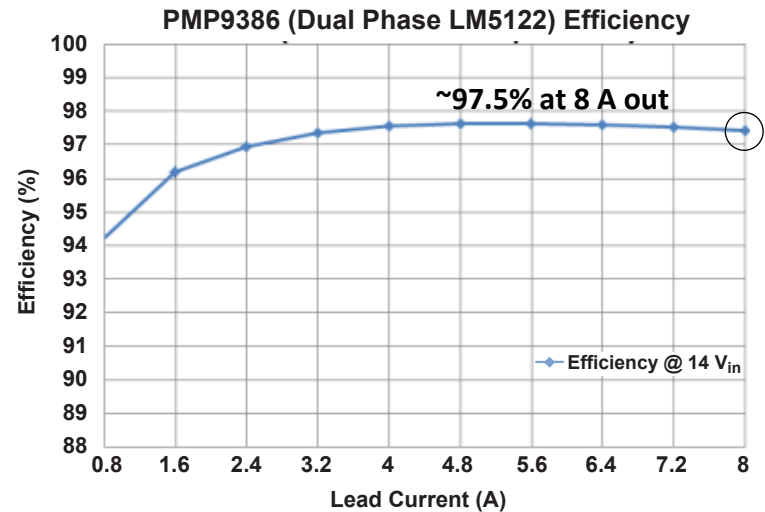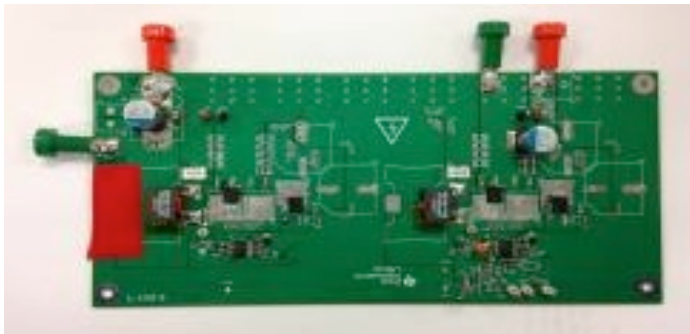

Conclusion

- Using equations and step-by-step approach provided herein enables designer to adjust design for optimizing efficiency or size
- Both size, cost and performance can be modified by using multiphase boost approach
- Thermal performance improved using two phase approach
 - Thermal stress on FETs significantly reduced with multiphase approach
- For single phase boost
 - Increasing switching frequency in an attempt to reduce size will result in exceeding FET thermal limits
- For two phase boost
 - Increasing switching frequency is feasible without thermal stress on FETs
 - Significant reduction in size can be further gained

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com