

Control Challenges for Low Power AC/DC Converters

Brian King and Rich Valley

Content Outline

1. The Low Power Flyback Converter

- Characteristics
- Key performance
- Typical operating and control modes

2. PSR Regulation Methods

- Constant Voltage (CV) – regulating V_{OUT}
- Constant Current (CC) – regulating I_{OUT}

3. Low Standby Power

- Lowering consumption
- Achieving low input power

4. Results and Comparison (10 W at 5 V)

- DCM and variable frequency – primary side voltage and current control
- DCM and fixed frequency – optical coupler feedback
- DCM, variable frequency – optical coupler feedback, primary side current control

The Low Power AC/DC Flyback

Key Points

1. Power inductor


- AKA, flyback transformer
- 3rd “bootstrap” winding

2. PWM Control

- Peak current control
- Switching frequency control
- Low pin count
- Requires start-up circuit

3. Feedback

- TL431 network
- Optical Coupler

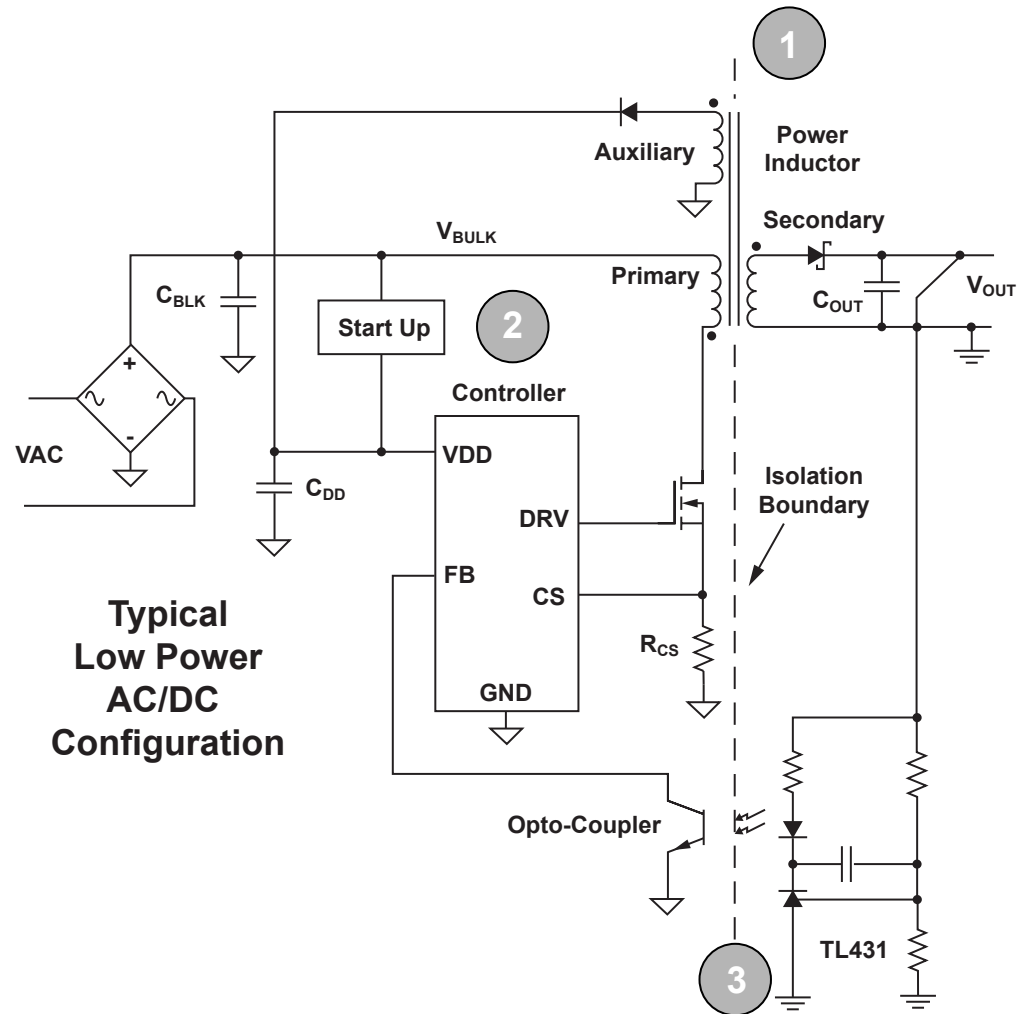



The Low Power AC/DC Power Supplies

3-35 Watts, 3 V to 20 V

- Universal input, 85-265 VRMS
- AC/DC adapters and chargers
- Set top boxes
- E-meters
- Auxiliary supplies – DTV, servers...

Key Parameters

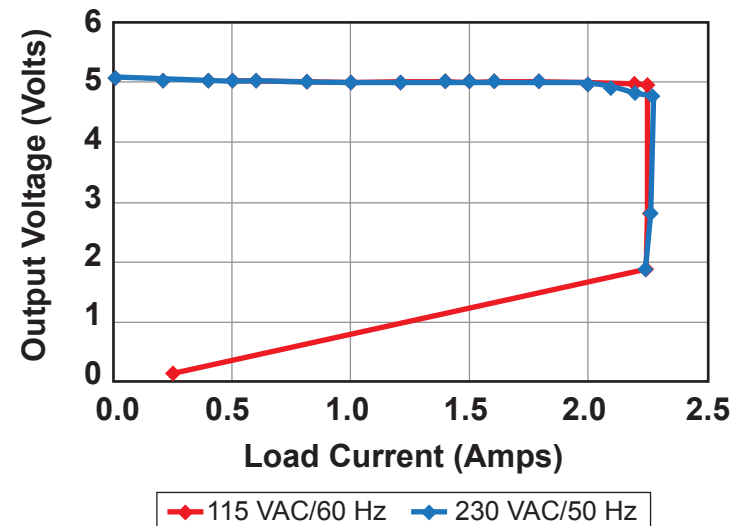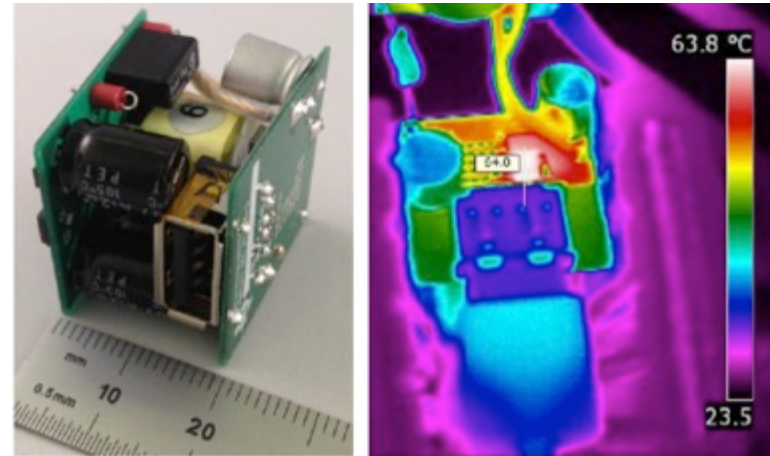
- Size and cost
- Voltage and current control
- Efficiency
- Standby power



Performance – Efficiency

Efficiency standards for External Power Supplies (EPS)

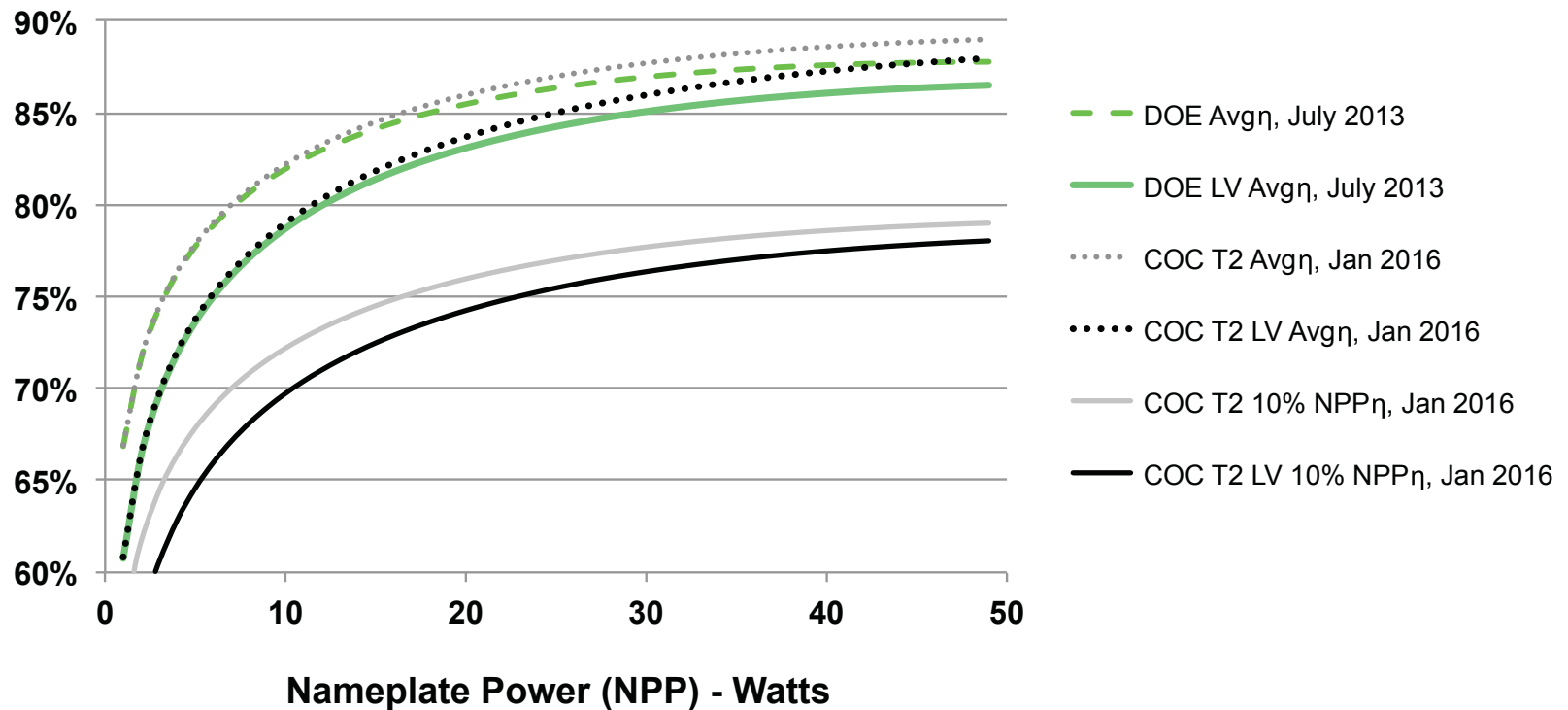- Department of Energy, DOE
- European Commission Code of Conduct, COC



Performance – Standby Power

Efficiency standards for External Power Supplies (EPS)

- European Commission, Tier 2 – January 2016 ————— 75 mW
- Department of Energy – July 2013 ————— 100 mW
- 5 Star Charger ————— 30 mW

No-load consumption score chart
Five stars = most energy efficient




★★★★★	$\leq 0.03\text{W}$
★★★★	$> 0.03\text{W}$ to 0.15W
★★★	$> 0.15\text{W}$ to 0.25W
★★	$> 0.25\text{W}$ to 0.35W
★	$> 0.35\text{W}$ to 0.5W
No Stars	$> 0.5\text{W}$

- OEM specifications at 10 mW and asking for 5 mW



Discontinuous Current Mode (DCM)

- Single switch control
- T_{ON} :
 - Switch on-time
 - Energy taken from V_{IN} and stored in primary
 - Core is “magnetized”
- T_{DM} :
 - Switch is off
 - Stored energy is fully transferred to V_{OUT}
 - Core is “demagnetized”
- T_{DIS} :
 - Discontinuous time
 - Currents are zero
 - $T_{DIS} = 0 \rightarrow$ transition mode


Basic Flyback Topology

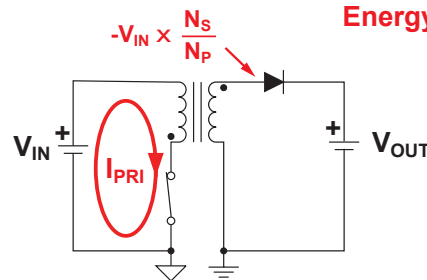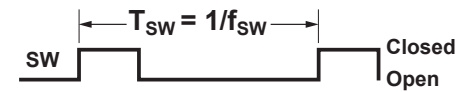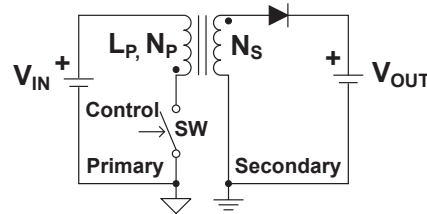

Energy Storage

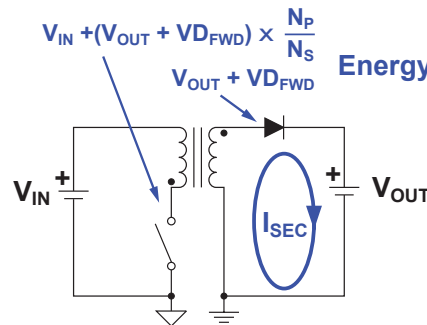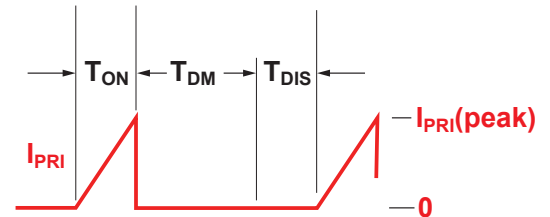

Energy Transfer

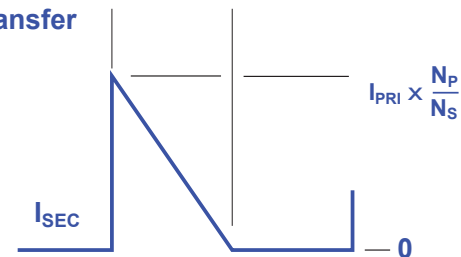

Power Control with the DCM Flyback

- Each switching cycle
 - A controlled energy is taken from the input
 - This energy (minus some losses) is delivered to the load
 - The system is at the same condition at the beginning of every cycle


$$1) CE_{ST} = \frac{1}{2} L_P \times I_{PRI(\text{peak})}^2 \text{ (transformer energy stored each cycle)}$$

$$2) P_{IN} \cong f_{sw} \times CE_{ST} \text{ (converter input power)}$$

$$3) \eta = \frac{P_{OUT}}{P_{IN}} \text{ (overall converter efficiency)}$$

- Power is modulated by changing:
 - Cycles/second – frequency modulation
 - Energy/cycle – amplitude modulation


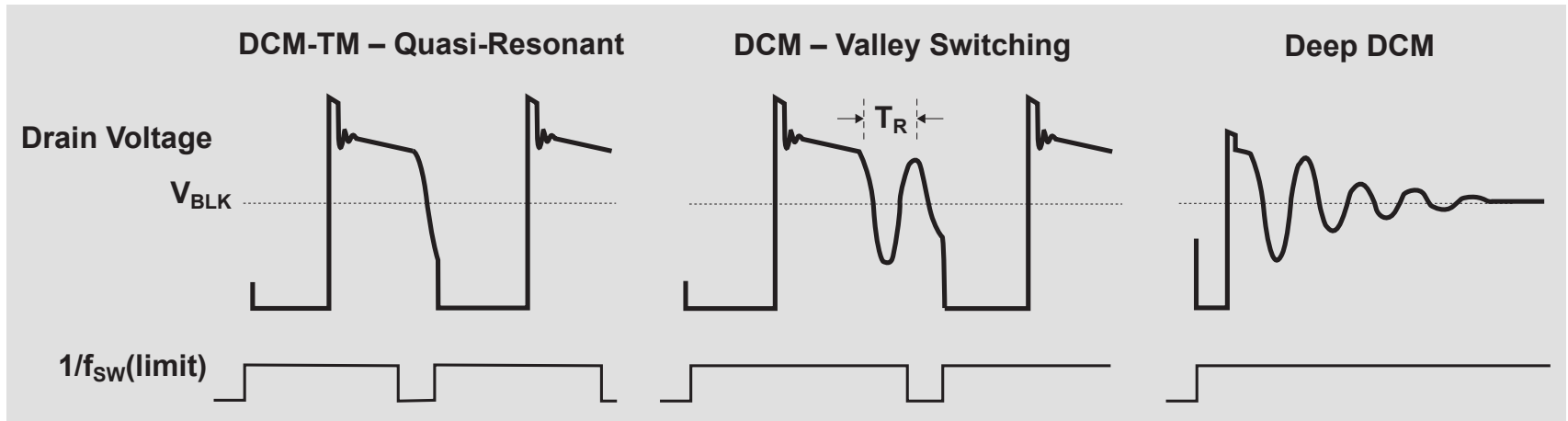
DCM or TM(Transition Mode) with Valley Switching



- Waiting for a zero crossing prevents continuous conduction mode (CCM)
- Switching on a valley reduces dissipation and EMI
- $1/f_{sw}(\text{limit})$ sets a minimum period



DCM, Fixed Frequency Control

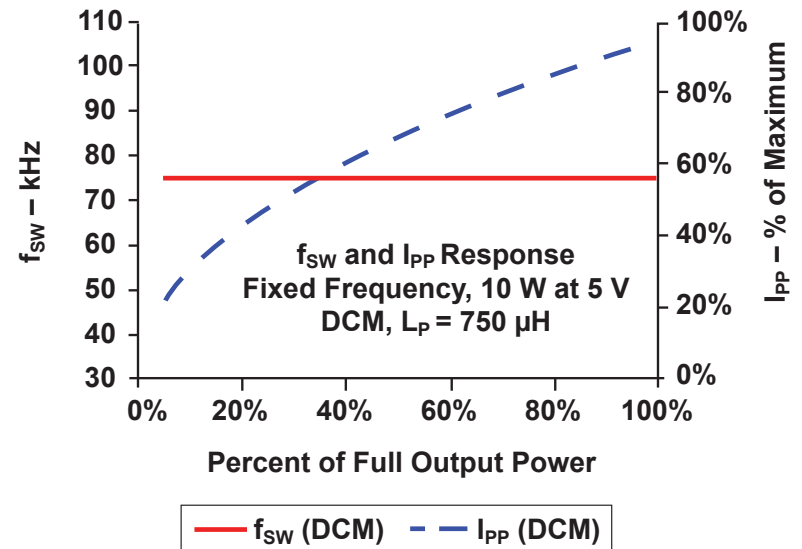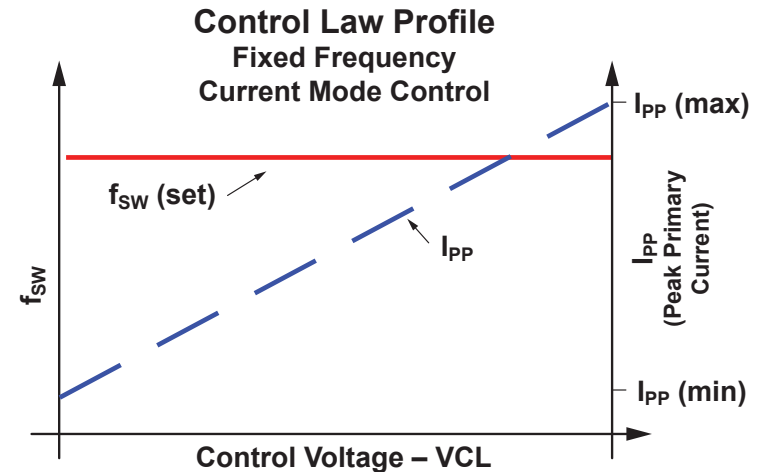- Frequency is constant
 - Peak current is modulated
- + Controlled switching frequency
- Lower efficiency
 - High stand-by power
 - Limited dynamic range





DCM, Variable Frequency Control

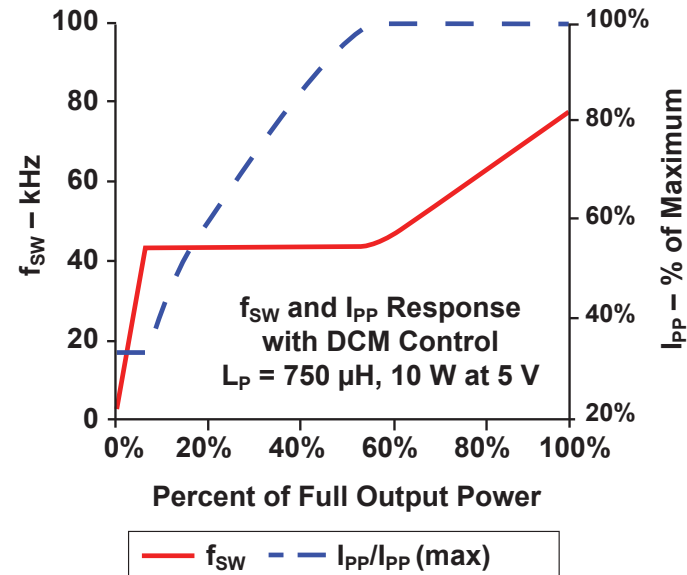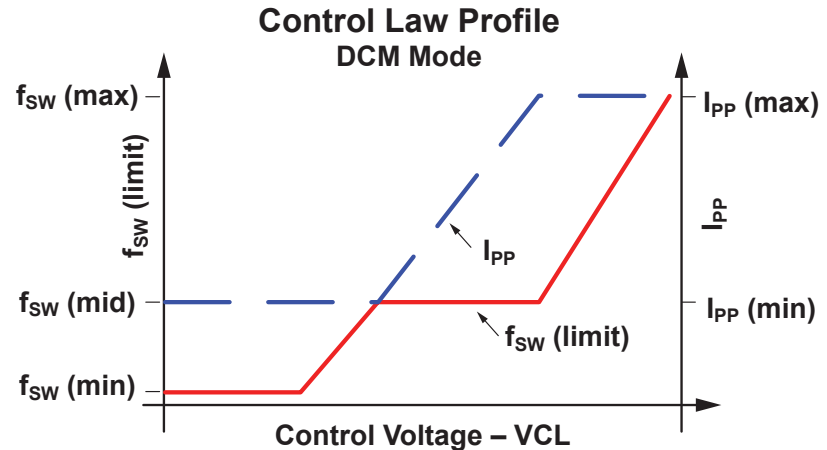- Peak current is modulated
 - Frequency is modulated
 - Approaches TM at low line full load
-
- + Smallest inductance
 - + Good efficiency
 - + Best current control
 - Wide frequency range



TM/DCM, Variable Frequency Control

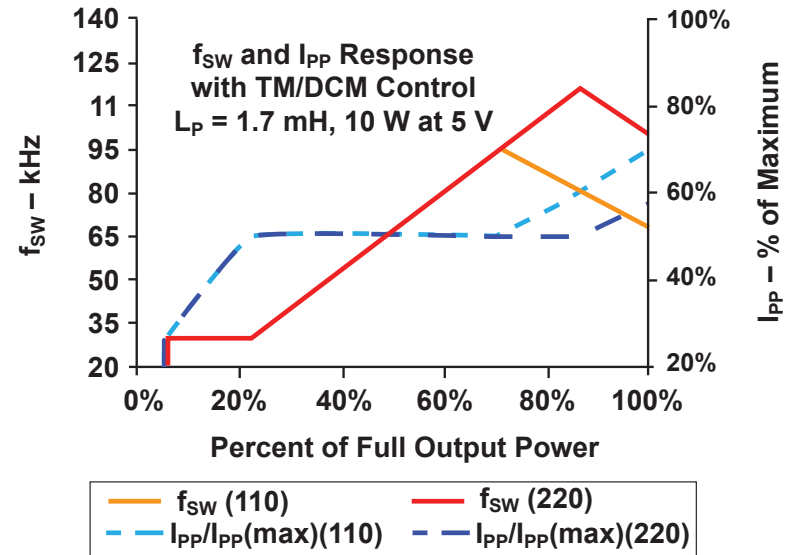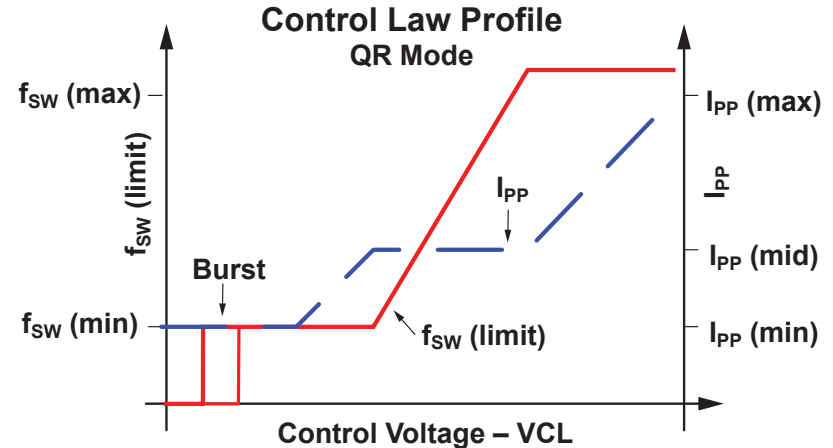- Peak current is modulated
 - Frequency is modulated
 - Operates TM at full load
- + Better full load efficiency
- Larger primary inductance
 - Wide frequency range
 - Reduced input voltage rejection




Primary Side Regulation (PSR)

Constant Voltage (CV) and
Constant Current (CC) Methods


Primary Side Regulation (PSR)

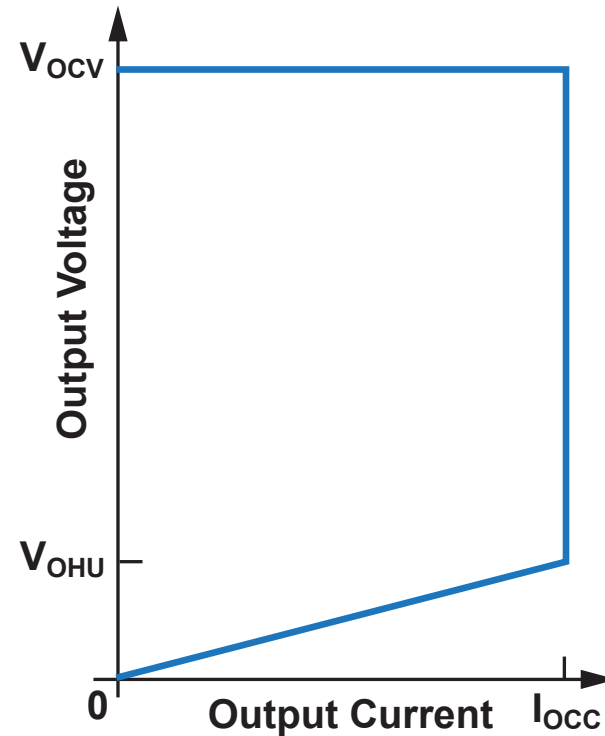- Controlling output voltage and current with no direct sensing
- Constant Voltage (CV) for $I_O = 0 \text{ A}$ to I_{OCC}
- Constant Current (CC) for $V_O = V_{OHU}$ to V_{OCV}
- The output hold up voltage, V_{OHU} , depends on the primary controller supply dropout




PSR – Component Reduction

From This

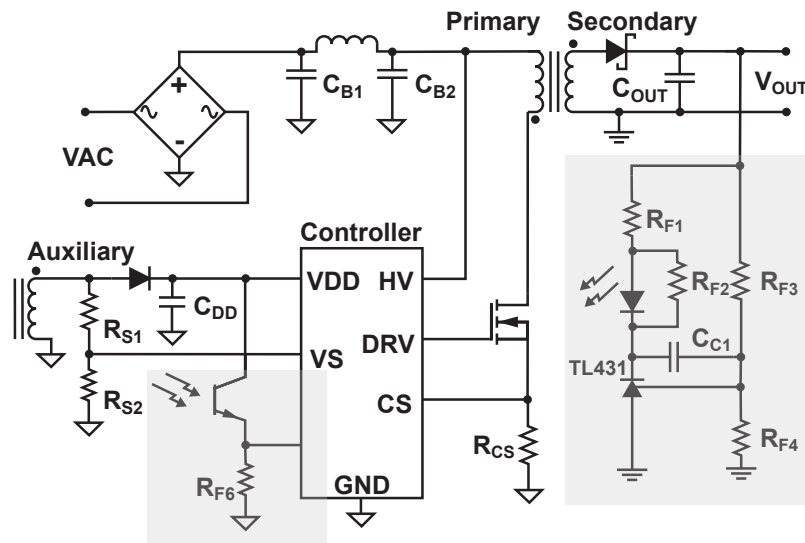

To This

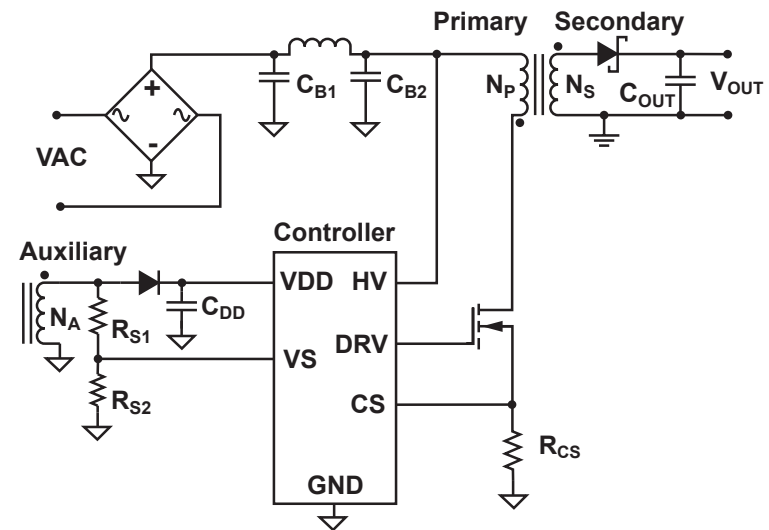



- Opto-coupler and TL431 circuits are eliminated
- Less parts = lower cost, smaller supply, higher reliability
- Less design, also less design flexibility

PSR – Feedback Concept

1. $V_{OUT} + V_D$, scaled by a turns ratio, at Aux during T_{DM}
2. Use for voltage feedback (at VS input)

But.....

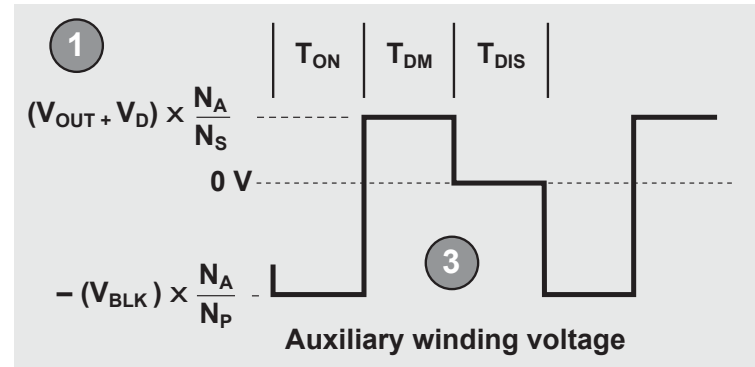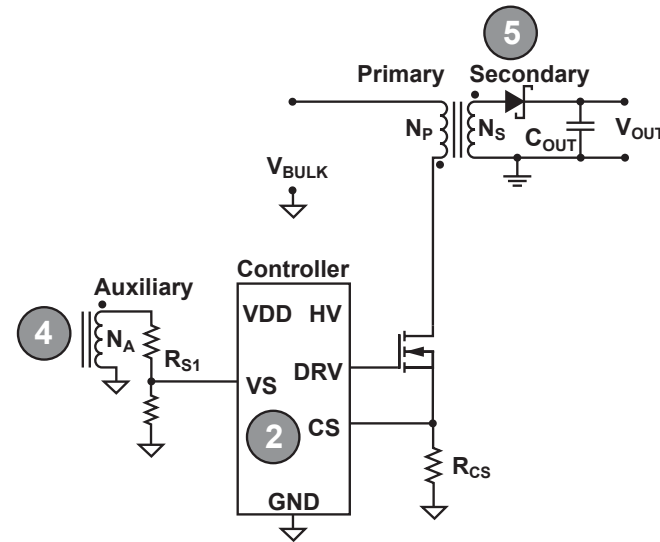3. Signal is not continuous
4. N_A / N_S must be controlled
5. V_D (output diode voltage) is a source of error
6. Nothing is this simple



T_{ON} = the switch ON time

T_{DM} = the transformer demagnetization time

T_{DIS} = the discontinuous current time

PSR – Feedback Concept

Auxiliary winding waveform:

Leakage inductance

- Reset spike
- Rings with C_{SWN}



1. ESR

- $I_{SEC} \times R_{ESR}$ slope

2. C_{SWN} rings with L_P


Best regulation if sampled when I_{SEC} goes to zero

→ “VS sample”

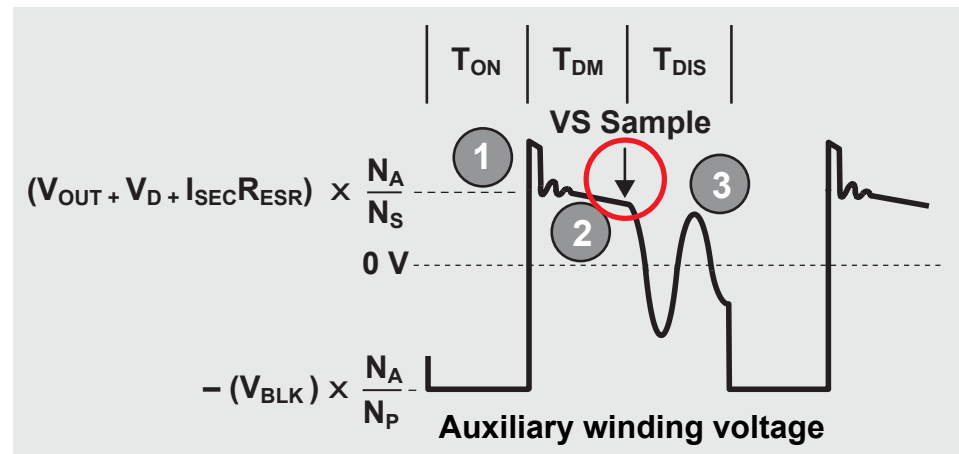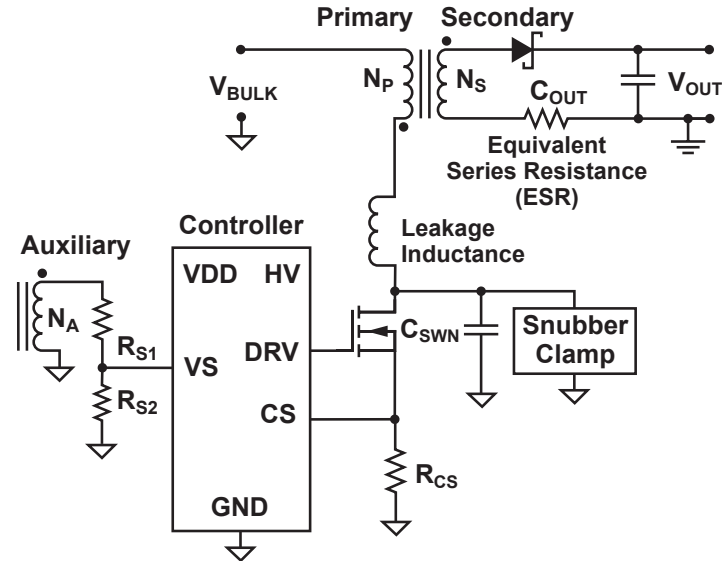

PSR – Voltage Loop

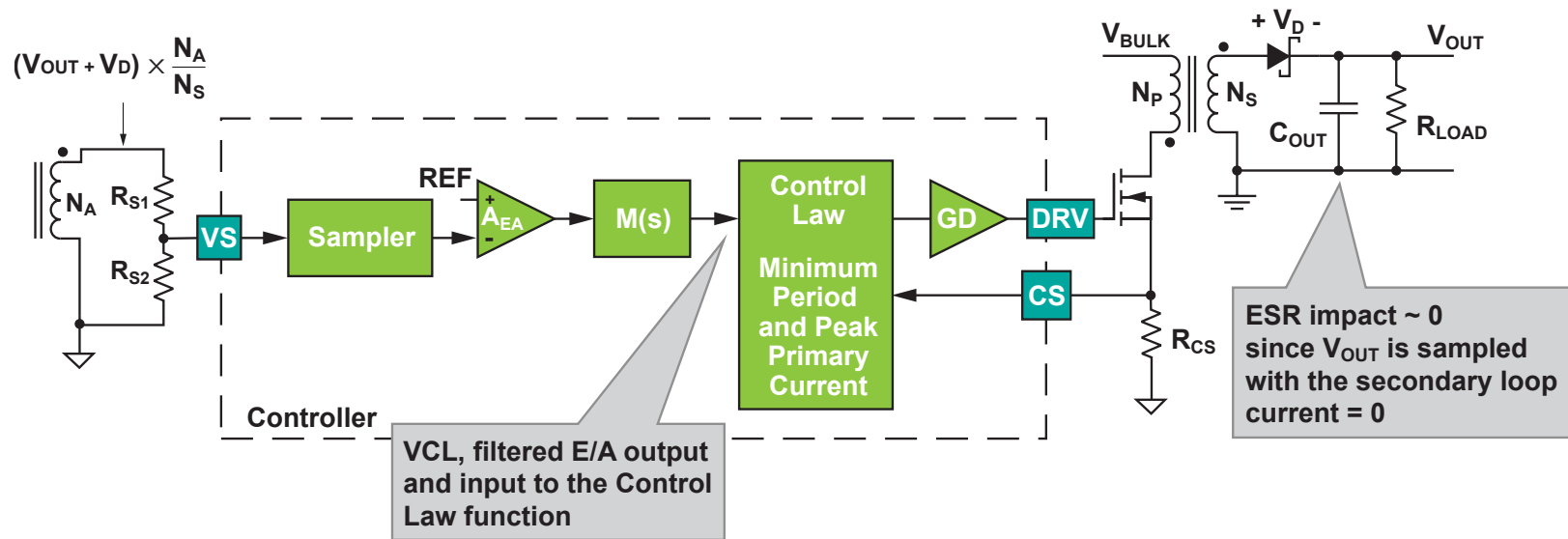
- Samples output at f_{SW} rate
- f_{SW} has wide range, $>100:1$, for low stand-by power
- Compensation ($M(s)$) done internally



PSR – Transient Response Problem

Poor Transient Response from Zero Load

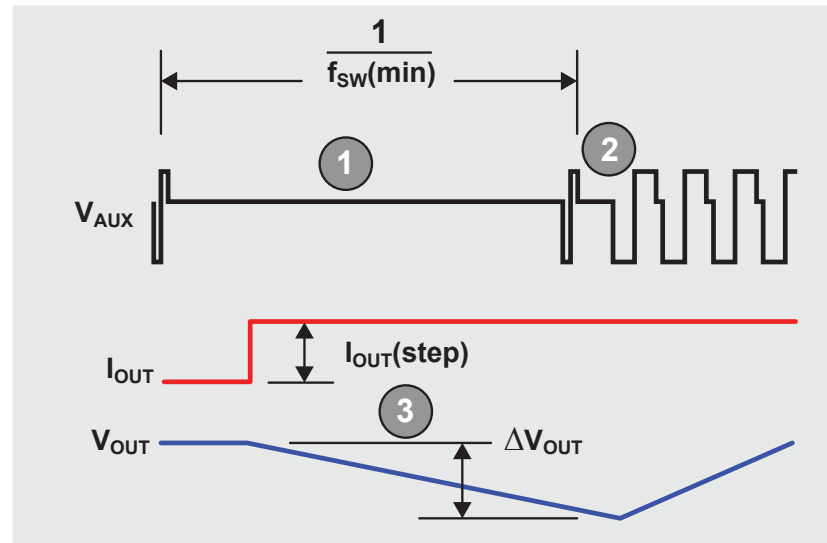1. Low switching frequencies
2. Feedback is only available during a switching event
3. Poor transient performance, or a very large output capacitor



As Bad as:

$$\Delta V_{OUT} = \frac{I_{OUT(step)}}{C_{OUT} \times f_{sw(min)}}$$

PSR Voltage Error Sources


- Reference, Error Amplifier, Resistors
- Rectifier Diode Drop
 - Actually regulating $V_{OUT} + V_D$
 - Diode-to-diode V_D at a fixed low current is consistent for a given diode selection
 - Diode temperature variation will impact V_{OUT} if not compensated for
- Transformer
 - Reasonable manufacturing gives good turn control
 - Impact of leakage inductance is small
- Winding Voltage Sampling Errors (generally seen at light loads)
 - Auxiliary diode, snubber diode, snubber noise corrupting signal
 - Auxiliary to secondary cross-regulation at light loads
 - VS filtering
- Generally +/- 5% is readily achievable across line and load

Constant Current Control – Concept

$$1) I_O = I_{SEC}(Avg) = \frac{I_{SEC}(peak)}{2} \times \frac{T_{DM}}{T_{SW}}$$

$$2) I_{SEC}(peak) = I_{PRI}(peak) \times \frac{N_P}{N_S}$$
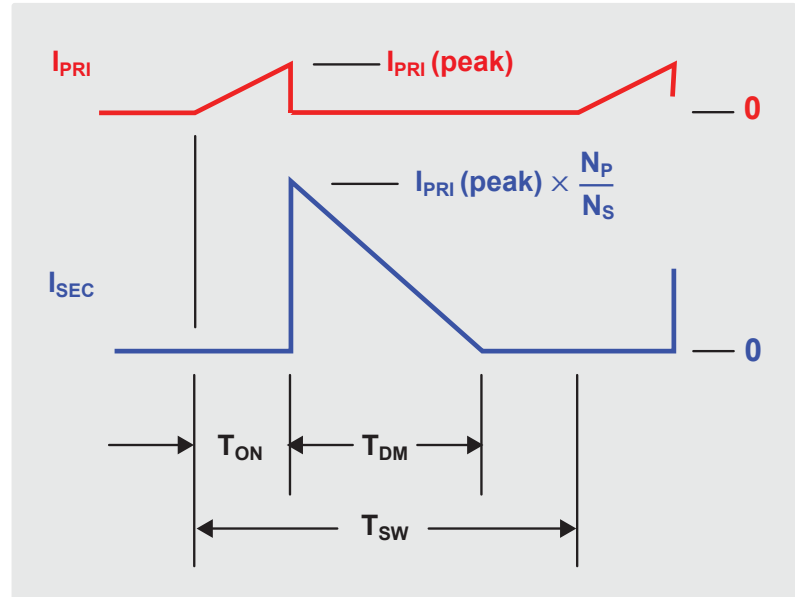
$$\text{Therefore: } 3) I_O = \frac{I_{PRI}(peak)}{2} \times \frac{N_P}{N_S} \times \frac{T_{DM}}{T_{SW}}$$



- Controlling the peak primary current and the demagnetization duty-cycle (T_{DM} / T_{SW}) will regulate the output current accurately (~+/-5% achievable)

Standby Power (P_{SB})

Power consumed with zero external load,
a very common state for power supplies

P_{SB} Components

$$P_{SB} = f_{SW}(sb) \times CE_{IN}(min) + P_{STRT} + P_{LKG}$$

Where:

$f_{SW}(sb)$ = converter switching frequency during stand-by


$CE_{IN}(min)$ = converter minimum input cycle energy

P_{STRT} = Start-up power

P_{LKG} = \sum Capacitor and junction leakage losses


- Generally $f_{SW} \times CE_{IN}$ dominates
 - Encompasses output preload and primary bias power
- P_{STRT} can be significant at low target P_{SB}

P_{SB} – Start-Up

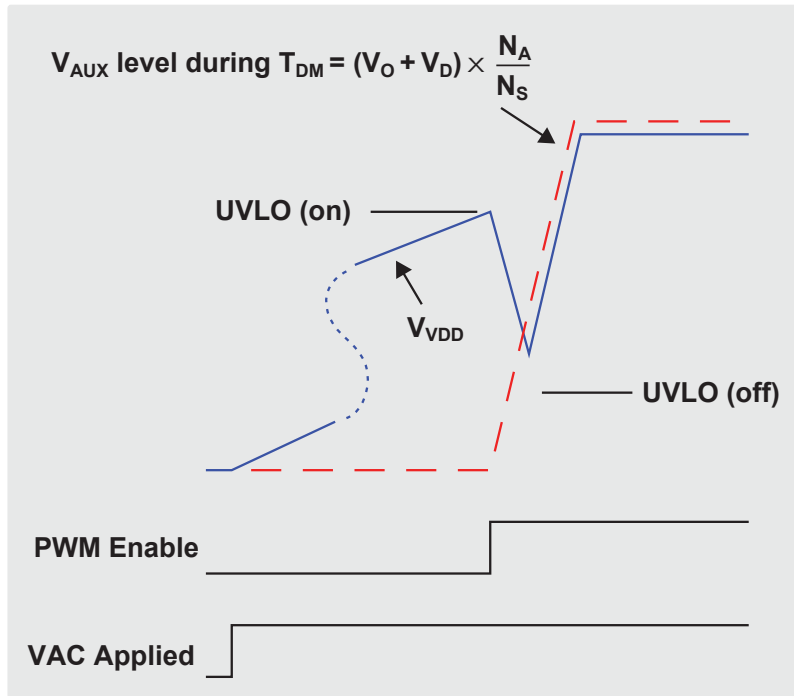


Resistive Start-Up:

7-300 mW to P_{SB}

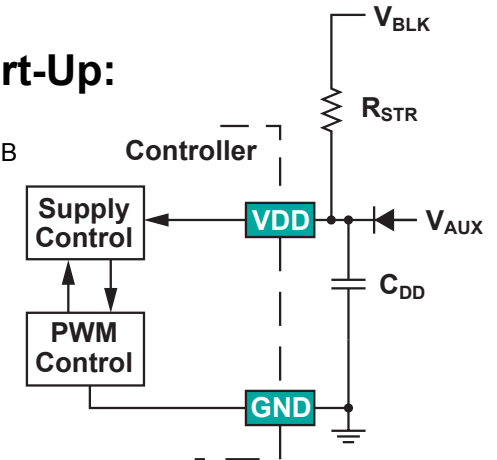


Active Start-Up:

No P_{SB} penalty

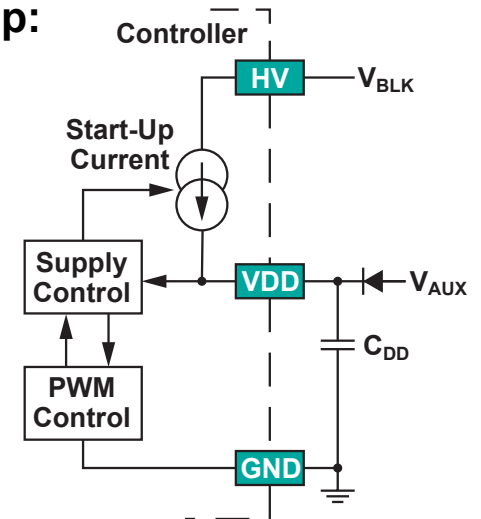

P_{SB} Control Law Must Haves

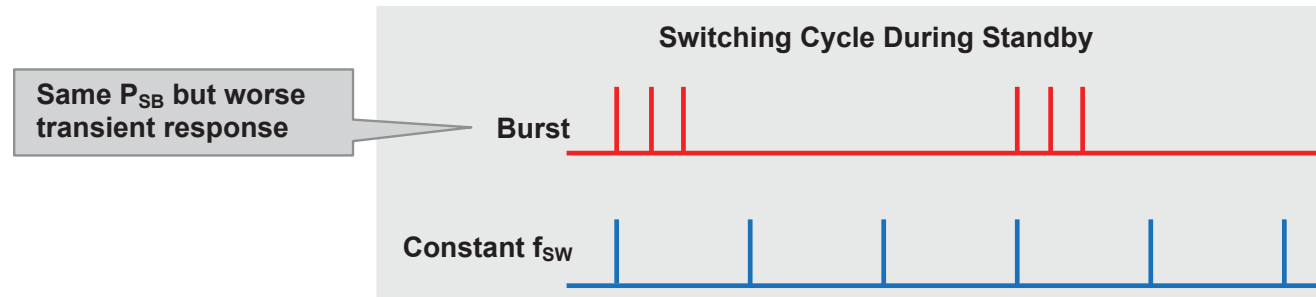

- Low input energy / cycle
- Low switching frequency
- Constant time / cycle
 - Burst mode versus constant $f_{sw}(sb)$
 - Same average cycles / second – worse transient response



P_{SB} and $CE_{IN}(\min)$

- The minimum cycle energy is dependent on the AM range and $f_{SW}(\max)$

$$CE_{IN}(\min) = \frac{P_O(\max)}{\eta_T \times f_{SW}(@P\max)} \left(\frac{1}{K_{AM}} \right)^2 \quad \text{where: } K_{AM} = \frac{I_{PRI}(\text{peak}, @P\max)}{I_{PRI}(\text{peak}, \min)}$$

- The maximum AM range, K_{AM} , will typically be limited to 3-5
- This expression does not take into account the impact of the switch-node capacitance
- η_T is an efficiency estimate ignoring capacitive and bias loss

P_{SB} – Switch Node Capacitance Impact

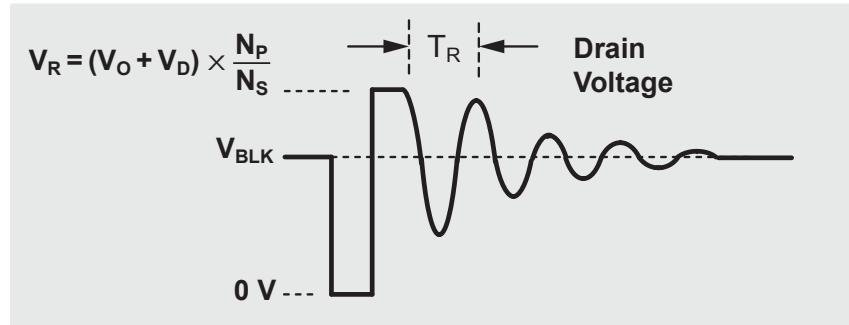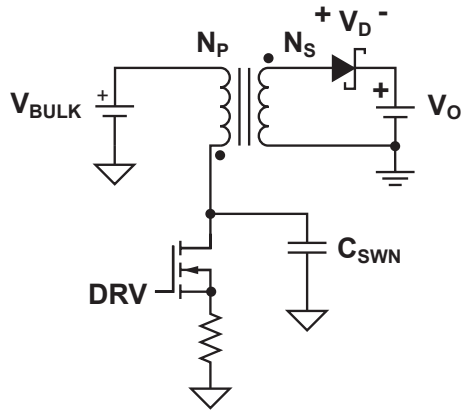

- Delta input cycle energy

$$\Delta CE_{IN}(\text{cap, total}) = C_{SWN} \times V_{BLK}^2$$

- A portion of this is dissipated in the switch and tank,

$$\Delta CE_{IN}(\text{cap, dissipated}) = \frac{1}{2} \times C_{SWN} \times (V_{BLK}^2 + V_R^2)$$

- A portion goes into the transformer \rightarrow output,

$$\Delta CE_{IN}(\text{cap, out}) = \frac{1}{2} \times C_{SWN} \times (V_{BLK}^2 - V_R^2)$$

P_{SB} – Switch Node Capacitance Impact

For the example to the right ignoring the effect of C_{SWN} :

$$CE_{IN}(\text{min}) = 7.81 \mu\text{J}$$

$$CE_{OUT}(\text{min}) = \eta_T \times CE_{IN}(\text{min}) = 6.25 \mu\text{J}$$

Incremental energy due to C_{SWN} :

$$\Delta CE_{IN}(\text{cap, total}) = 9.33 \mu\text{J}$$

$$\Delta CE_{IN}(\text{cap, dissipated}) = 4.89 \mu\text{J}$$

$$\Delta CE_{IN}(\text{cap, out}) = 4.44 \mu\text{J}$$

$$\Delta CE_{OUT}(\text{cap, out}) \cong \eta_T \times \Delta CE_{IN}(\text{cap, out}) = 3.55 \mu\text{J}$$

Total minimum energy w/ C_{SWN} :

$$CE_{IN}(\text{min, total}) = 7.81 \mu\text{J} + 9.33 \mu\text{J} = 17.14 \mu\text{J}$$

$$CE_{OUT}(\text{min, total}) = 6.25 \mu\text{J} + 3.55 \mu\text{J} = 9.80 \mu\text{J}$$

Example Power Supply Parameters

P_O (max)	10 W
f_{SW} (max)	100 kHz
V_{BLK} (max)	365 V
V_R (nom)	80 V
K_{AM}	4
C_{SWN}	70 pF
η_T^*	80%

* Efficiency estimate ignoring capacitive and bias loss

← Limits very light load efficiency and dictates a minimum load

P_{SB} – Minimum Load Requirements


- The converter has a minimum load it will deliver that is equal to:

$$P_o(\text{sb, total}) > f_{SW}(\text{min}) \times \left(\frac{P_o(@P \text{ max})}{f_{SW}(@P \text{ max})} \left(\frac{1}{K_{AM}} \right)^2 + \frac{\eta_T \times C_{SWN} \times (V_{BLK}^2 - V_R)^2}{2} \right)$$


- Bias power plus a preload will adjust $f_{SW}(\text{sb})$ to approach $f_{SW}(\text{min})$, or exceed for improved transient response
- If the preload is not adequate then regulation will be lost with V_o rising

P_{SB} – Versus Transient Response

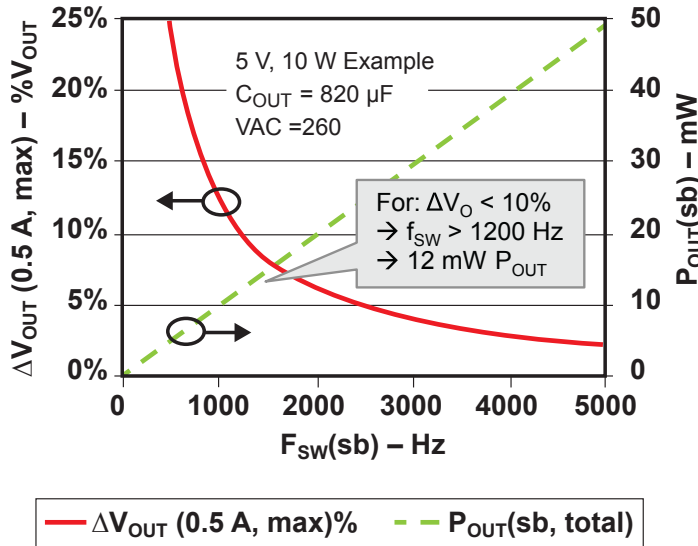$P_{OUT}(sb)$ and Transient Delta Versus $f_{SW}(sb)$



$P_{IN}(sb)$ and $f_{SW}(sb)$ Versus VAC

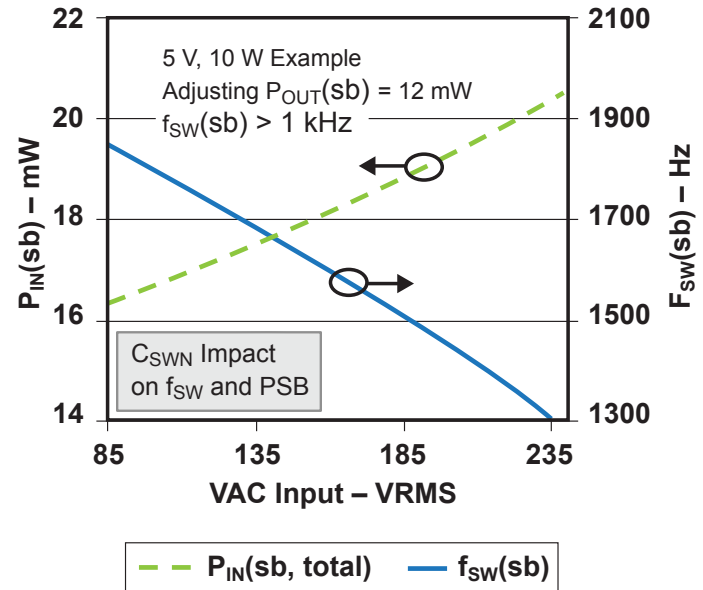

$$P_{IN}(sb, \text{ total}) > f_{SW}(sb) \times \left(\frac{P_O(\text{max})}{\eta_T \times f_{SW}(@P_{\text{max}})} \left(\frac{1}{K_{AM}} \right)^2 + C_{SWN} \times 2 VAC_{RMS}^2 \right)$$

Low Power Flyback Control Recap

- Discontinuous operation with variable frequency optimizes efficiency across load
- Primary side regulation can provide good V and I regulation but transient response can suffer
- Standby power benefits from:
 - Low switching frequencies
 - Low bias and start-up overhead
 - Low switch-node capacitance

Results and Comparison

How do different controllers affect the performance of a typical power supply?

AC/DC 5 V / 10 W Adaptor

General Specifications:

- Universal AC input : 85 V to 265 V, 50/60 Hz
- 5 V output; 2 A max output current


Control Methodologies Evaluated:

- DCM, fixed-frequency, control with opto feedback (DCM/FF/Opto)
- DCM with valley switching and PSR (DCM/VS/PSR)
- DCM with valley switching and opto feedback (DCM/VS/Opto)

Controlled Parameters:


- All designs operate at ~100 kHz at maximum load
- Same transformer, FET, diode used on all designs

DCM/FF/Opto Example

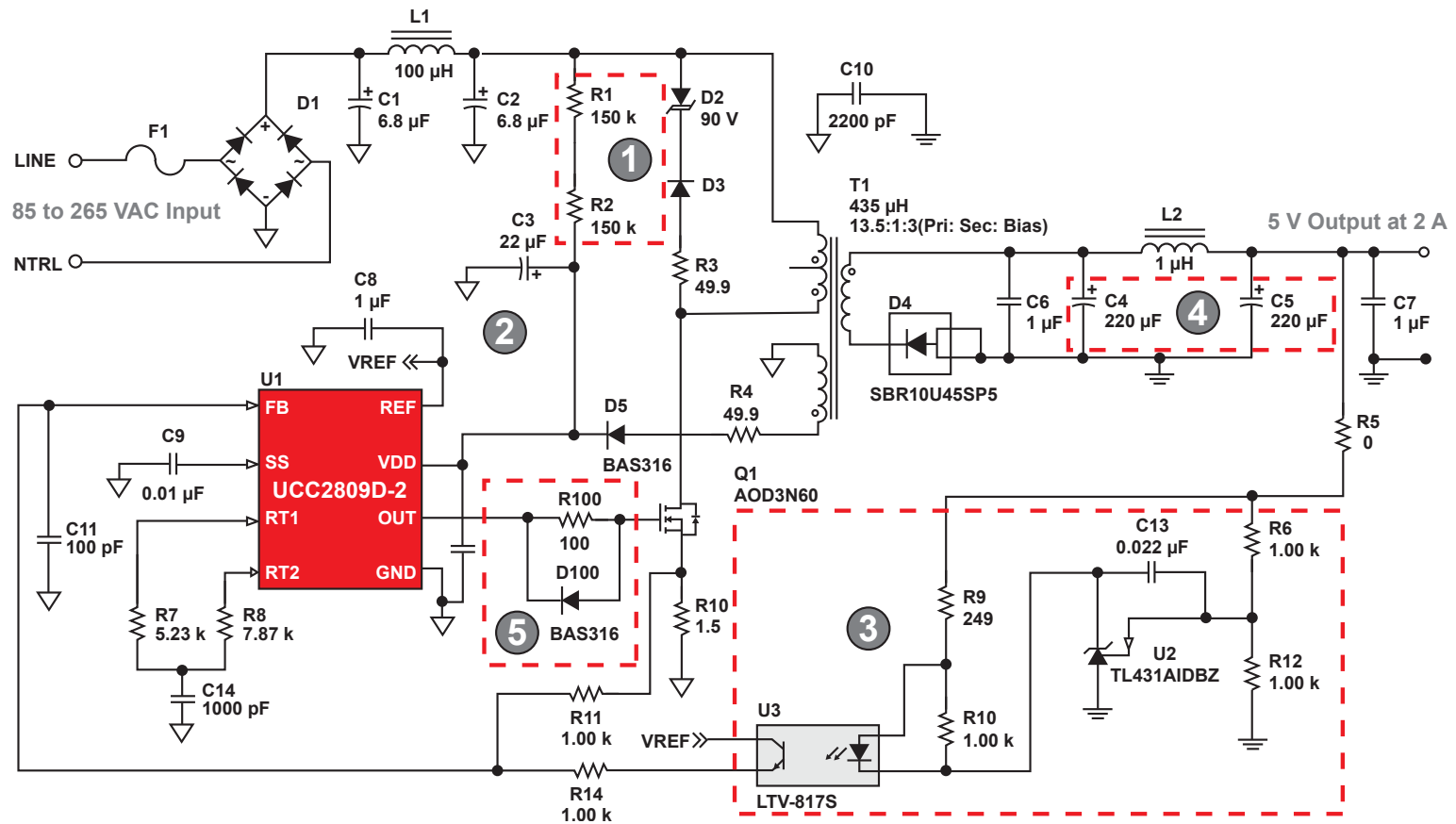


1. Start-up resistors increase standby power
2. Large bias cap; factors include I_{DD} , opto current, UVLO hysteresis
3. TL431 and opto-coupler for regulation
4. Faster loop response allows smaller output caps
5. Minimum on-time requires turn-on resistor at no load operation

DCM/VS/PSR Example

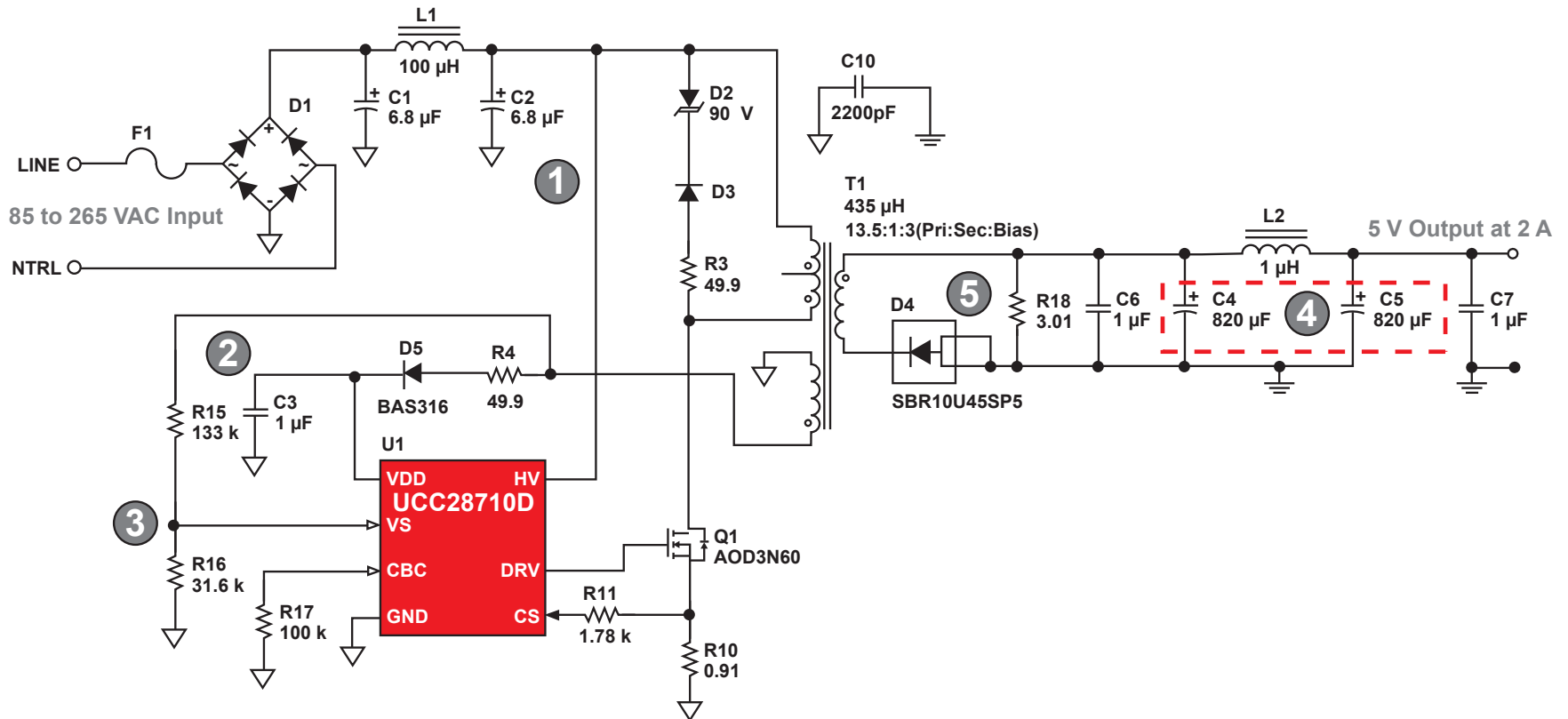

1. No start-up resistors (lower standby)
2. Small bias capacitor
3. PSR eliminates opto-coupler and TL431
4. Larger output capacitors needed for transients
5. Small pre-load resistor needed for no load operation

DCM/VS/Opto Example

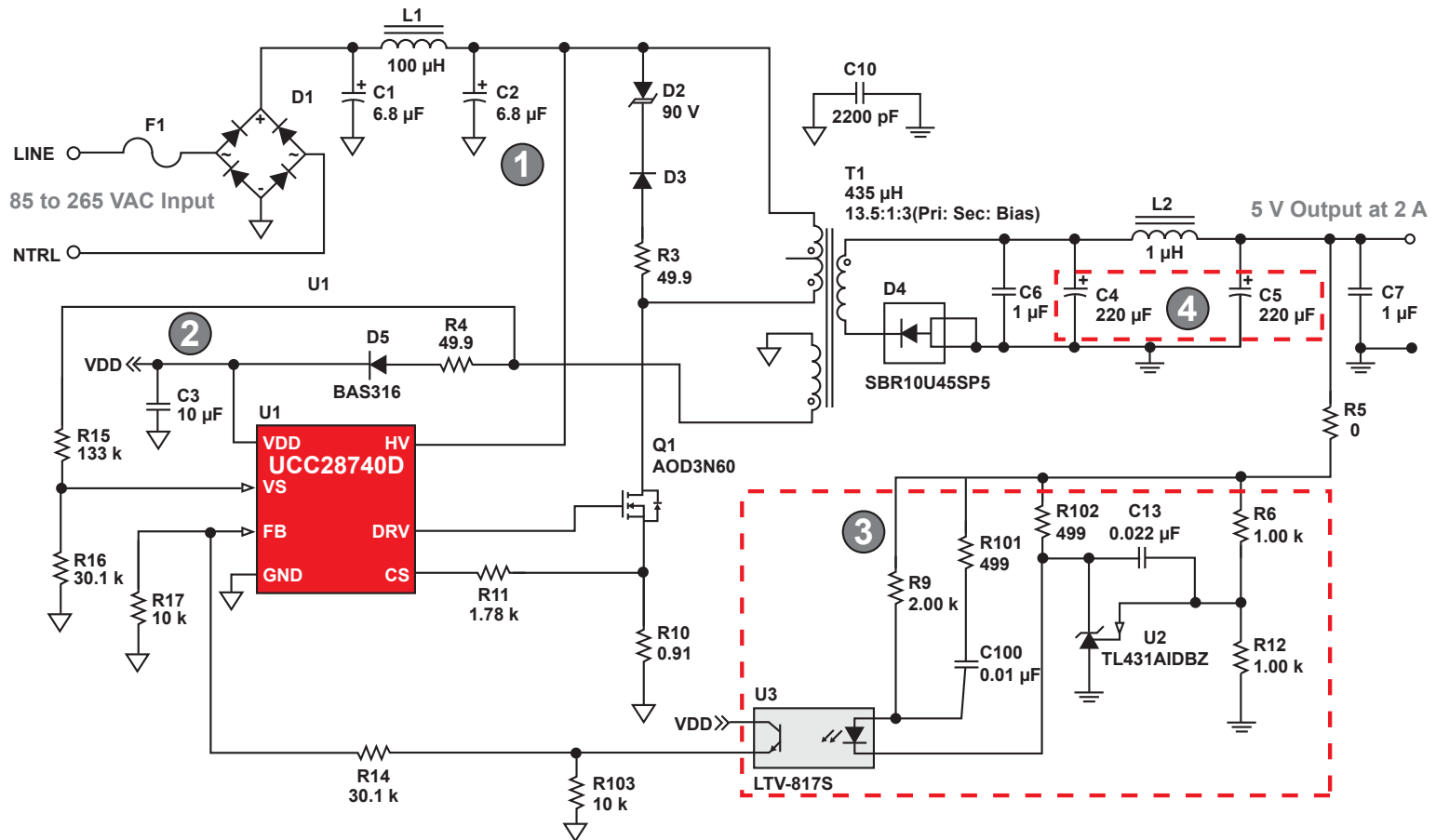



1. No start-up resistors (lower standby power)
2. Medium sized bias capacitor
3. TL431 and opto-coupler regulation

4. Faster loop response allows smaller output caps

Photographs



DCM/FF/Opto

www.ti.com/tool/pmp9203

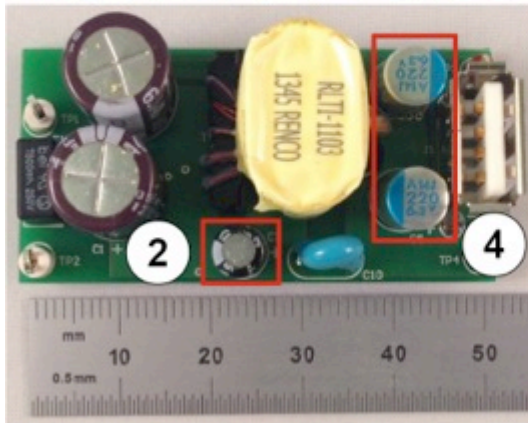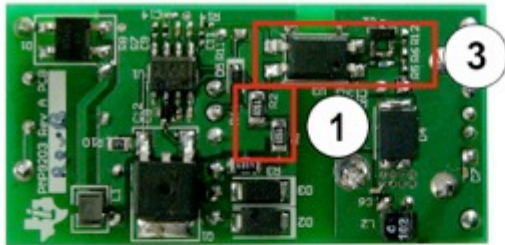



DCM/VS/PSR

www.ti.com/tool/pmp9202

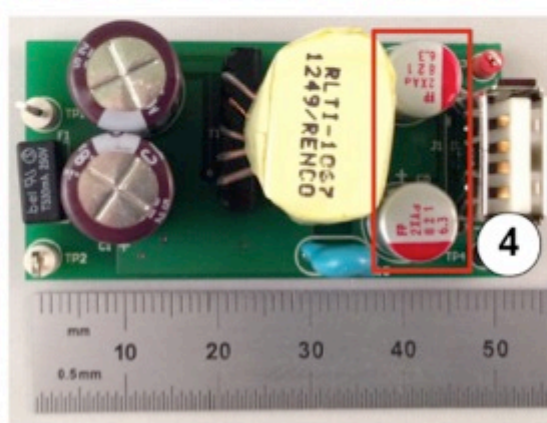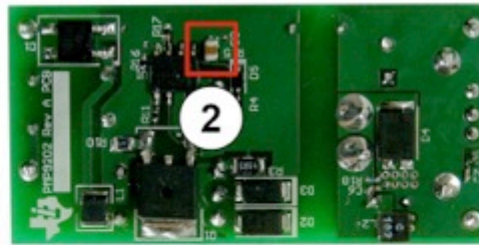

DCM/VS/Opto


www.ti.com/tool/pmp9204

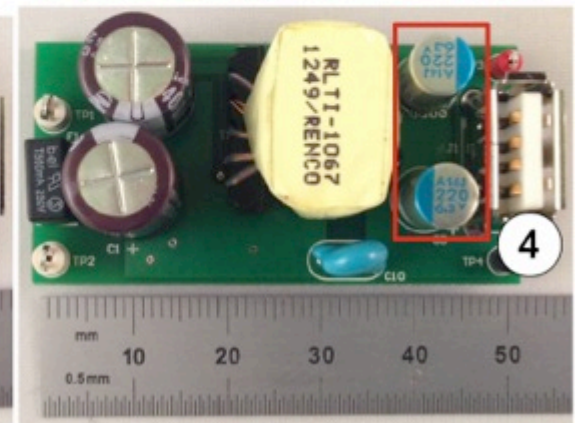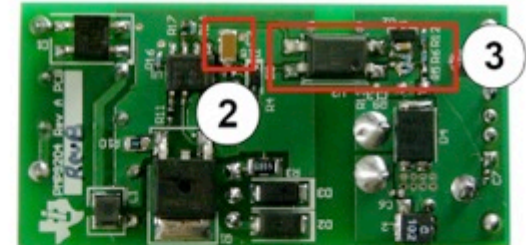

1. Start-up resistors
2. Bias capacitor


3. TL431 and opto-coupler
4. Bias capacitor

Load Regulation

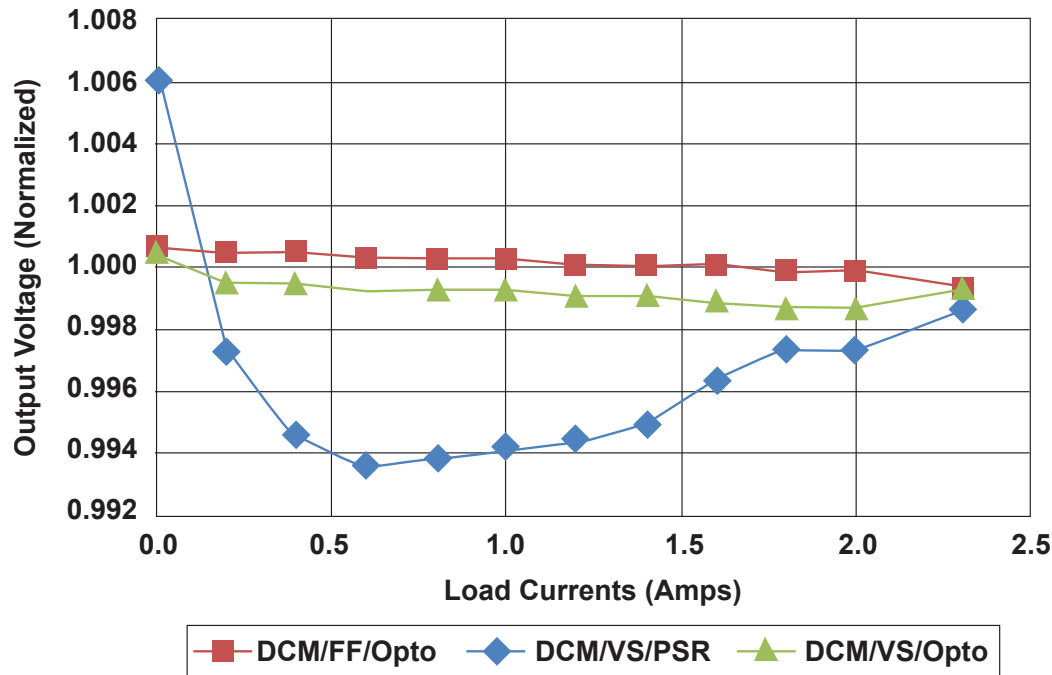



- TL431 and opto-coupler provides excellent load regulation
- PSR uses cable-drop compensation
 - Compensates for resistive drops on the secondary side
 - Keeps load regulation within +/-1%

Overload Protection

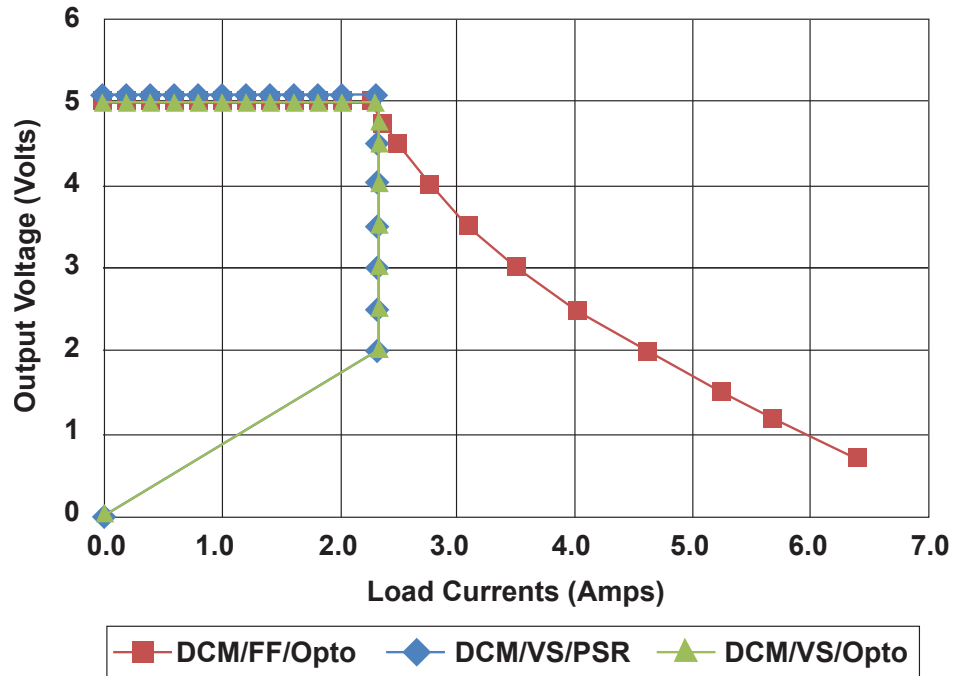


- Traditional fixed-frequency controller:
 - Frequency and peak current held constant
 - Currents during overload can become excessive
- DCM/VS controllers include current regulation feature

Efficiency

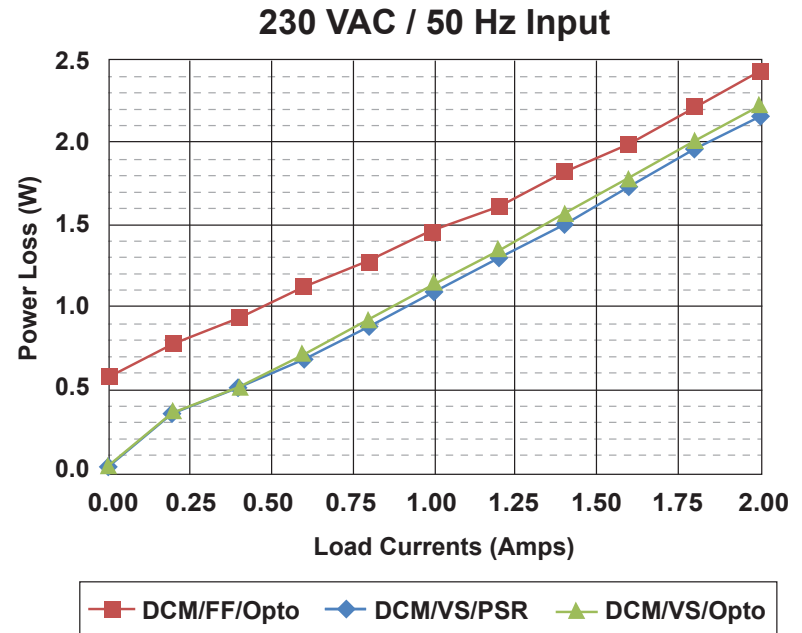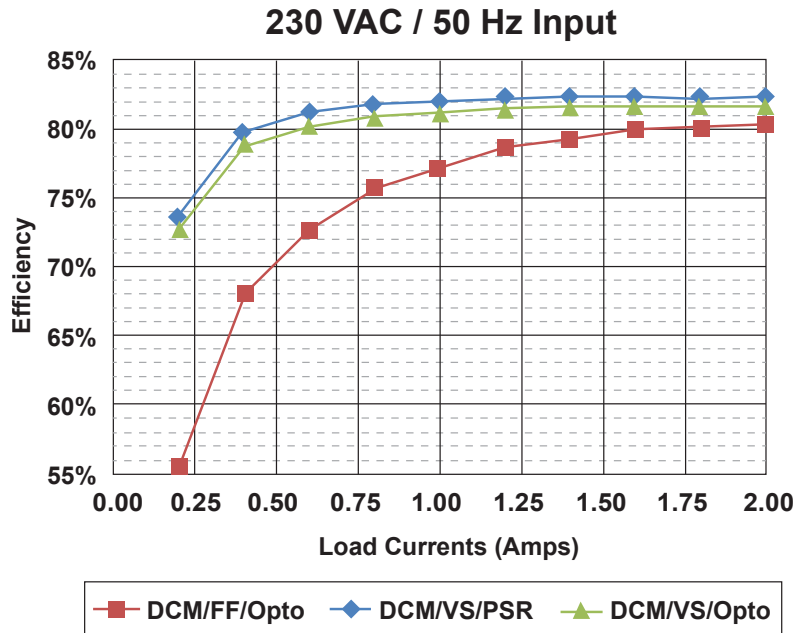



- All designs achieve >80% efficiency at max load
- DCM/VS controllers provide better efficiency at low to medium loads
 - Due to reduced frequency operation
- Start-up resistors have major impact at higher input voltages

Standby Power Consumption

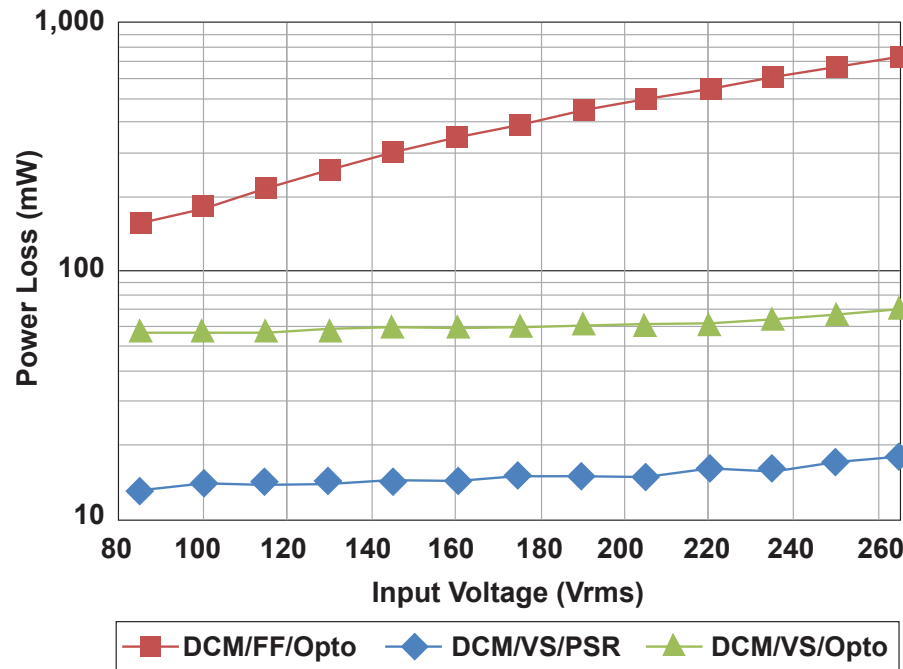



- Pre-load resistor of PSR design accounts for a large portion of P_{sb}
- TL431 and opto-coupler biasing increases P_{sb}
- Fixed frequency example P_{sb} dominated by start-up resistors

Load Transient Response

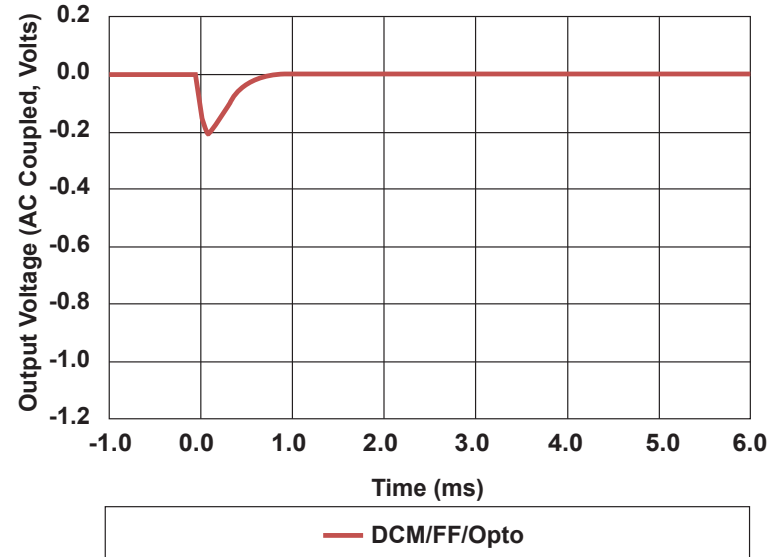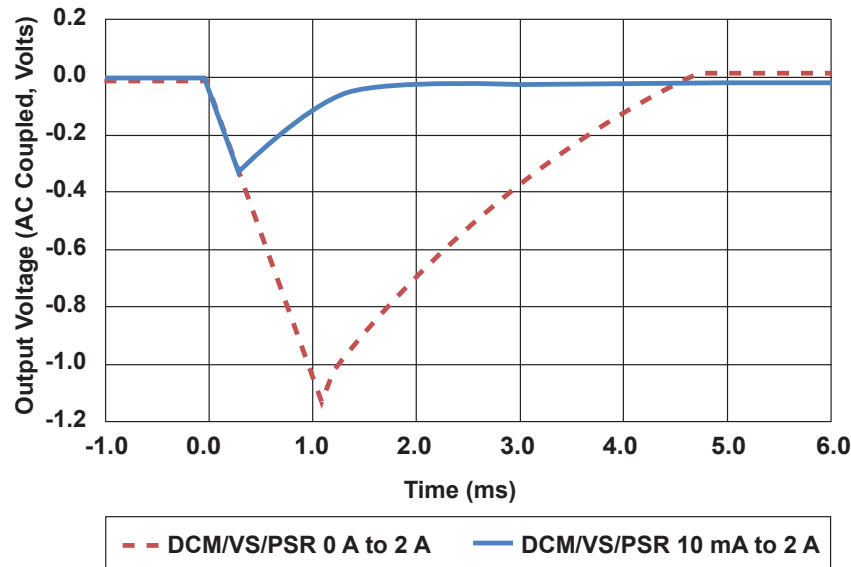

- PSR response varies
 - Dependent on when in the switching cycle the transient hits
 - Starting at 0 A vs. a few mA makes a big difference
- TL431 and opto-coupler response is predictable
 - Dependent on output capacitance and bandwidth

Small Form Factor Example

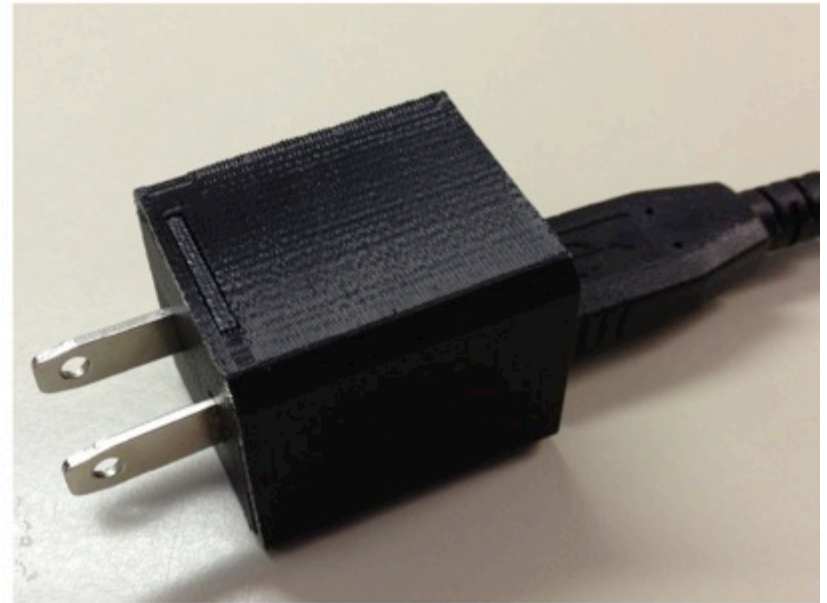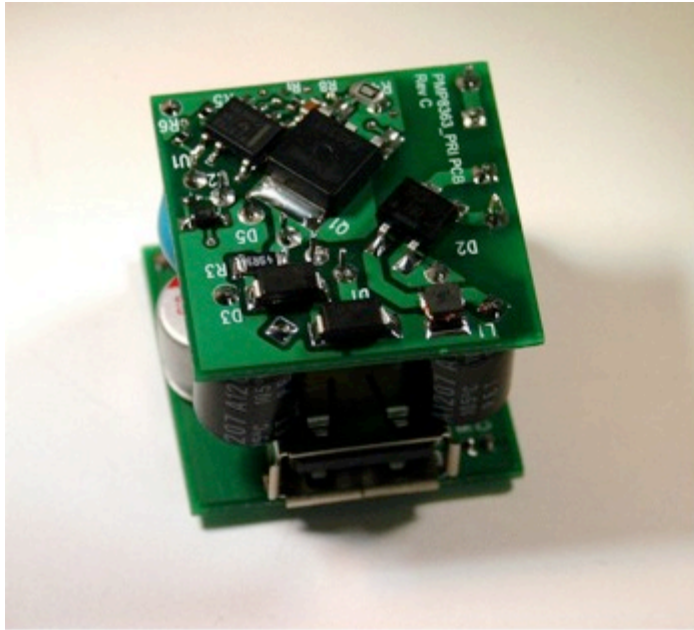

- DCM/VS/PSR example design can be laid out to fit into a 1"x1" cube
- Two secondary transformer wires are the only electrical connection between the two circuit boards (not possible with opto feedback)
- Small product size requires efficiency >80% to prevent thermal issues
- PMP8363 available on PowerLab: <http://www.ti.com/tool/pmp8363>

Comparison Summary

	DCM/FF/Opto	DCM/VS/PSR	DCM/VS/Opto
Output Voltage Accuracy	+/-2% ★	+/-5%	+/-2% ★
Load Regulation	+/-0.1% ★	+/-0.6%	+/-0.1% ★
Max Load Eff. (115 VAC / 230 VAC)	82.0% / 80.4% ★	82.2% / 82.5% ★	81.3% / 81.7% ★
Standby Power (115 VAC / 230 VAC)	216 mW / 584 mW	14 mW / 16 mW ★	57 mW / 64 mW ★
Load Transients (0 A to 2 A)	-200 mV ★	-1100 mV	-200 mV ★
Current Regulation	Not Provided	+/-5% ★	+/-5% ★
# of Components	41	27 ★	37
Relative Cost	Low	Lowest ★	Low

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com