

# **Guidelines for Choosing the Right Buck Regulator Control Strategy (Part B)**


Brian Cheng  
Eric Lee  
Brian Lynch  
Robert Taylor

# How Do You Choose?



- **Part A**
  - Buck regulator basics
  - Fixed frequency control
- **Part B**
  - Variable frequency control
    - Constant on-time
    - Adaptive on-time
  - TI D-CAP™ families
    - D-CAP2™
    - D-CAP3™
    - D-CAP+™
  - Conclusions





# Variable Frequency Control

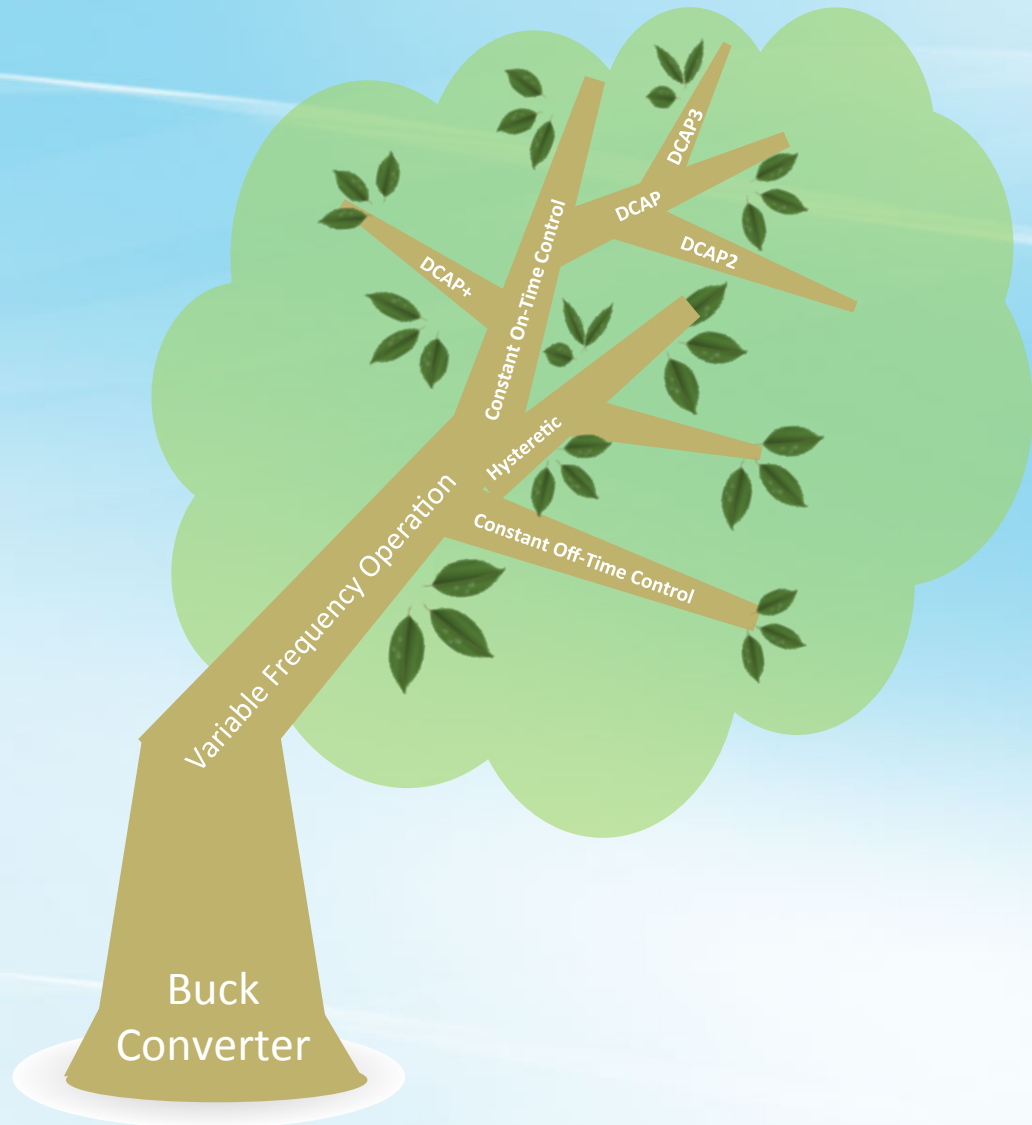

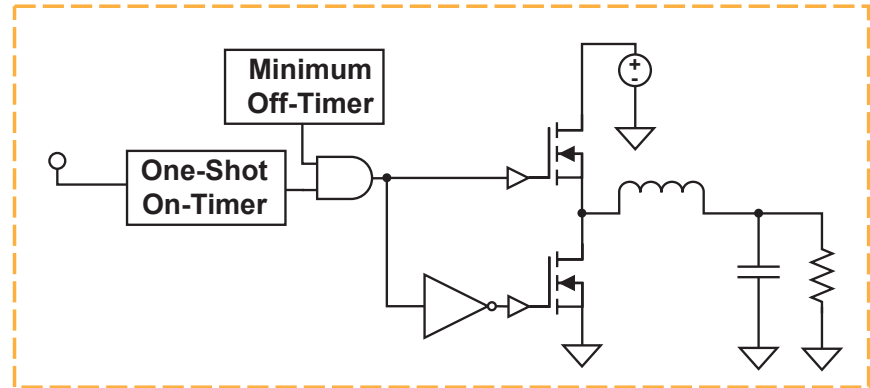
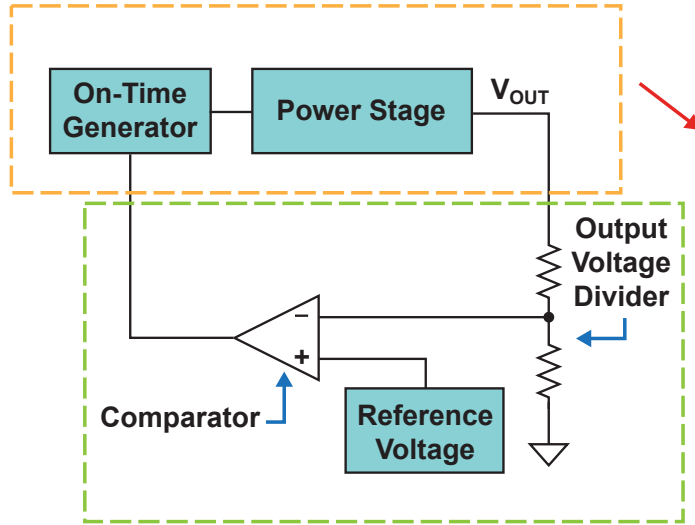
# Constant On-Time Control – Basic Operation



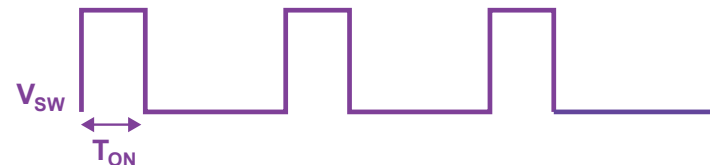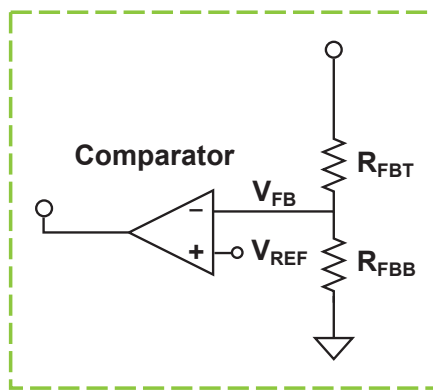- Initiate fixed on-time when  $V_{FB} < V_{REF}$
- On-time can be fixed or changed by input voltage




# Adaptive On-Time Control – Frequency

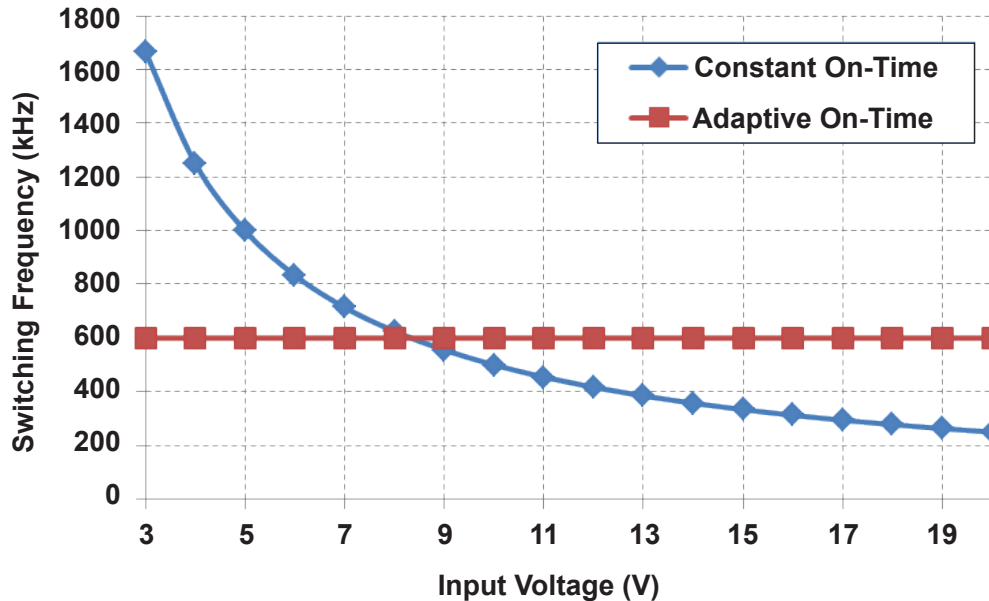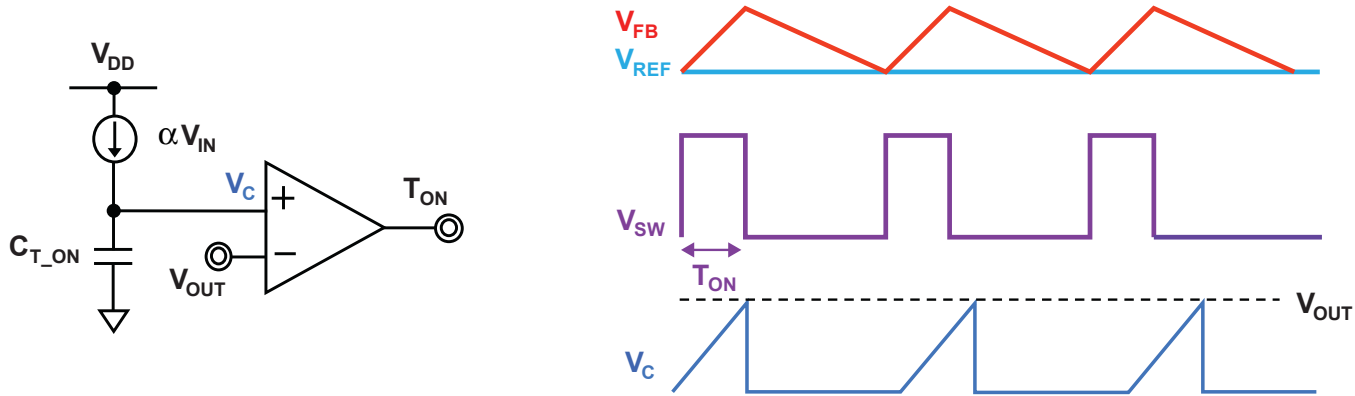


- Constant on-time has a fixed  $T_{ON}$
- Adaptive on-time adjusts the  $T_{ON}$  based on the input voltage

# COT Control – Transient Performance

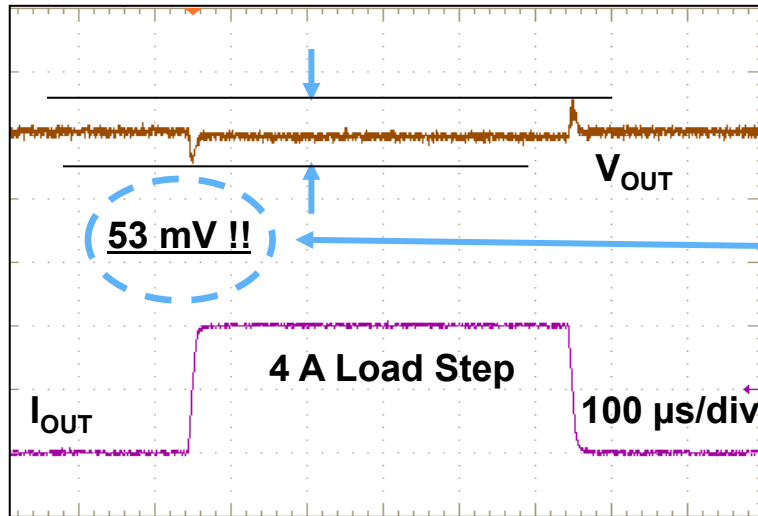

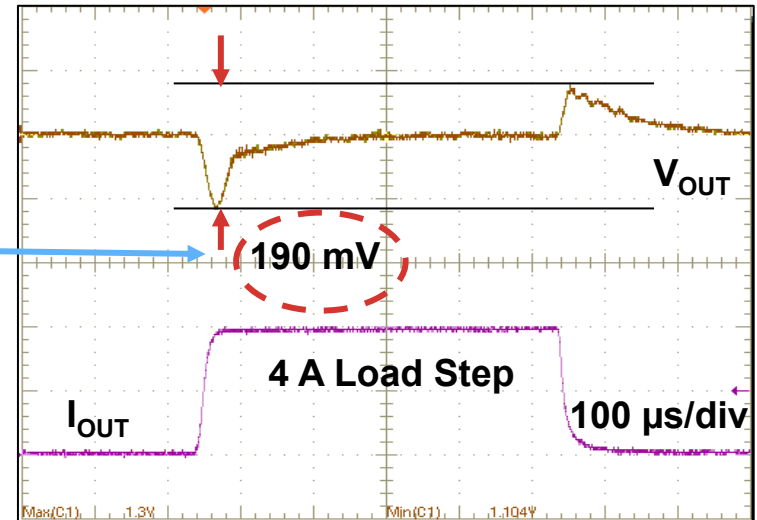
**D-CAP™ Mode** – Output Cap = 22  $\mu$ Fx3



**Voltage Mode** – Output Cap = 100  $\mu$ Fx4

- D-CAP™ mode: direct output capacitor voltage feedback
- D-CAP™ mode does not have an error amplifier or compensation

# COT Control – Seamless DCM/CCM

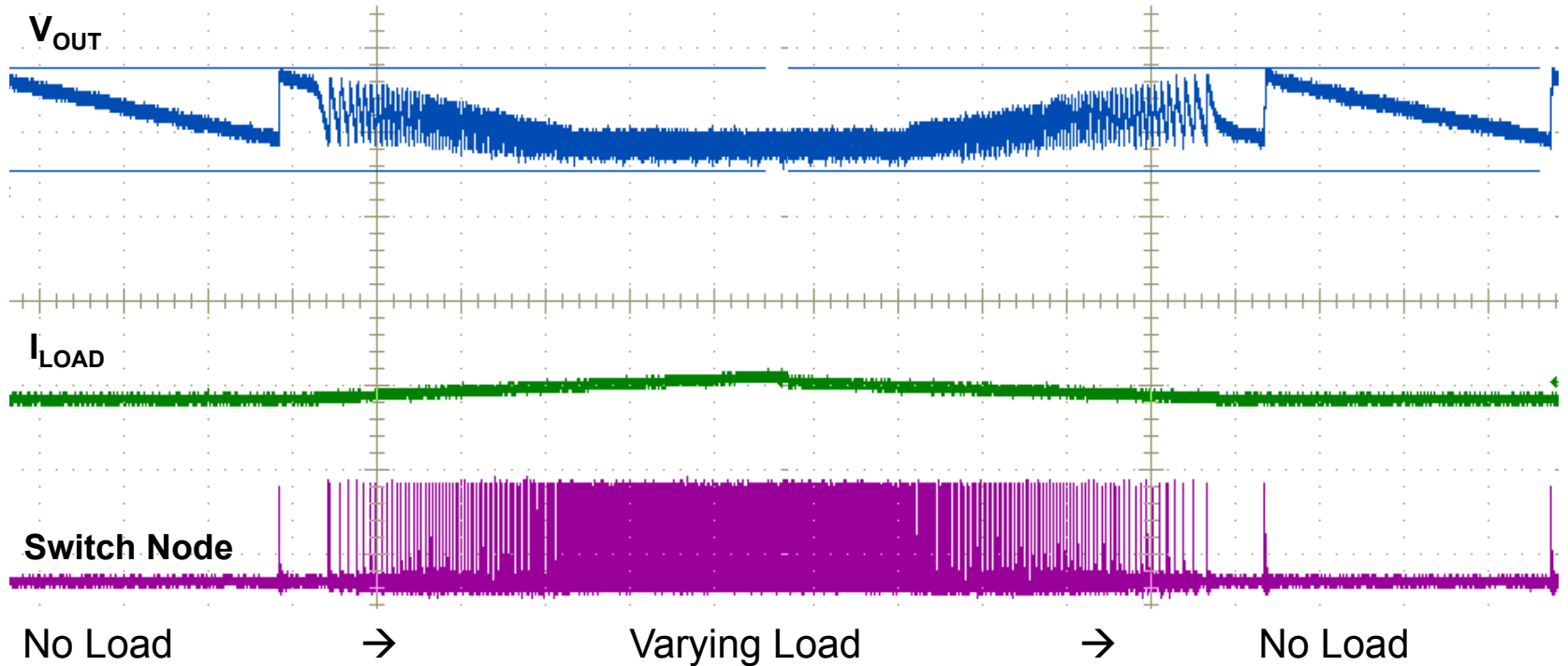


- The DCM/CCM transition is happening naturally without a mode change

# COT Control – High Efficiency @ Light Loads


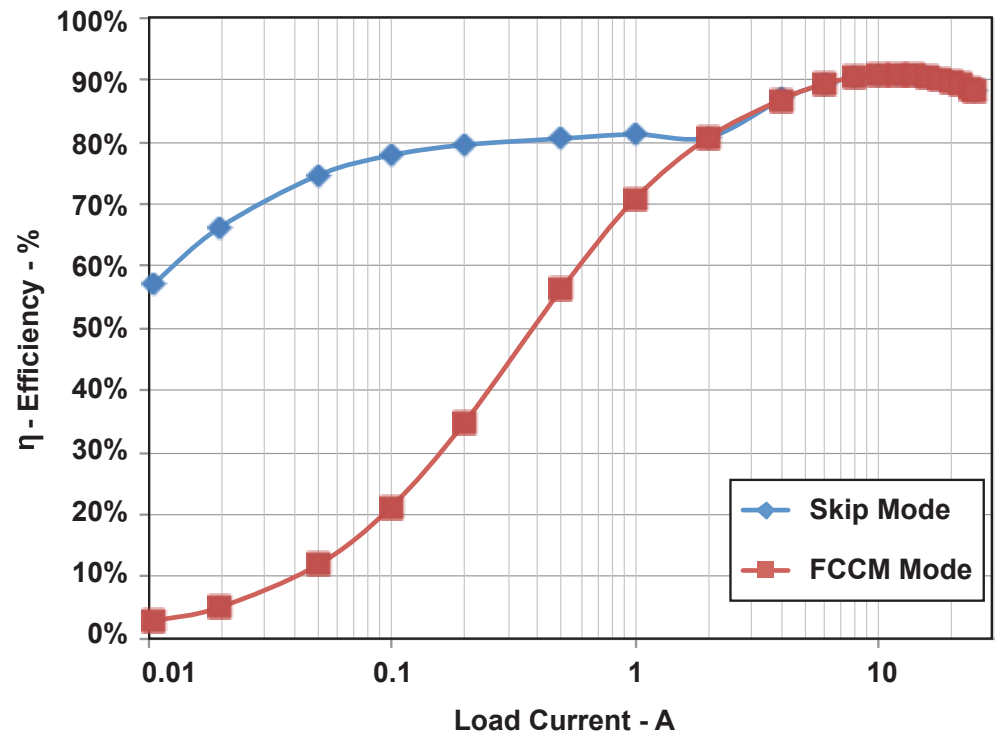
## TPS53219 + CSD86350

- Efficiency  $F_{SW} = 500 \text{ kHz}$ , 12 V to 1.1 V
  - > 80% from 0.2 A to 25 A
  - > 55% efficiency in Skip mode at 10 mA






# COT Control – External Components

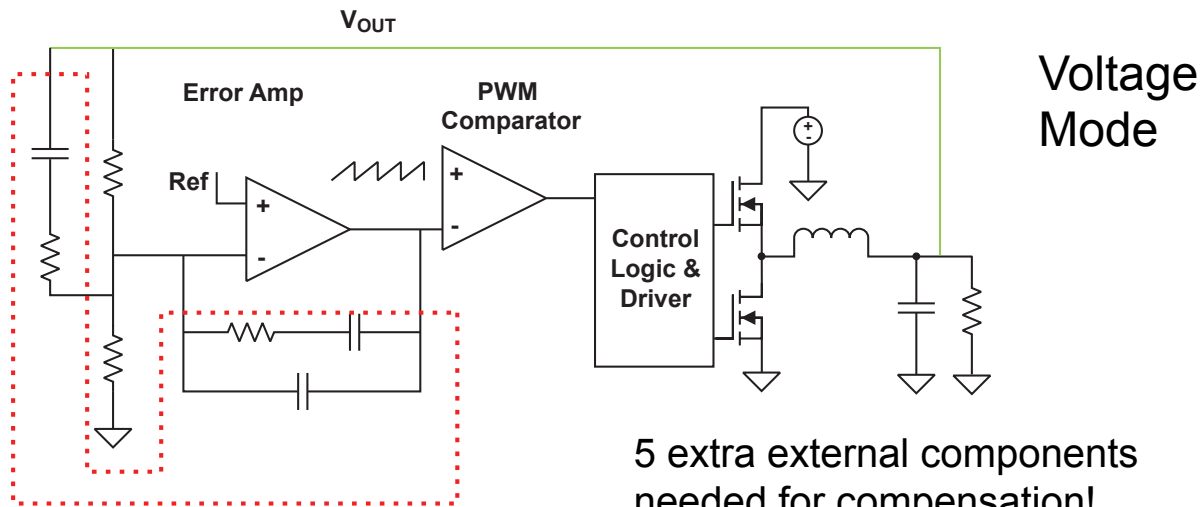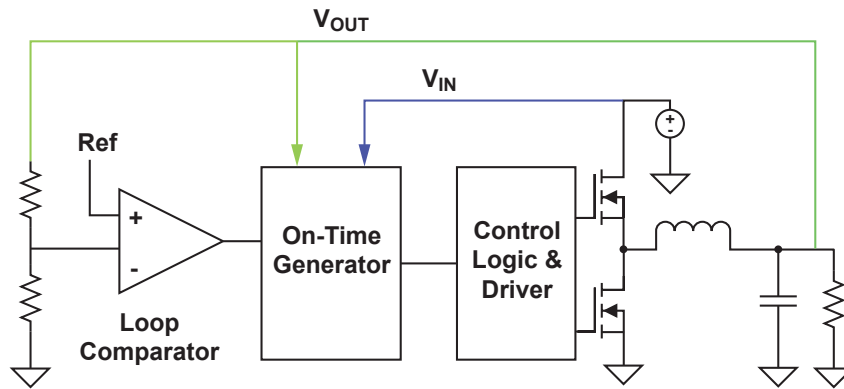

# TI D-CAP™ Control Architecture

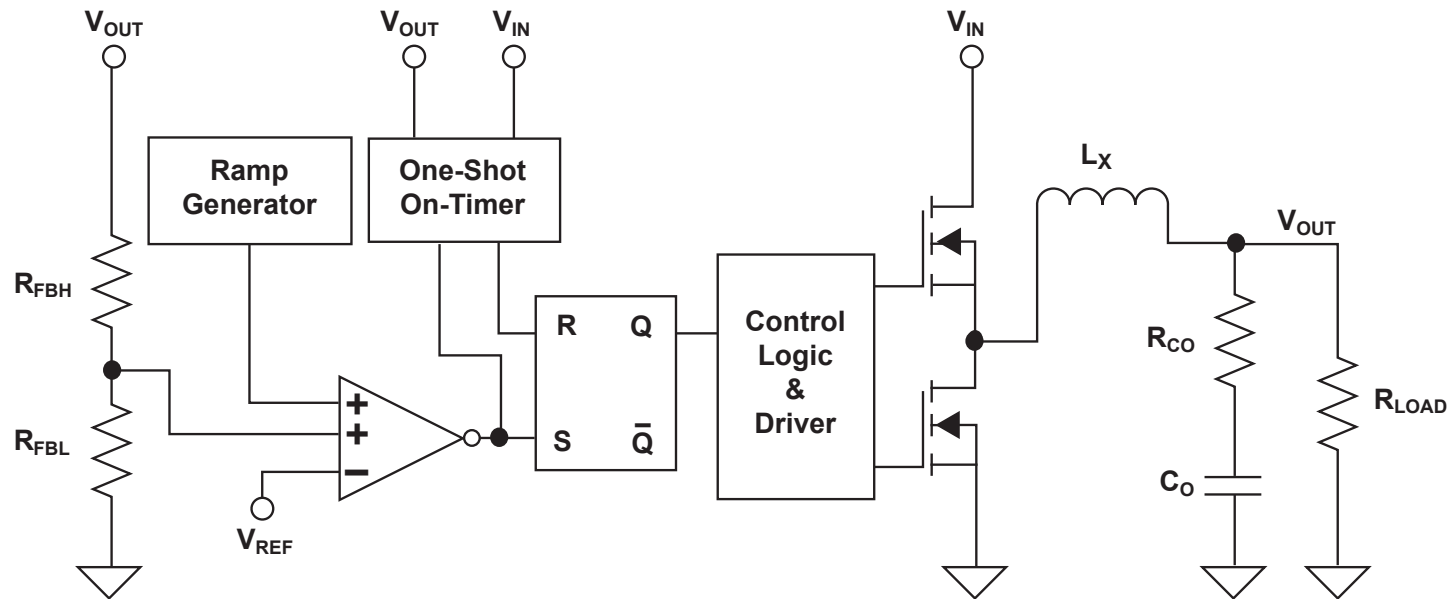


- Adaptive constant on-time  $T_{ON} = \frac{V_{OUT}}{V_{IN}} \times K$
- Ramp is generated to improve the jitter performance


# COT Control – Ramp Compensation

- Ramp compensation improves jitter performance by reducing the noise band
- Ramp compensation is built-in to most TI D-CAP controllers

### No Ramp Compensation

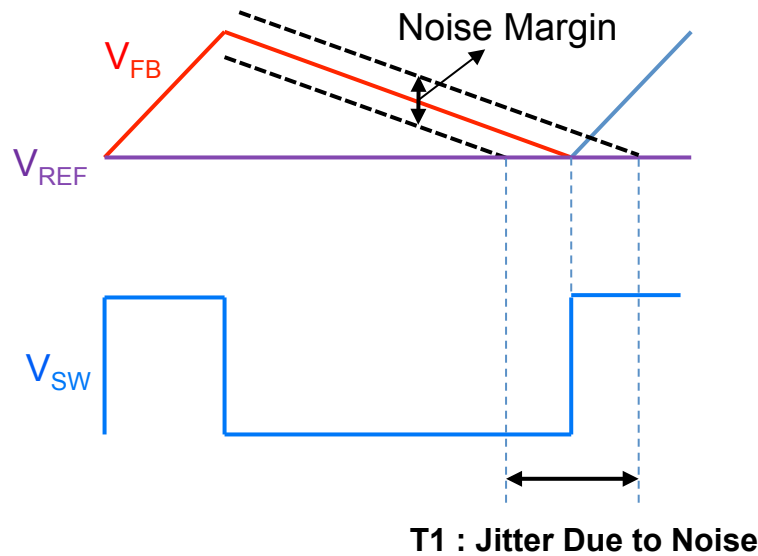



### With Ramp Compensation

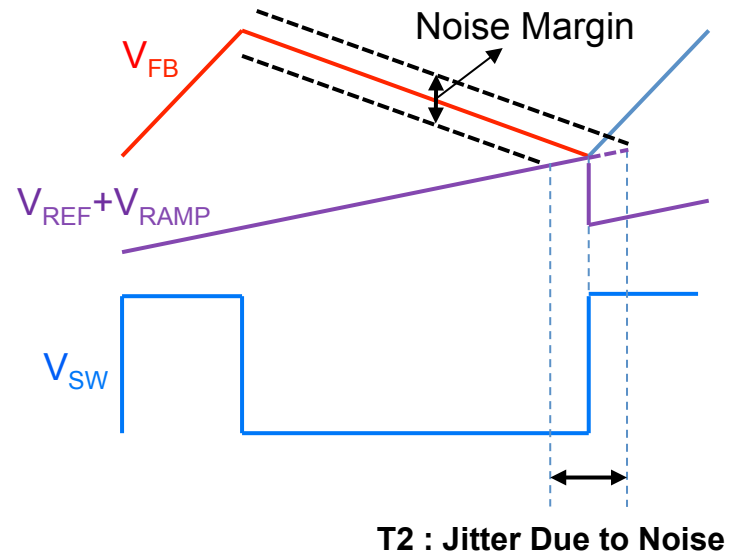

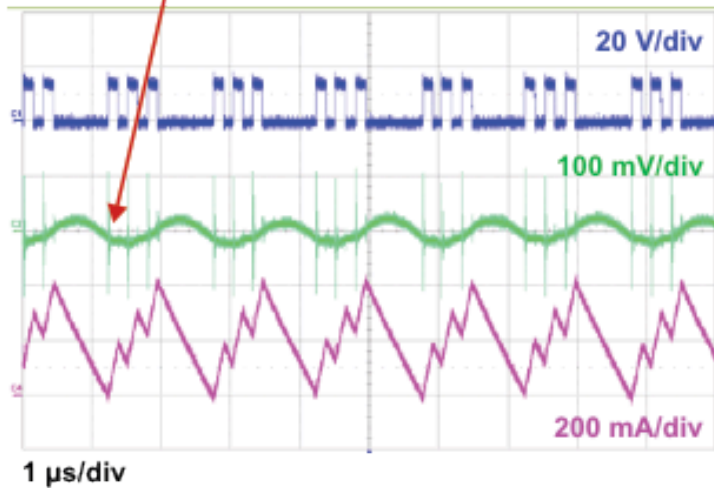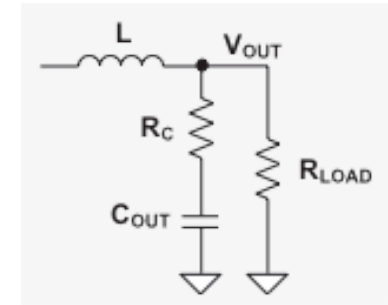
# TI D-CAP™ – Ripple Requirements

Feedback signal going down when it should be going up!!

$$\Delta V_{OUT} = \Delta I_L \times R_{Co} + \frac{\Delta I_L}{8 \times f_{SW} \times C_O} = V_{ESR} + V_C$$



Without Series Resistor  $R_C$

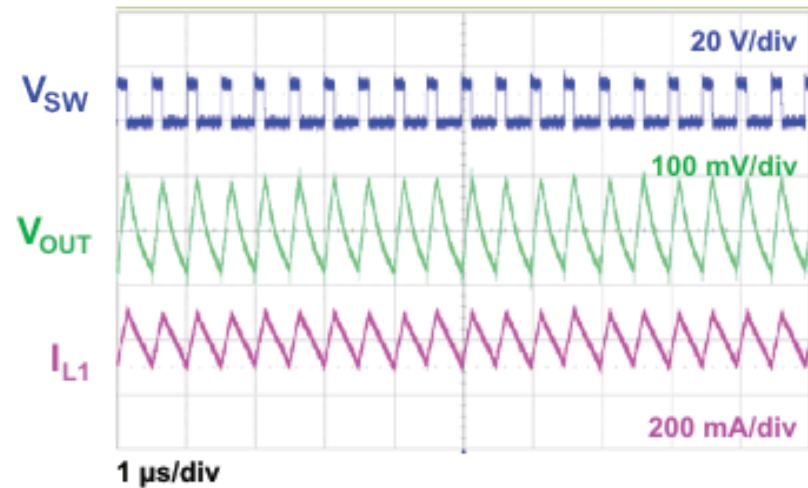


With Sufficient  $R_C$

# TI D-CAP™ – Stability Measurement



- Conventional open-loop Bode plot measurement is not applied to COT control architecture since output is directly fed back to PWM modulator
- Closed-loop frequency measurement used to indicate stability issue
- Due to inherent load feed-forward capability, bandwidth measured from small-signal analyses will not indicate large-signal load transient performance

# TI D-CAP2™ Control Architecture

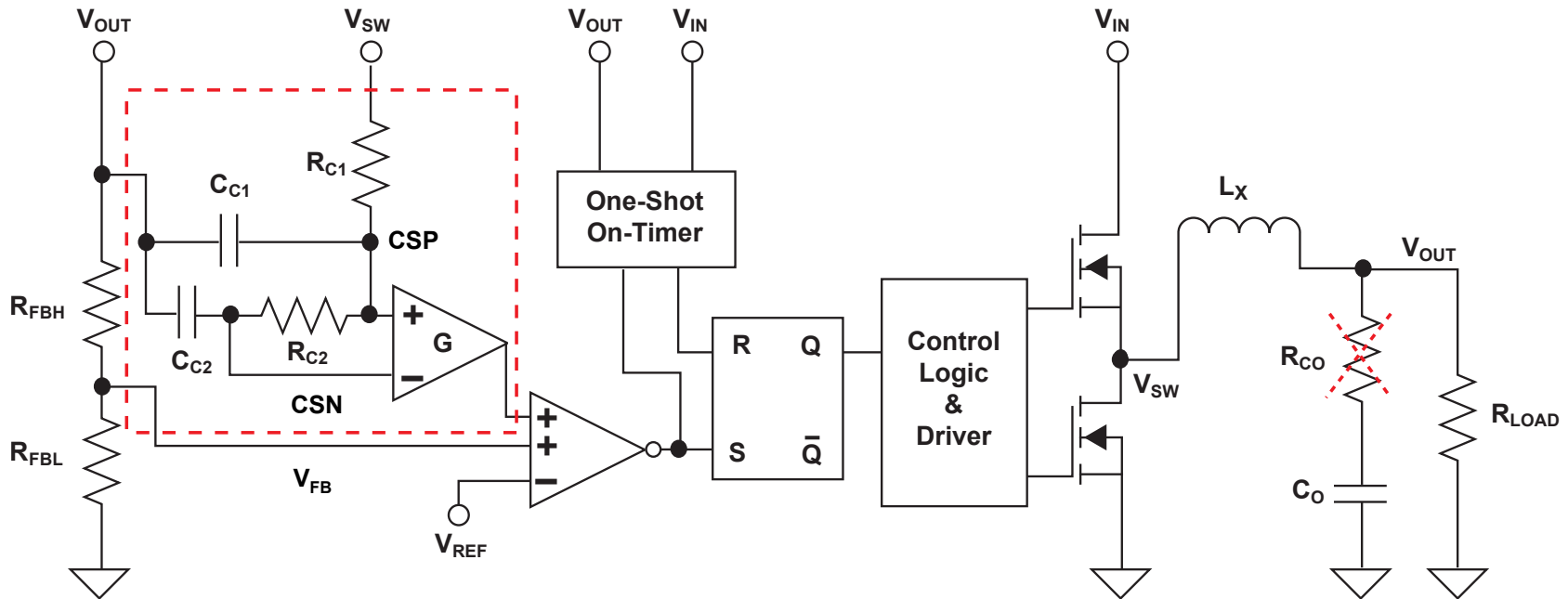

- Adaptive constant on-time  $T_{ON} = \frac{V_{OUT}}{V_{IN}} \times K$
- Ripple injection is added to D-CAP2™
- This allows stability with low output ripple and ceramic output capacitors

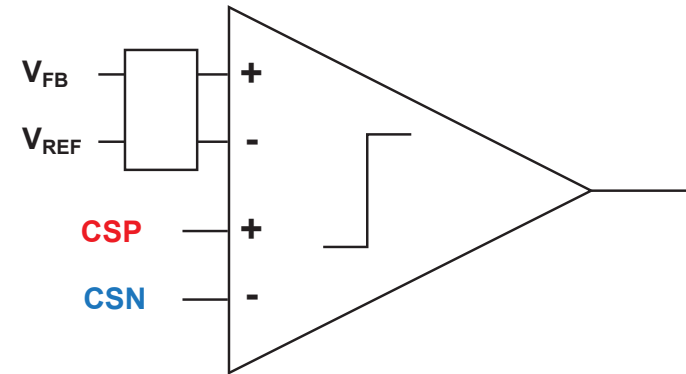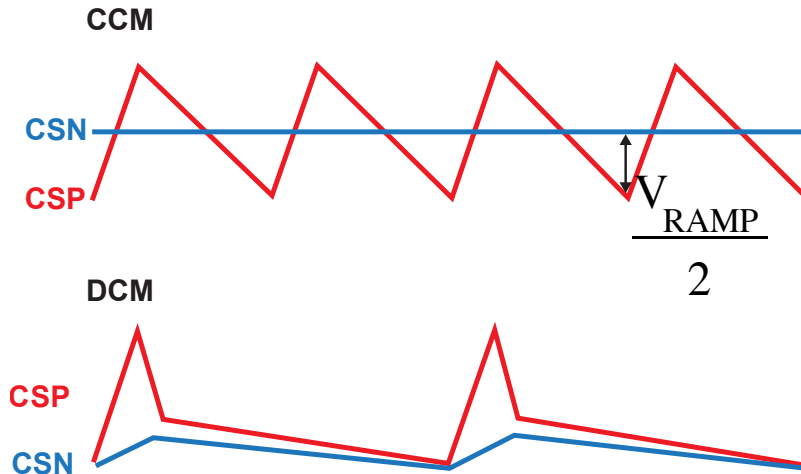
# TI D-CAP2™ – Output Accuracy in DCM/CCM




- Under CCM:  $V_{FB} - V_{REF} \cong \frac{V_{RAMP}}{2}$
- Under deep DCM:  $V_{FB} \cong V_{REF}$
- Offset is not constant in CCM and DCM

# TI D-CAP2™ – Duty Cycle Dependency

12 V to 0.6 V

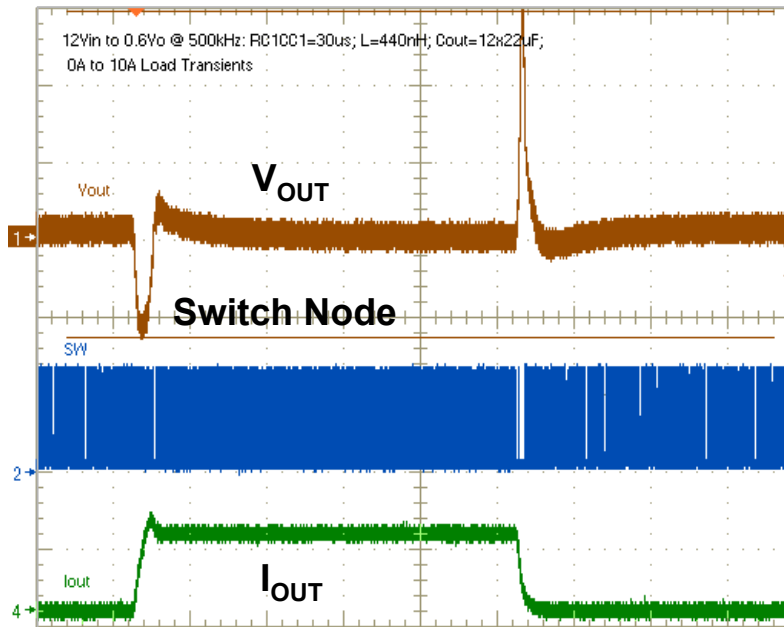


12 V to 5 V

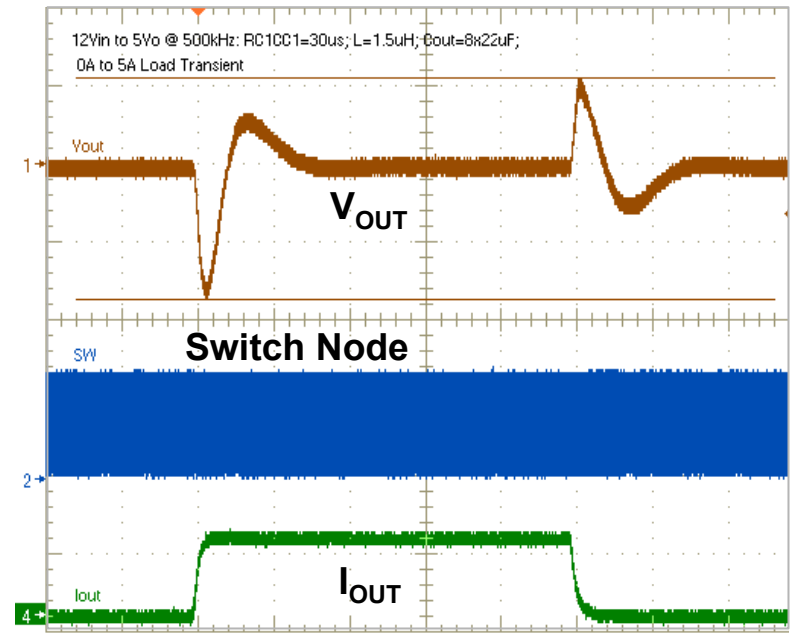

- Fixed  $R_{C1}C_{C1}$  time constant = 30  $\mu$ s for both outputs
- Transient performance is very different with different duty cycles




# TI D-CAP3™ Control Architecture

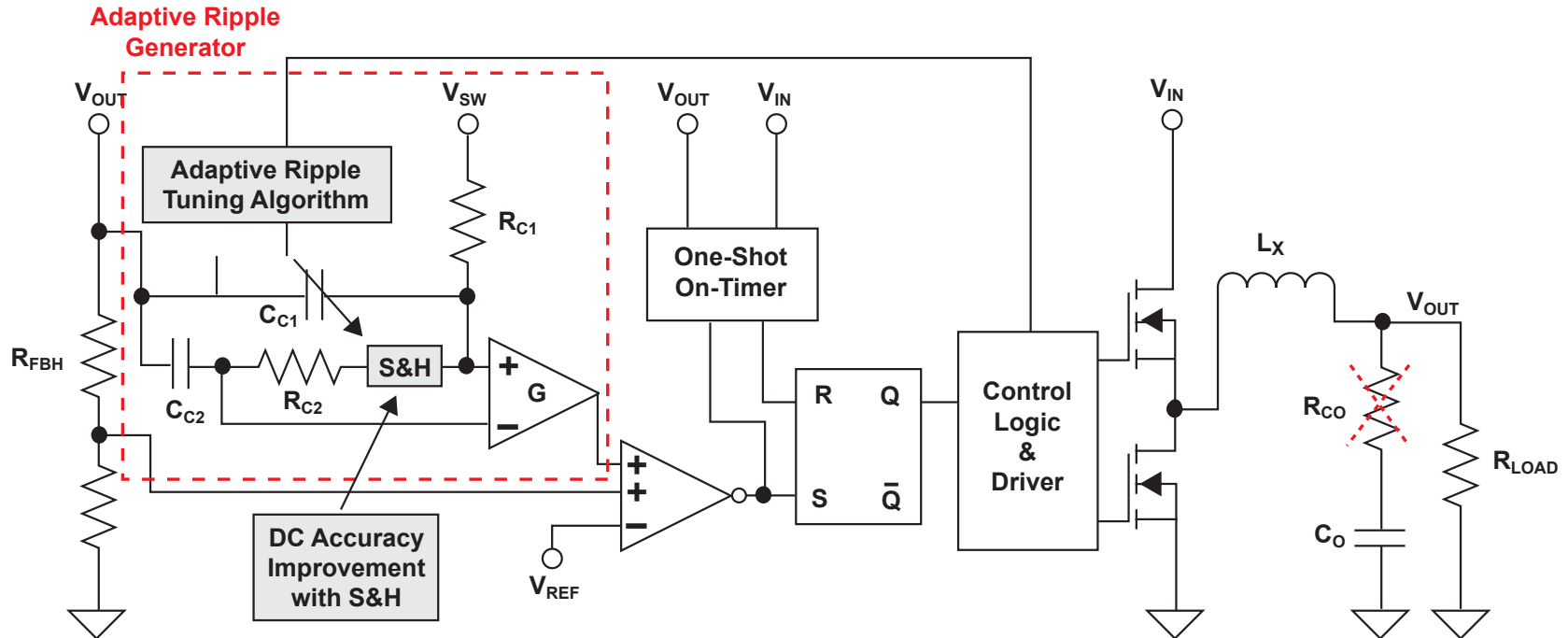


- All of the benefits of D-CAP2™
- Adaptive ripple algorithm changes  $R_{C1}C_{C1}$  time constant with  $V_{IN}$ ,  $V_{OUT}$  and  $I_{OUT}$
- Sample and hold circuit improves DC accuracy

# TI D-CAP3™ – $V_{OUT}$ Accuracy

## D-CAP2™

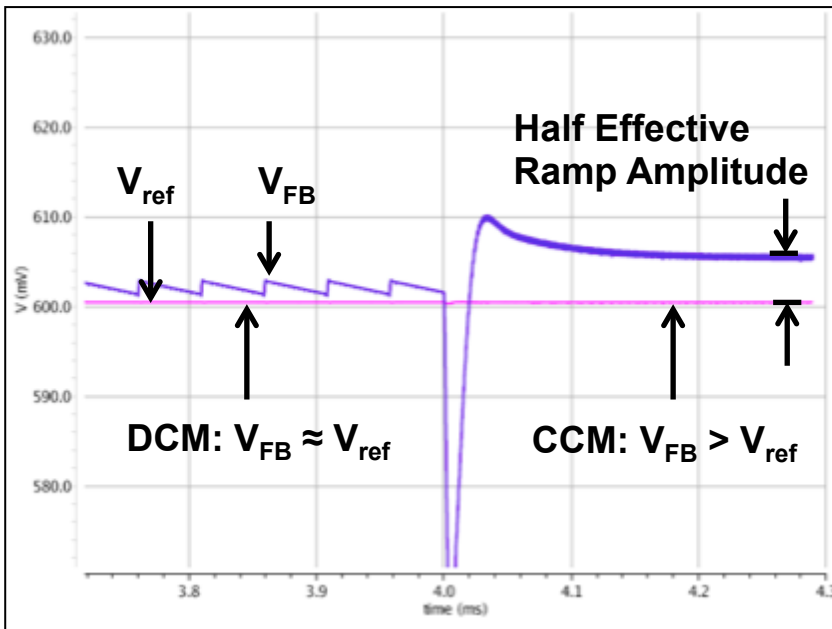

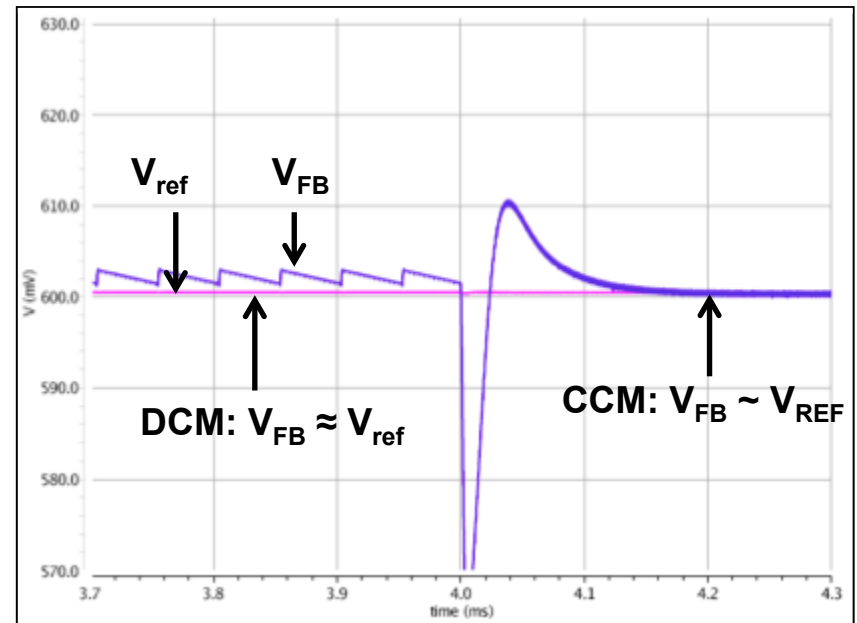
## D-CAP3™ (With Sample-and-Hold Circuits)




- DC accuracy is improved in CCM operation

# TI D-CAP3™ – Adaptive Ripple Injection

## D-CAP2™ 12 V to 5 V

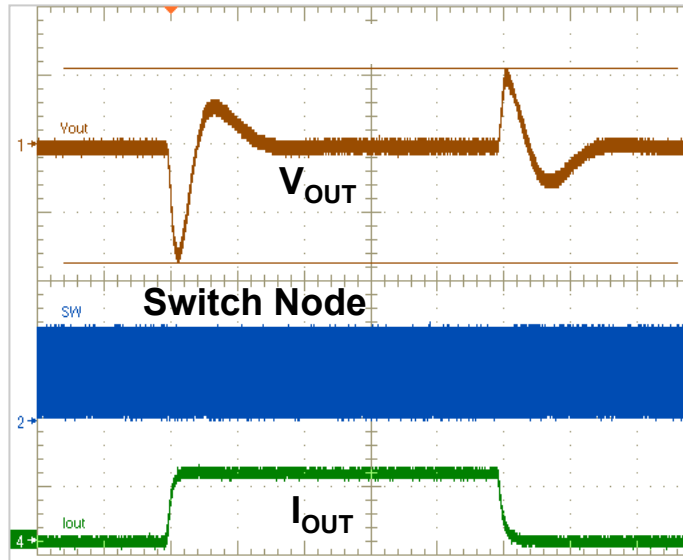

## D-CAP3™ 12 V to 5V (With Adaptive Ripple)

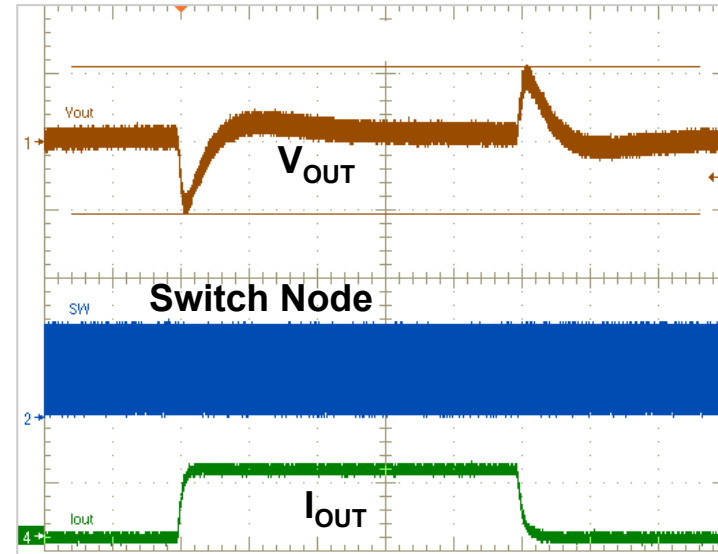


CH1 – Brown, 200 mV/Div

CH2 – Blue, 10 V/Div

CH4 – Green, 5 A/Div

- Time constant for D-CAP2™ = 30  $\mu$ s
- Time constant for D-CAP3™ = 120  $\mu$ s
- Adaptive ripple algorithm changes RC time constant with  $V_{IN}$ ,  $V_{OUT}$  and  $I_{OUT}$
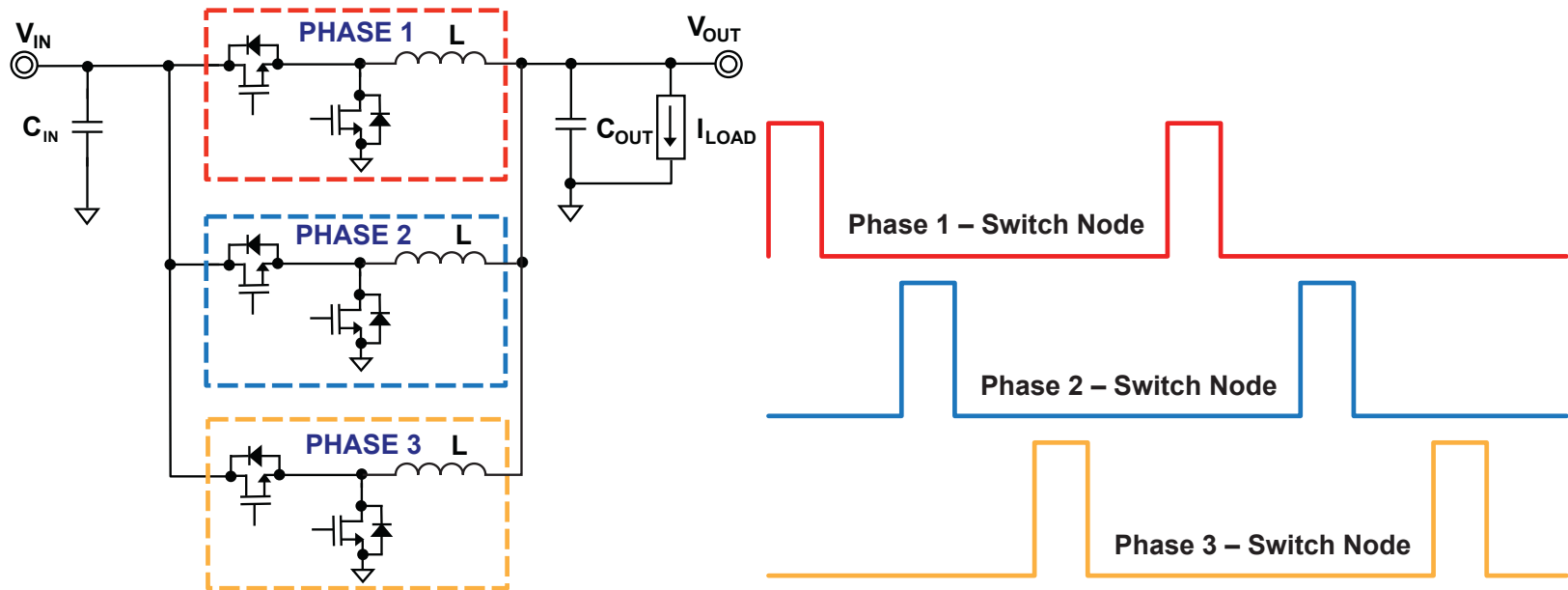
# Multiphase DC-DC Converter – Introduction




- Set of parallel converters
- Each power-stage is known as a ***phase***
- The phases operate equally spaced through the period


# Multiphase DC-DC Converter – Output Ripple

Reduced output ripple current → Lower output capacitance to maintain same voltage ripple

Normalized Output Current Ripple

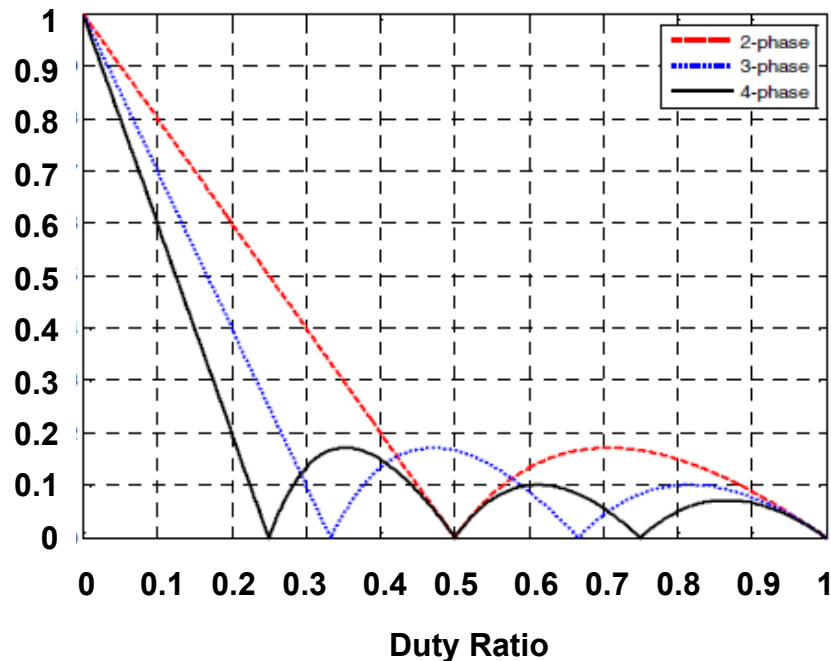


Example – Two-Phase System

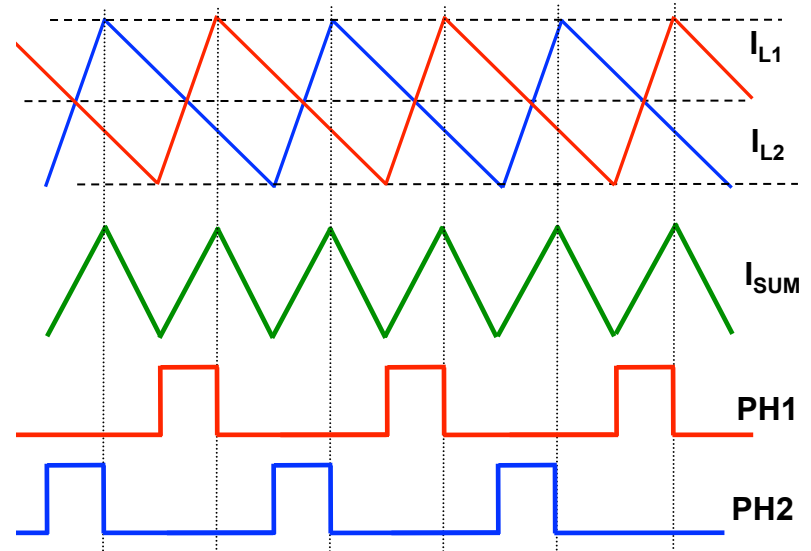
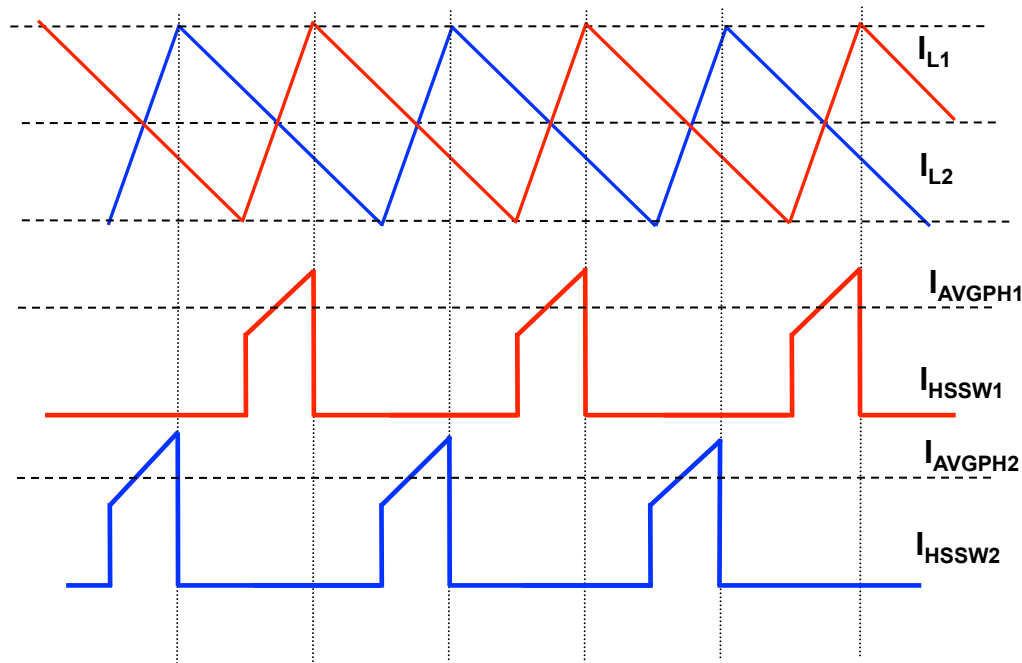
# Multiphase DC-DC Converter – Input Ripple


**Reduced switch current** → Distributed power loss and better thermal performance



**Lower input RMS current** → Smaller capacitance, lower ESR power loss, reduced self heating
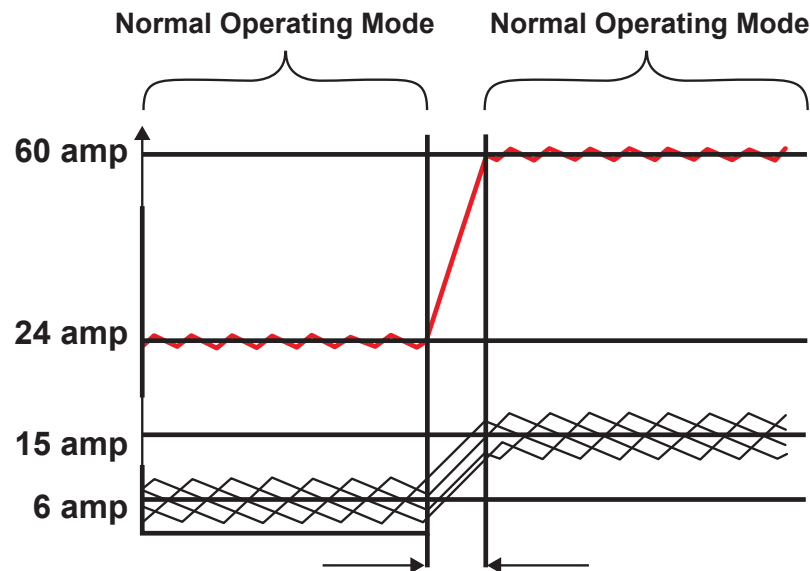
# Multiphase DC-DC Converter – Load Transients


Improved transient with pulse overlap → Lower output capacitance



- During load insertion, all the phases (N) are turned on
  - If L is the inductor of each phase, effective inductance is  $L/N$
  - Ability to deliver current to the output capacitor is N times higher than single-phase

# Multiphase DC-DC Converter – High Efficiency



## High Efficiency Over Wide Load Range

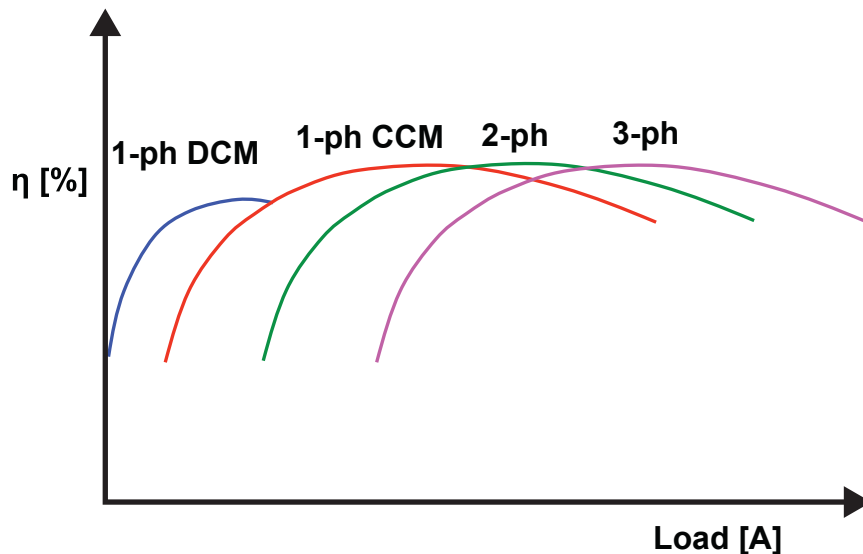

- Dynamic phase management is integral to achieve high-efficiency over wide loading conditions
  - Higher load current, more phases
  - As load current is reduced, there is a trade-off between switching and conduction losses — dropping phases can optimize the efficiency
  - At extreme light load, the power supply transitions to single-phase discontinuous conduction mode (DCM)




# TI D-CAP+™ Control Architecture

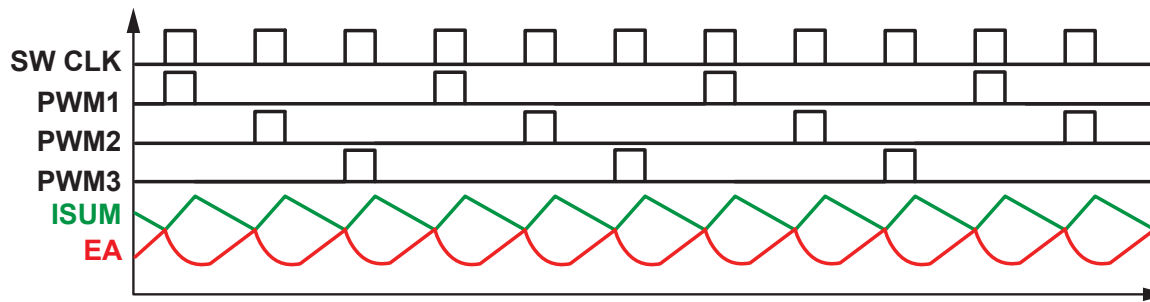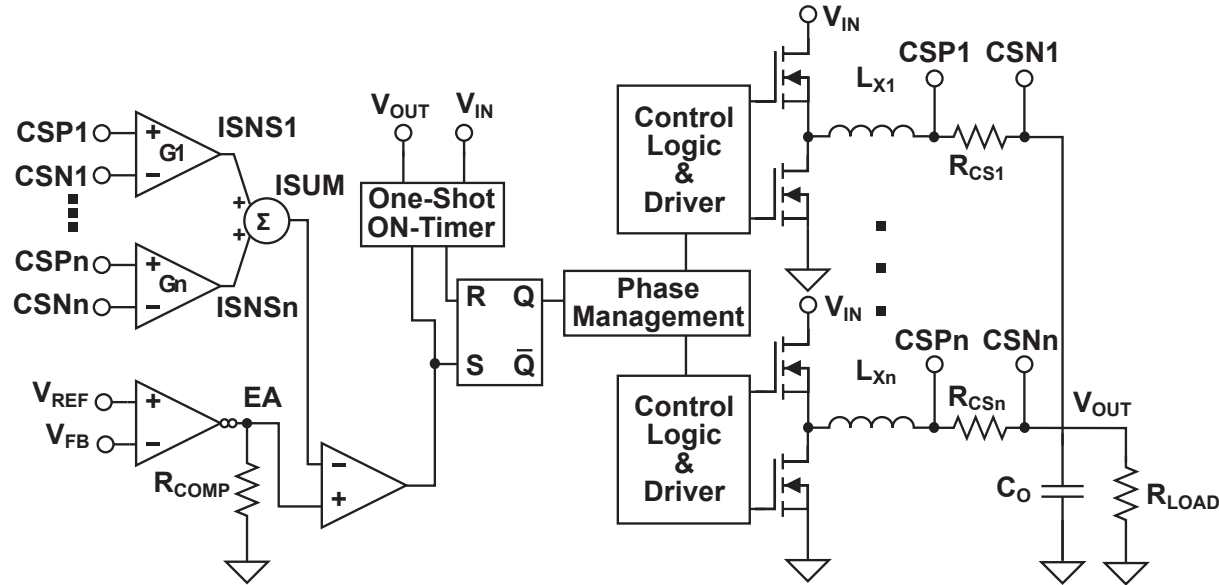


# TI D-CAP+™ – Illustrated Transient Waveforms

## Load Step-Up

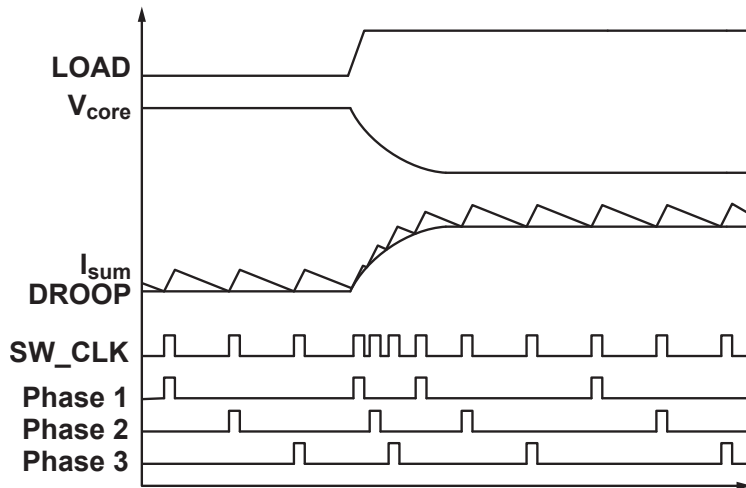


## Load Step-Down

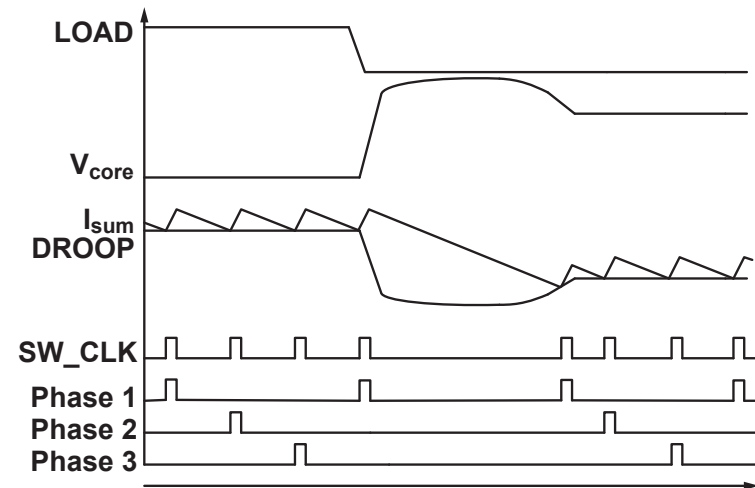

- Pseudo constant switching frequency at steady state without internal clocks
- Variable switching frequency during load transients
- Dynamic current sharing during load transients



# TI D-CAP+™ – Dynamic Phase Shedding

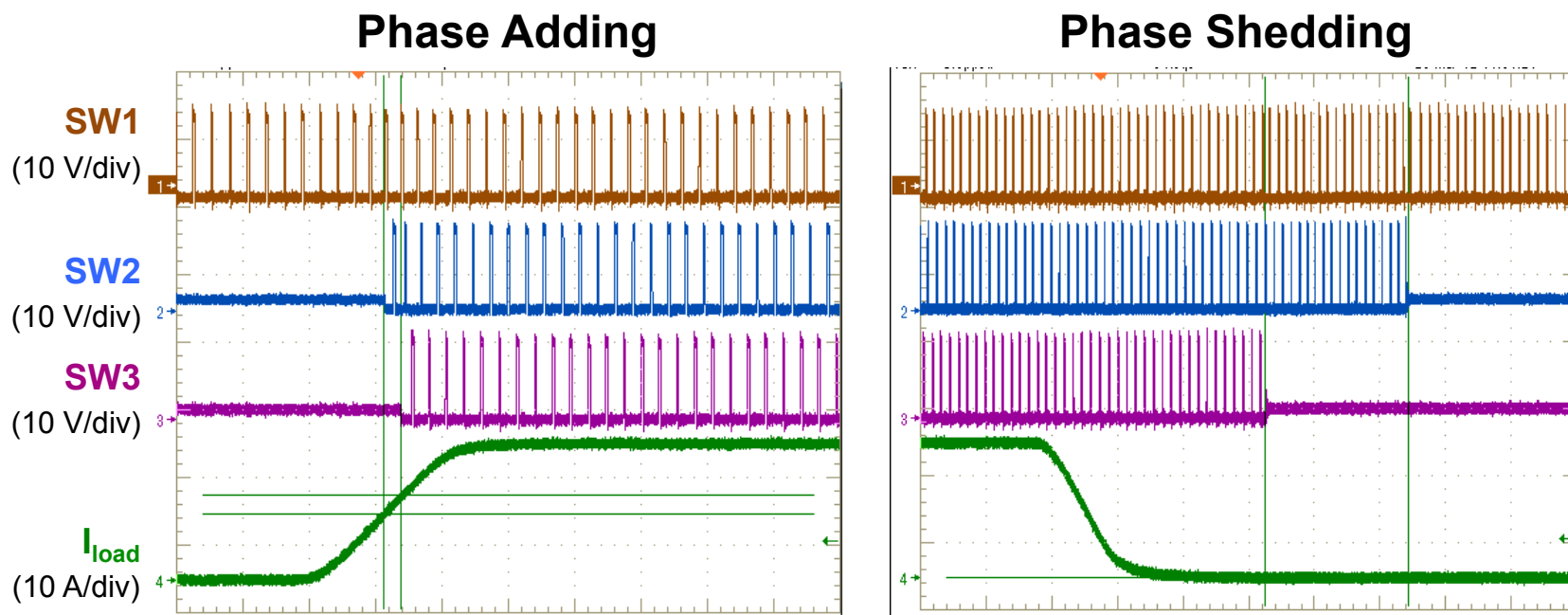

- Phase adding/shedding is determined based on the instantaneous ISUM
- Consists of both current and time hysteresis for phase shedding
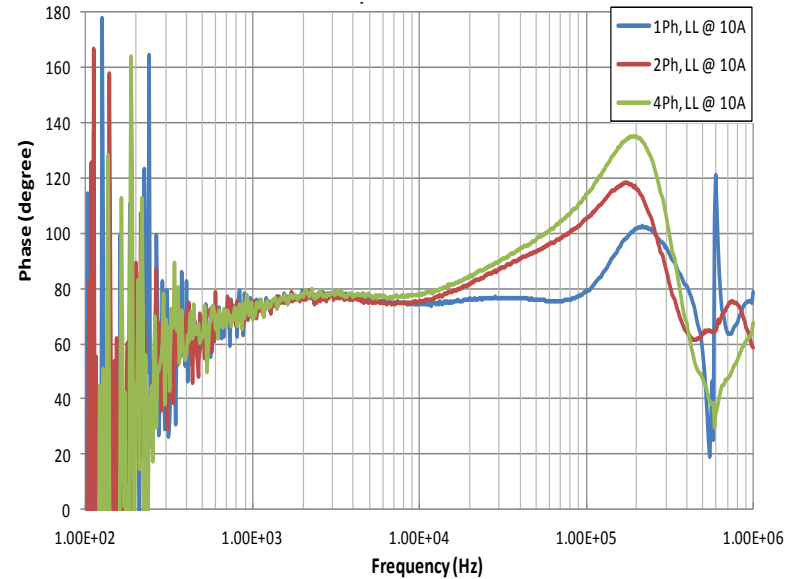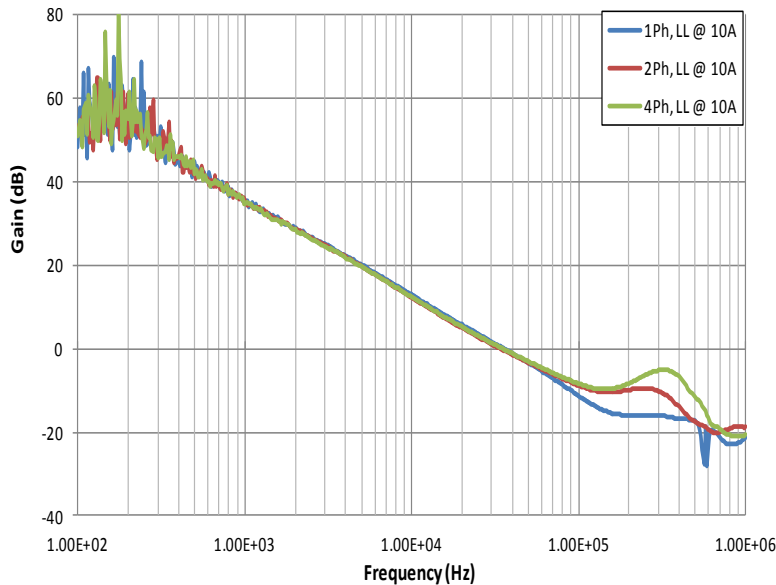
# TI D-CAP+™ – Loop Gains with Different Phases


TPS53640 with 12 V<sub>IN</sub> to 1.7 V<sub>OUT</sub> @ 600 kHz, 10 A load and 1 mΩ loadline



**Loop Gain is Insensitive to the Number of Phases**
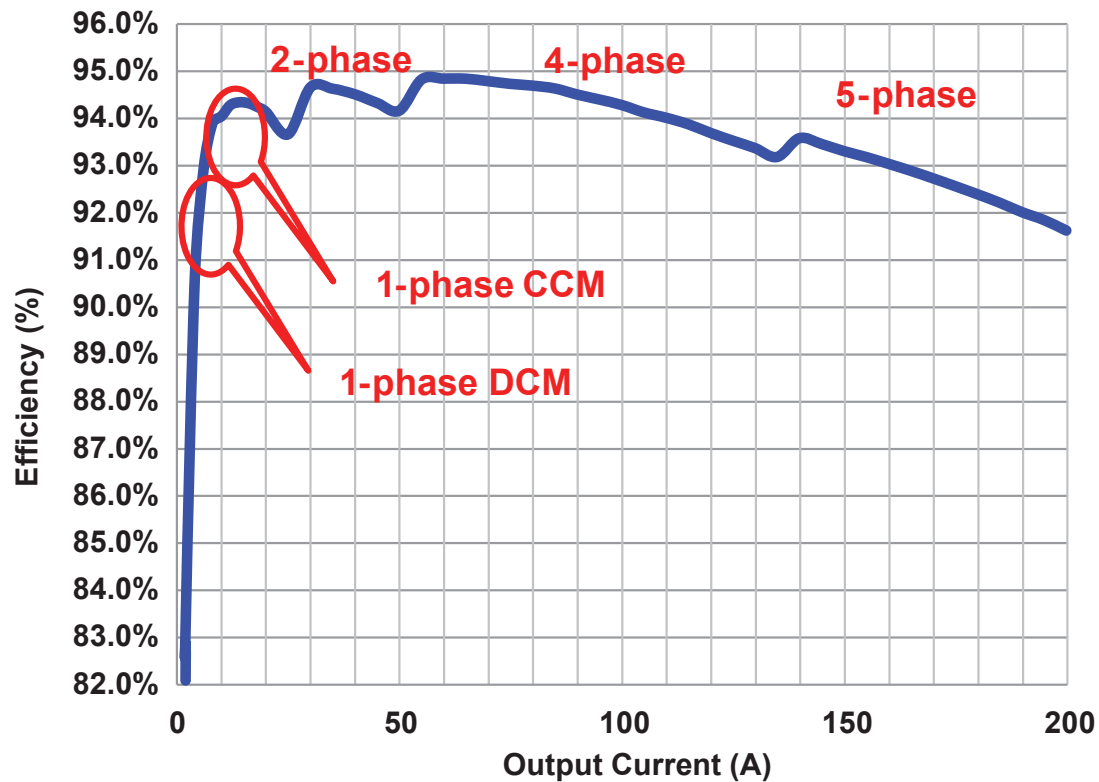
# TI D-CAP+™ – High Efficiency



TPS53661 + CSD95372B with 12 V<sub>IN</sub> to 1.8 V<sub>OUT</sub> @ 600 kHz, 150 nH


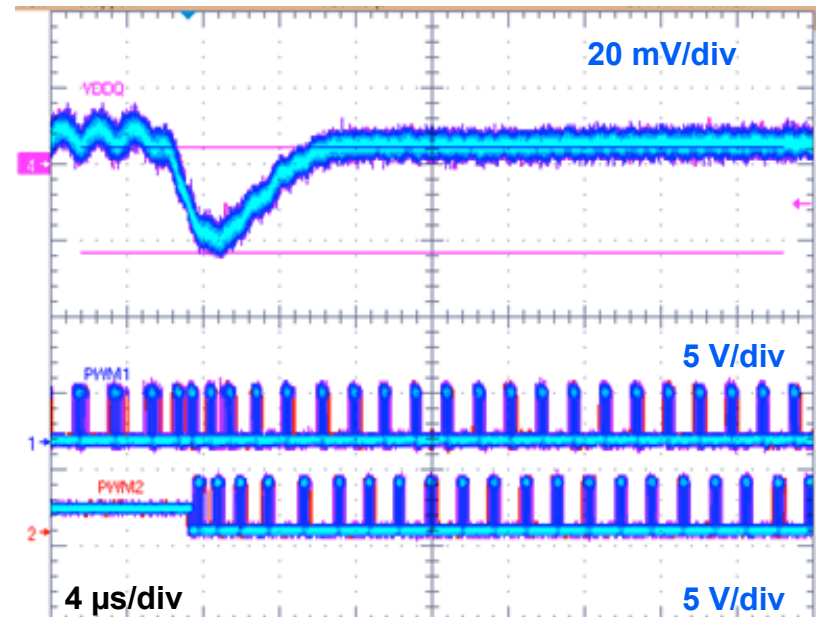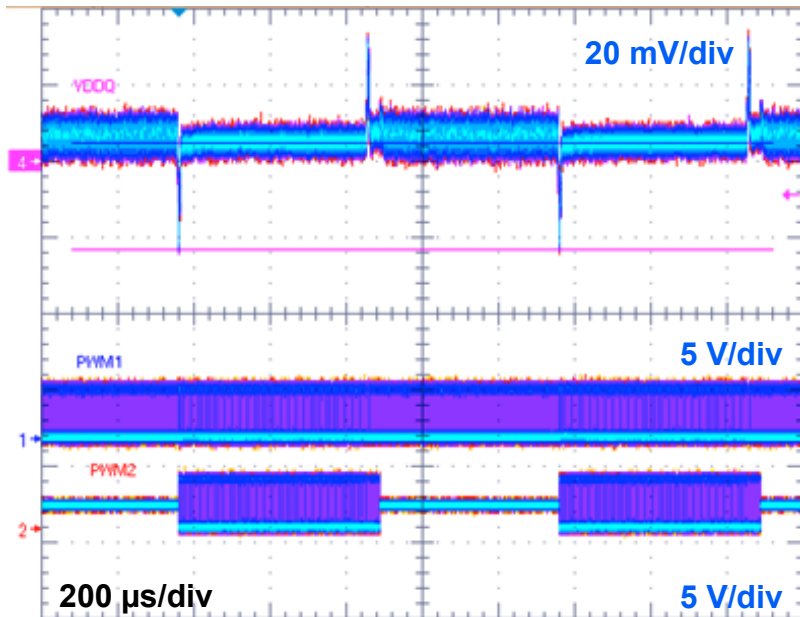
# TI D-CAP+™ – Fast Phase Adding


120 nH @ 500 kHz with 2x470  $\mu$ F/4.5 m $\Omega$  + 8x22  $\mu$ F/DIMM

LF RR @ 1 kHz, 50% duty cycle (@ sensing point) 14.2 A-59.5 A @ 11.3 A/ $\mu$ s




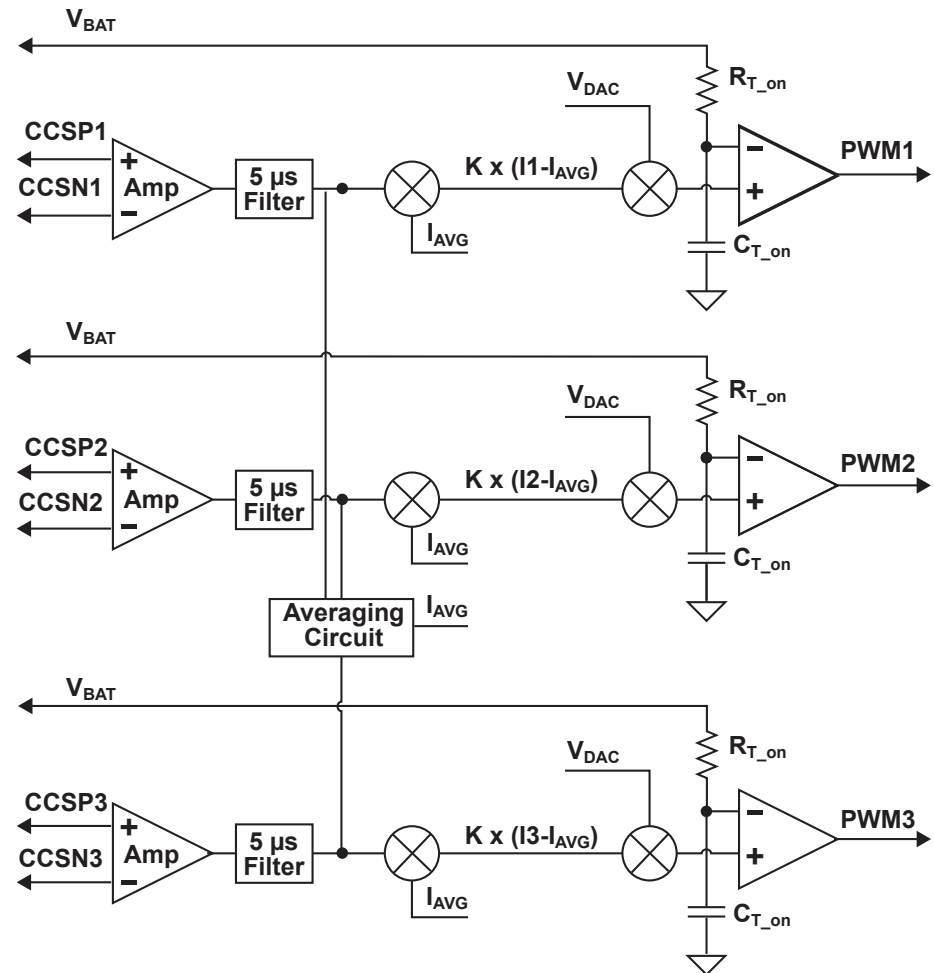
# TI D-CAP+™ – Dynamic Current Sharing



- Currents are amplified, filtered and compared with average current
- At each on-time, the on-time reference (DAC) is “tweaked” by a voltage equivalent to  $K \times (I_{IN} - I_{AVG})$
- Since filtering is light ( $5 \mu\text{s}$ ), system response is  $< 25 \mu\text{s}$
- Current sharing loop analysis paper is available on request



# TI D-CAP+™ – Dynamic Current Sharing

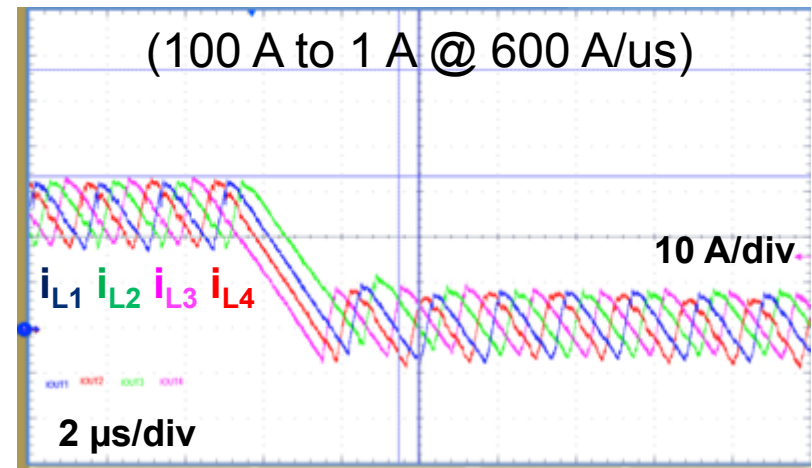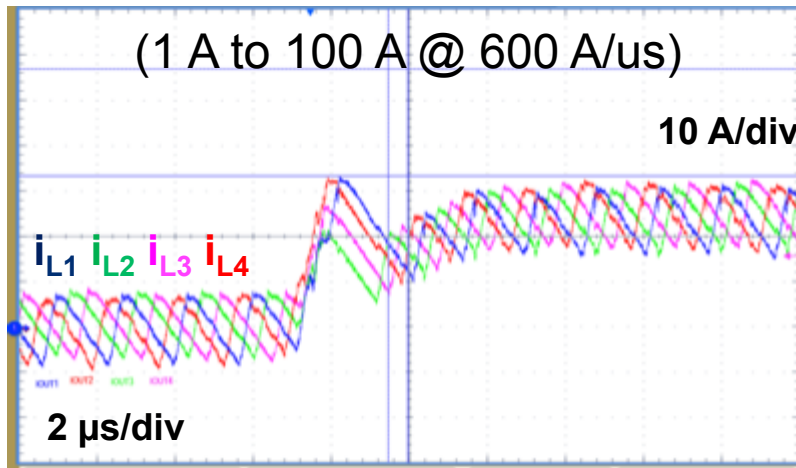

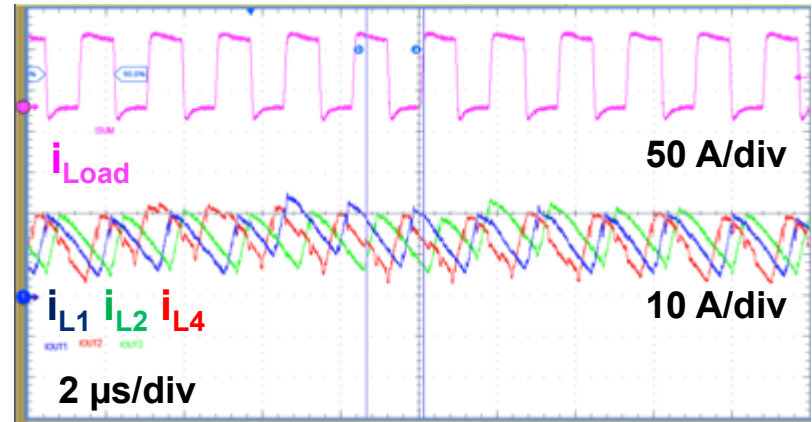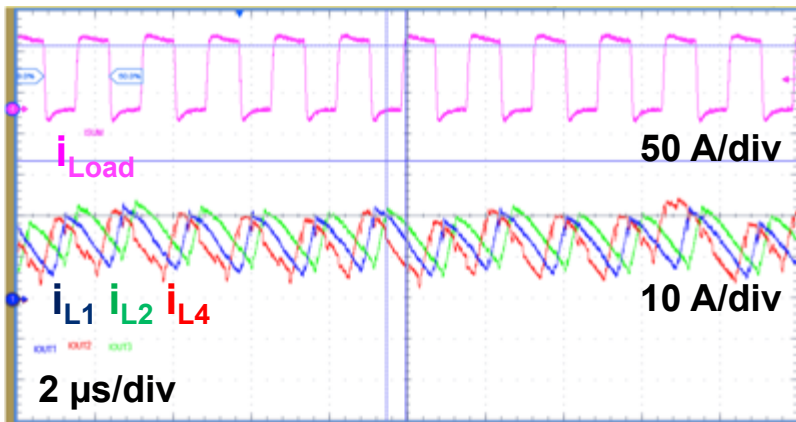(1 A to 100 A @ 600 A/ $\mu$ s and Load Frequency = Switching Frequency)





# Comparisons of TI D-CAP™ Families

Control Architecture	Features
D-CAP™	<ul style="list-style-type: none"><li>• Adaptive on-time control</li><li>• Fast load transient response</li><li>• Ramp compensation built-in</li><li>• High efficiency @ light loads</li></ul>
D-CAP2™	<ul style="list-style-type: none"><li>• Internal ripple compensation for MLCCs</li></ul>
D-CAP3™	<ul style="list-style-type: none"><li>• Sample-and-hold for DC accuracy improvement for CCM/DCM</li><li>• Adaptive ripple compensation</li></ul>
D-CAP+™	<ul style="list-style-type: none"><li>• With actual current feedbacks</li><li>• Extension to multi-phase applications</li><li>• Dynamic current sharing</li><li>• Dynamic phase shedding</li></ul>


# COT Control – Advantages and Challenges

Advantages	Disadvantages
Simple design, no compensation required	Variable switching frequency (Solution: D-CAP/D-CAP2/D-CAP3/D-CAP+)
Excellent load transient response	Sensitive to PCB design for jitter (Solution: D-CAP/D-CAP2/D-CAP3/D-CAP+)
Excellent line transient response	Minimum ripple requirement or output capacitor type limitations (Solution: D-CAP2/D-CAP3/D-CAP+)
Seamless DCM/CCM transitions for good light-load efficiency	Poor load/line regulation (Solution: D-CAP3/D-CAP+)
	Not easy for multi-phase configurations (Solution: D-CAP+)

# Design Example #3





## COT Control – Design Specifications

Design Specifications	
Input voltage range	5 V to 18 V
Target output voltage	1.2 V
Output current range	0 A to 6.6 A
Switching frequency	500 kHz
Controller	TPS53515

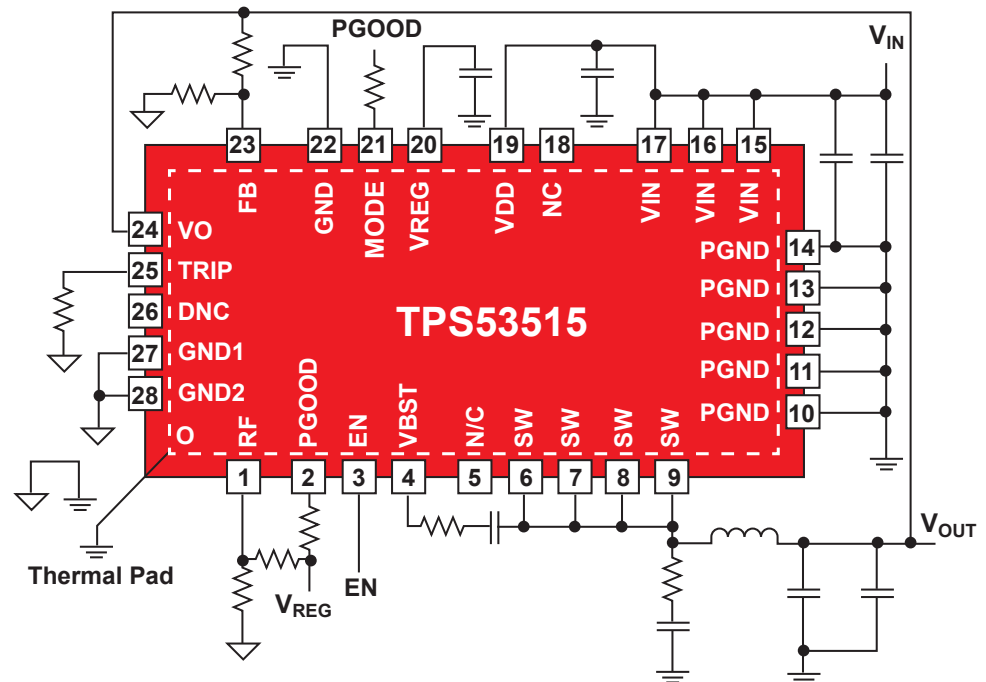

# Design Example #3


## COT Control – Performance Graph

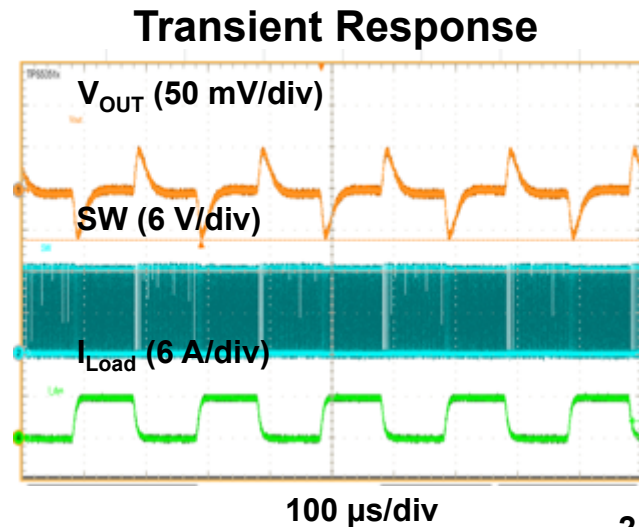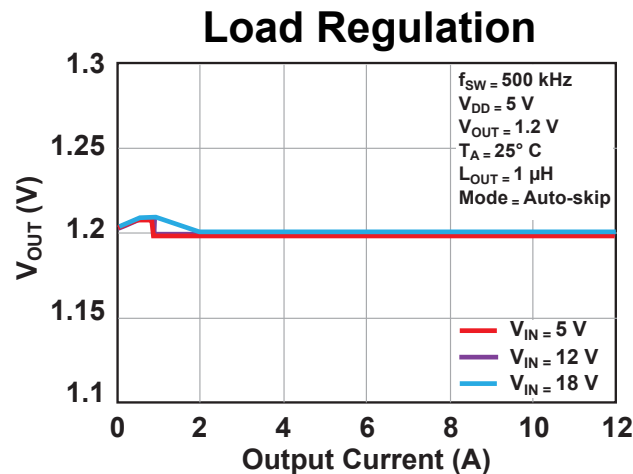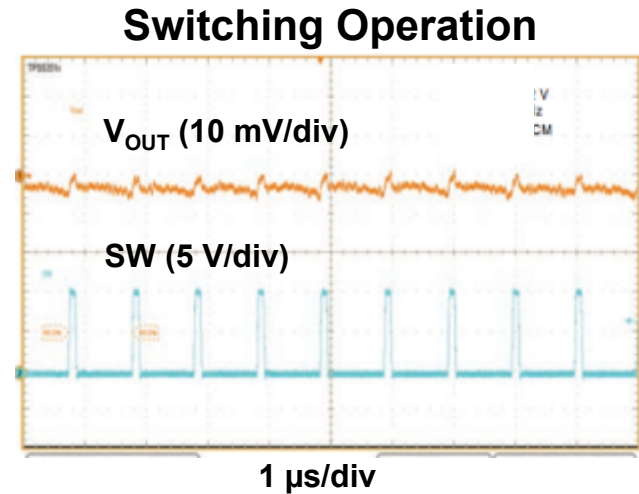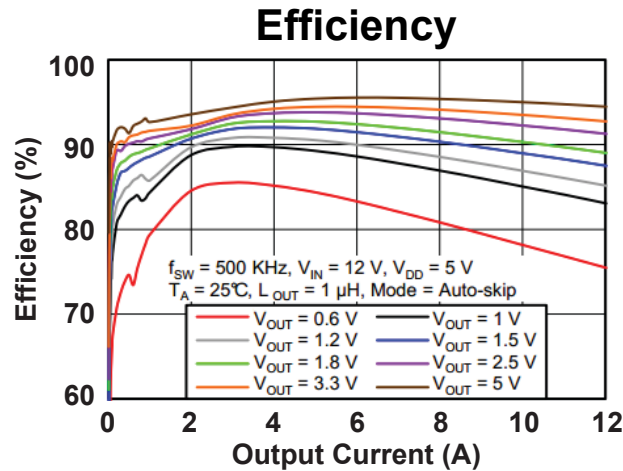

# Design Example #4

## D-CAP+ Design Specifications

Design Specifications	
Input voltage range	12 V
Target output voltage	1.6 V-1.9 V
Output current range	0 A to 189 A
Switching frequency	600 kHz
Controller	TPS53641

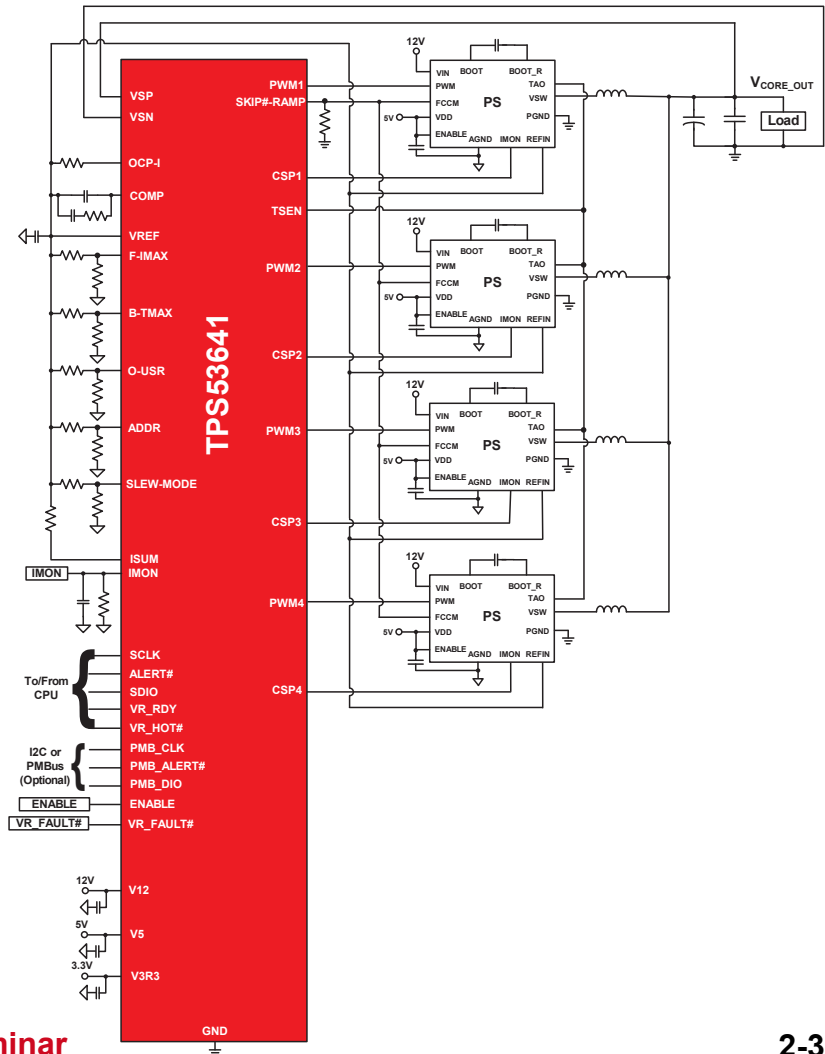


# Design Example #4


## D-CAP+ Performance Graph

12 V to 1.8 V with 4-phase operations @ 600 kHz, 150 nH, and 1 mΩ loadline

Loadline Regulation @ 25C and 105C

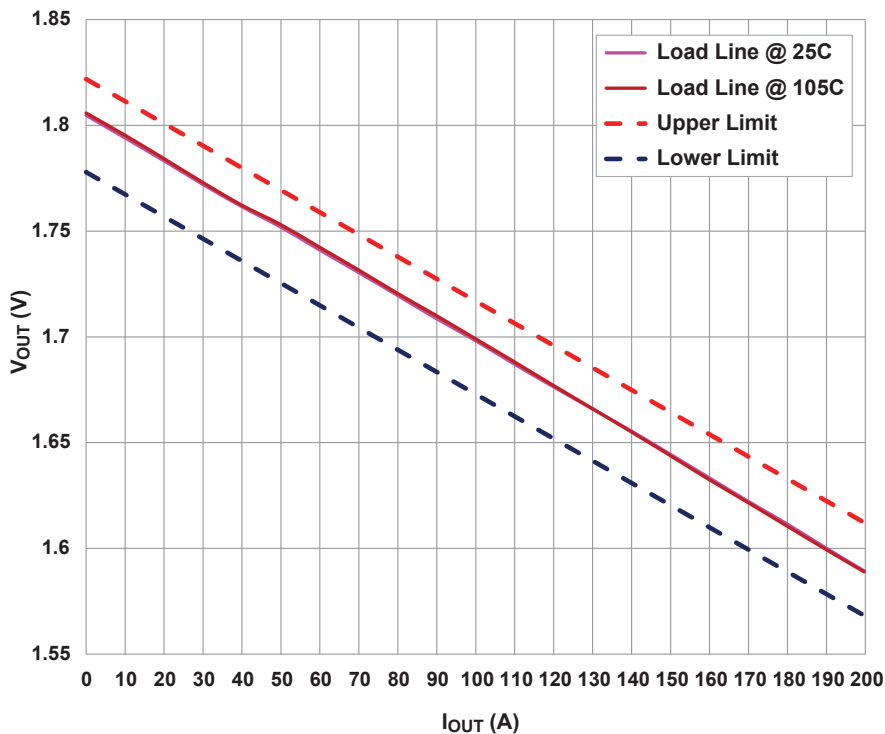

Phase Interleaving and Jitter @ 90 A

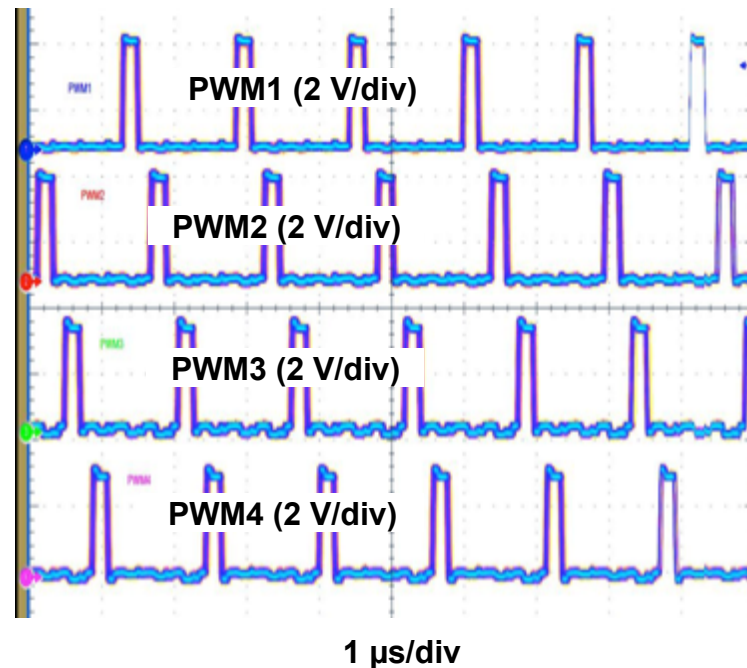


# Design Example #4
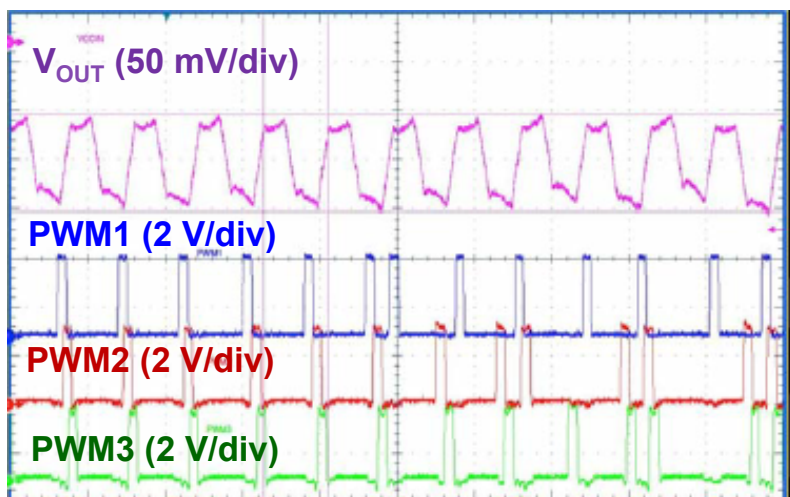
## D-CAP+ Performance Graph (2)


12 V to 1.8 V with 4-phase operations @ 600 kHz, 150 nH, and 1 mΩ loadline

High-Frequency Transient Response  
(31 A to 189 A load @ 600 kHz)




1  $\mu$ s/div

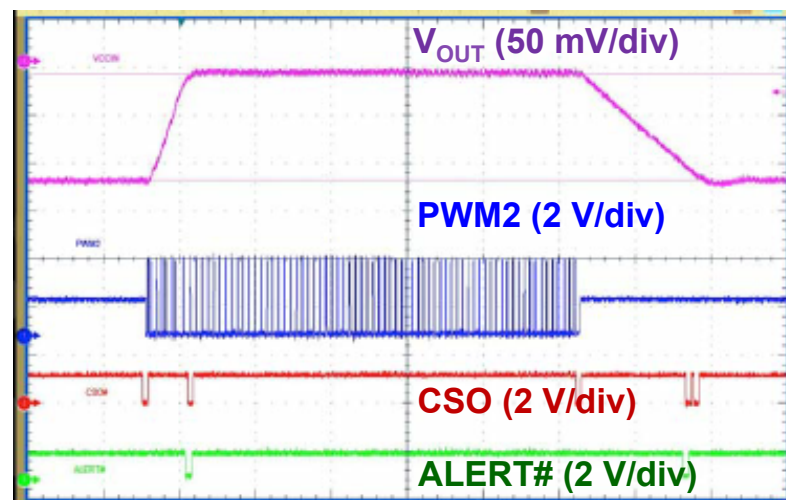Dynamic Voltage Change  
(1.6 V to 1.82 V @ 5 A)



20  $\mu$ s/div

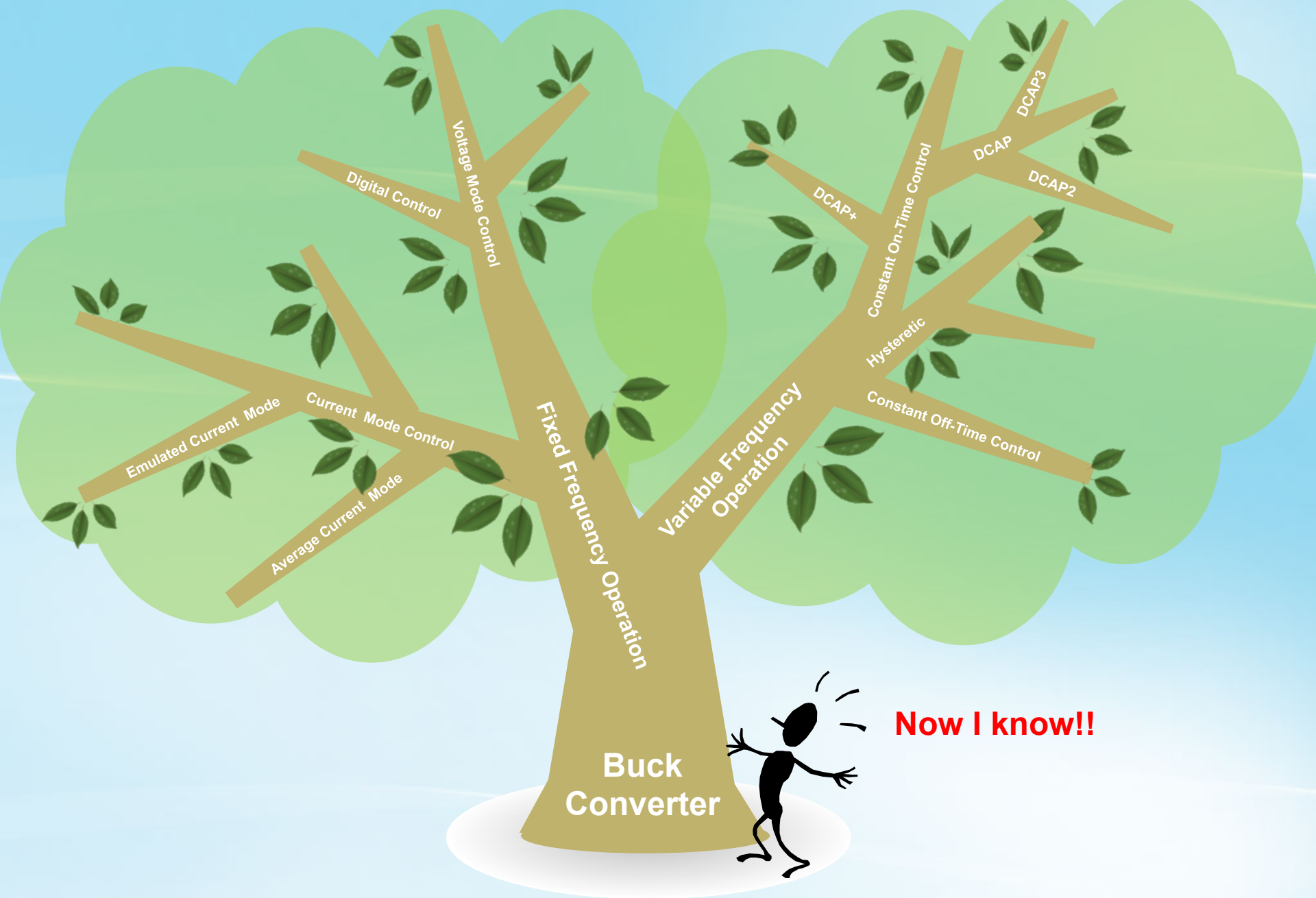

Buck Converter

**Now I know!!**



# References

- SEM 1500 - Under the Hood of Low Voltage DC/DC Converters
- SLVA301 - Loop Stability Analysis of Voltage Mode Buck Regulator with Different Output Capacitor Types – Continuous and Discontinuous Modes
- Easy Calculation Yields Load Transient Response
  - <http://powerelectronics.com/site-files/powerelectronics.com/files/archive/powerelectronics.com/ar/502pet23.pdf>
- Controlling Output Ripple and Achieving ESR Independence in Constant On-Time (COT) Regulator Designs
  - <http://www.ti.com/lit/an/snva166a/snva166a.pdf>
- Buck Regulator Topologies for Wide Input/Output Voltage Differentials
  - <http://www.ti.com/lit/an/snva594/snva594.pdf>
- Switching Power Supply Topology Voltage Mode vs. Current Mode
  - <http://www.ti.com/general/docs/litabsmultiplefilelist.tsp?literatureNumber=slua119>
- Modeling, Analysis and Compensation of the Current-Mode Converter
  - <http://www.ti.com/general/docs/lit/getliterature.tsp?baseLiteratureNumber=SLUA101&fileType=pdf>

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)